

Electrical Circuit (1)

Source Transformation (week9 class1)

Dr. Akram Al-Mahrouk



Philadelphia University

Chapter 4 Circuit Theorems 127

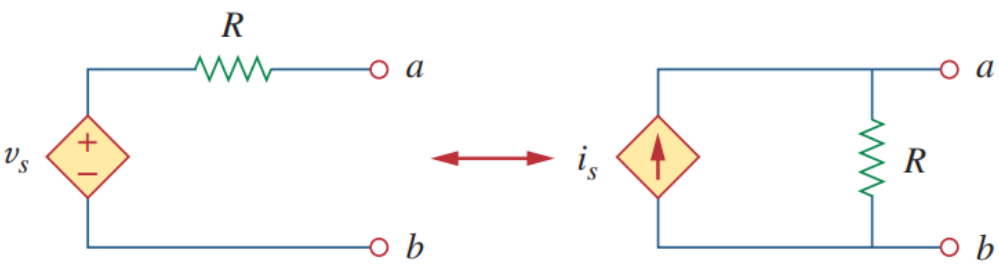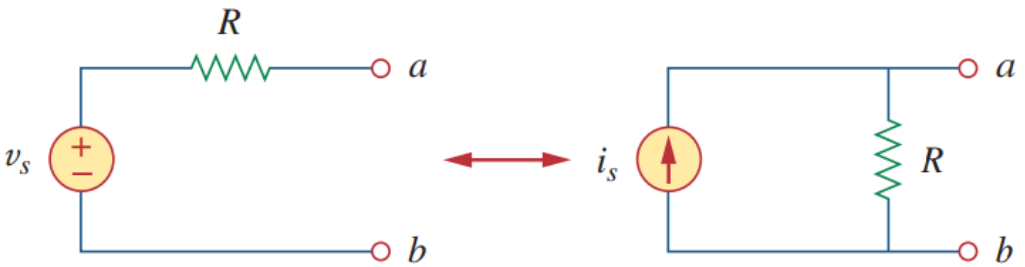- 4.1 Introduction 128
- 4.2 Linearity Property 128
- 4.3 Superposition 130
- 4.4 Source Transformation 135
- 4.5 Thevenin's Theorem 139
- 4.6 Norton's Theorem 145
- 4.7 †Derivations of Thevenin's
and Norton's Theorems 149
- 4.8 Maximum Power Transfer 150
- 4.9 Verifying Circuit Theorems
with *PSpice* 152
- 4.10 †Applications 155
 - 4.10.1 Source Modeling
 - 4.10.2 Resistance Measurement
- 4.11 Summary 160
 - Review Questions 161
 - Problems 162
 - Comprehensive Problems 173


Source Transformation

A **source transformation** is the process of replacing a voltage source v_s in series with a resistor R by a current source i_s in parallel with a resistor R , or vice versa.







Source Transformation

Ex1)

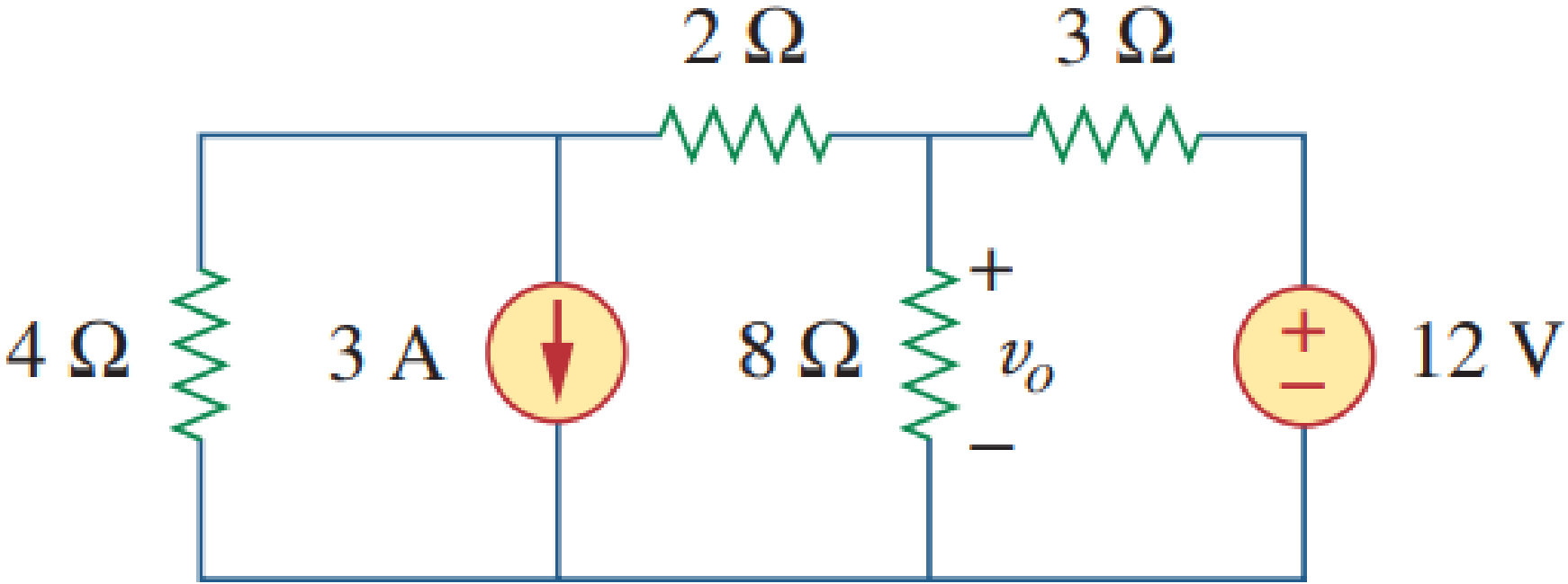




Source Transformation

Ex1)

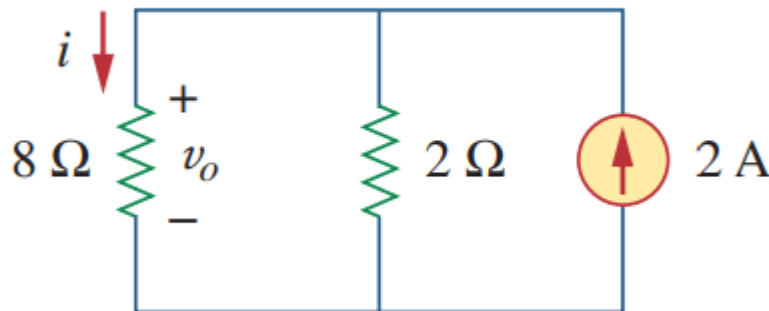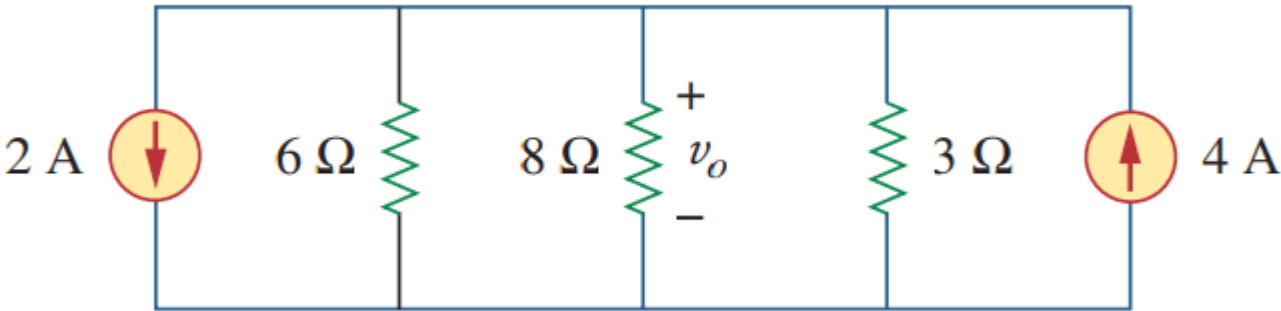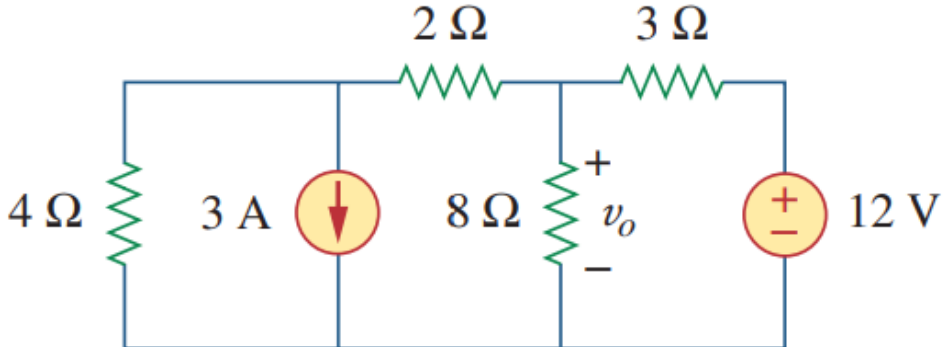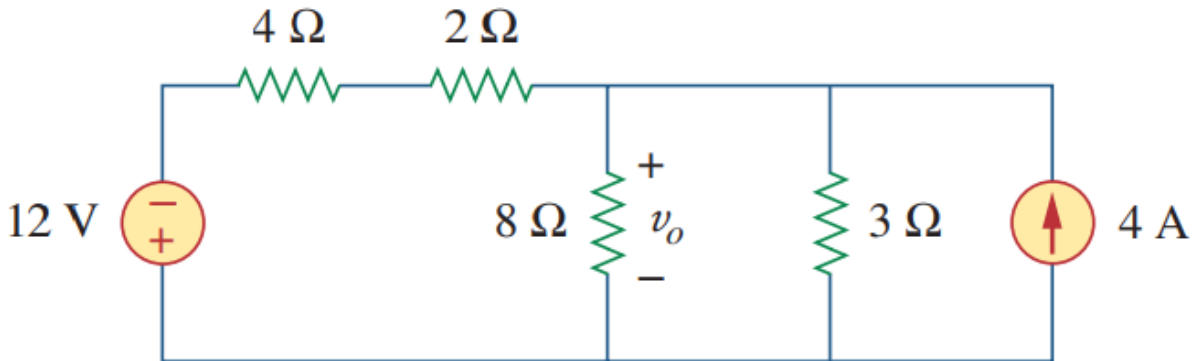




Source Transformation

Ex2)

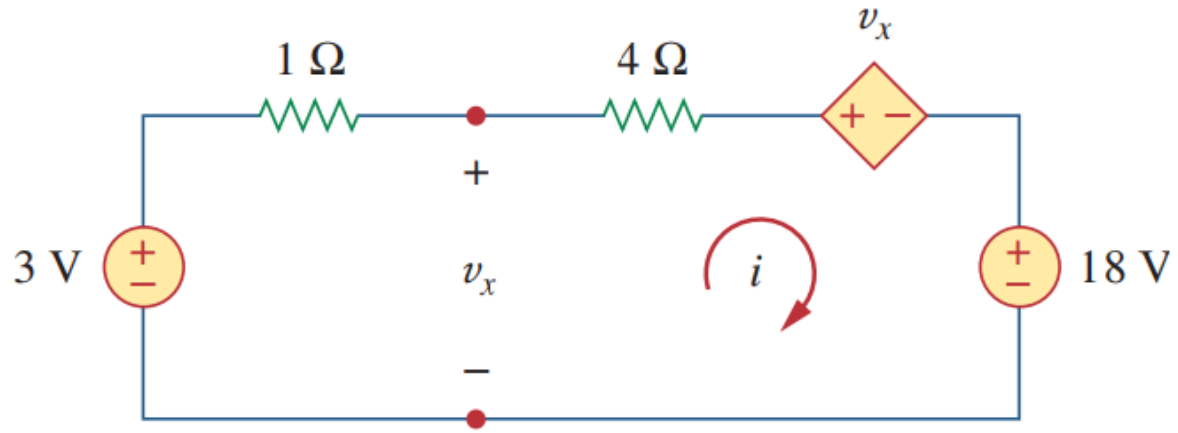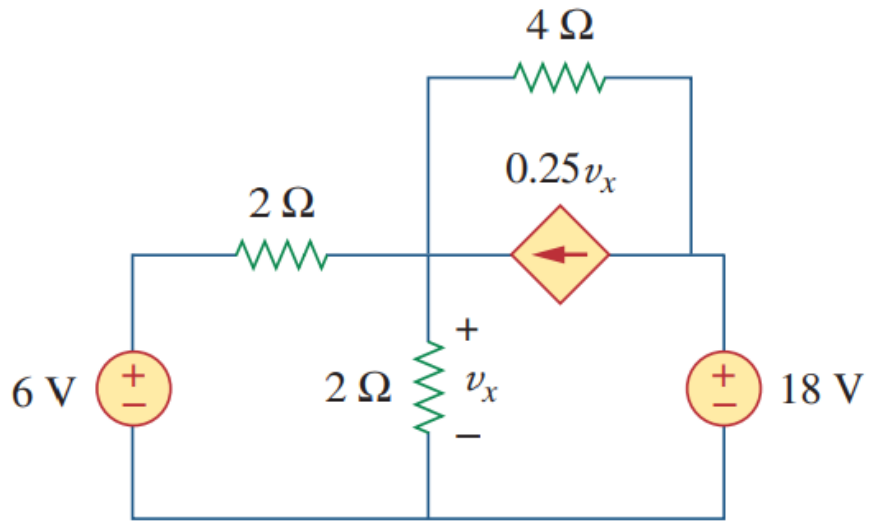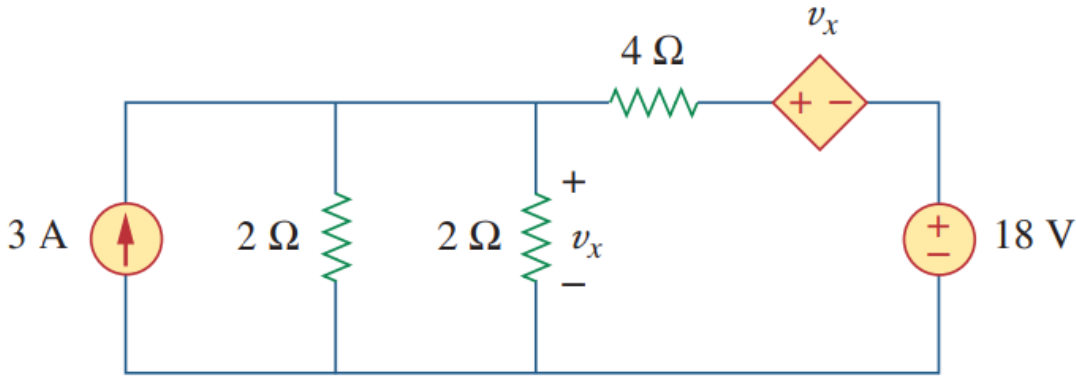

Source Transformation

Ex2)

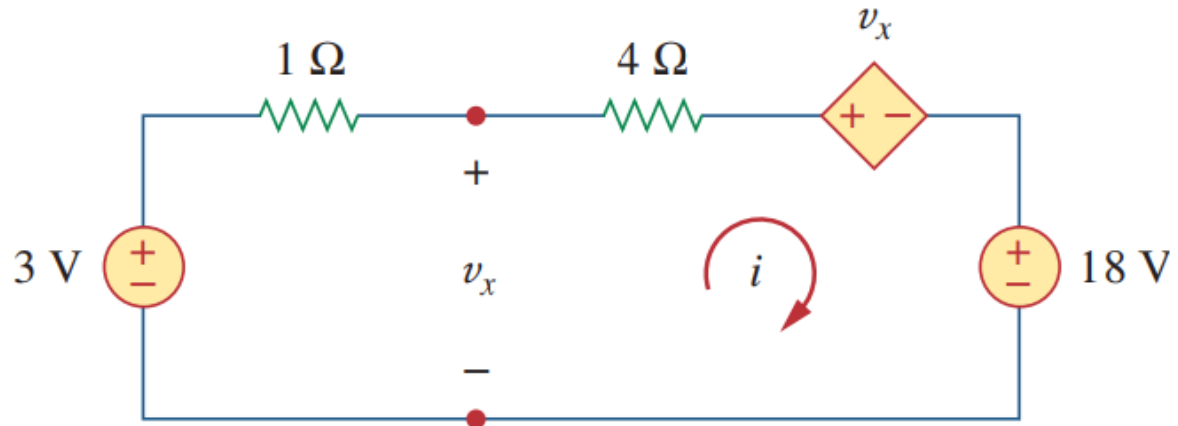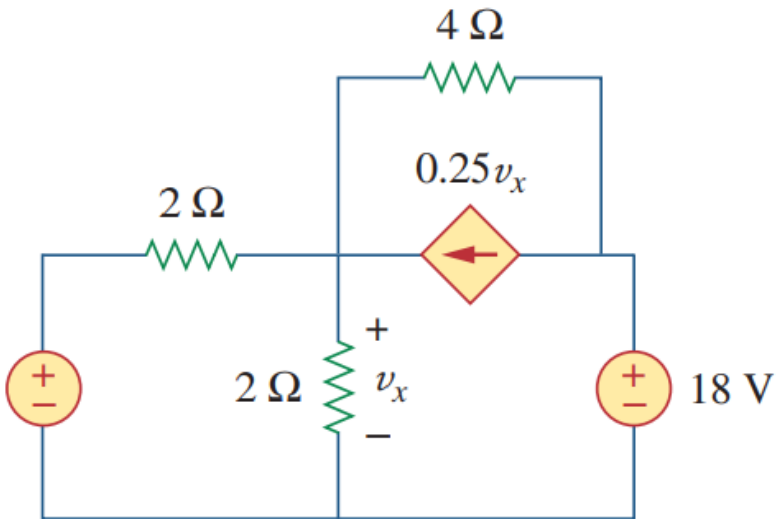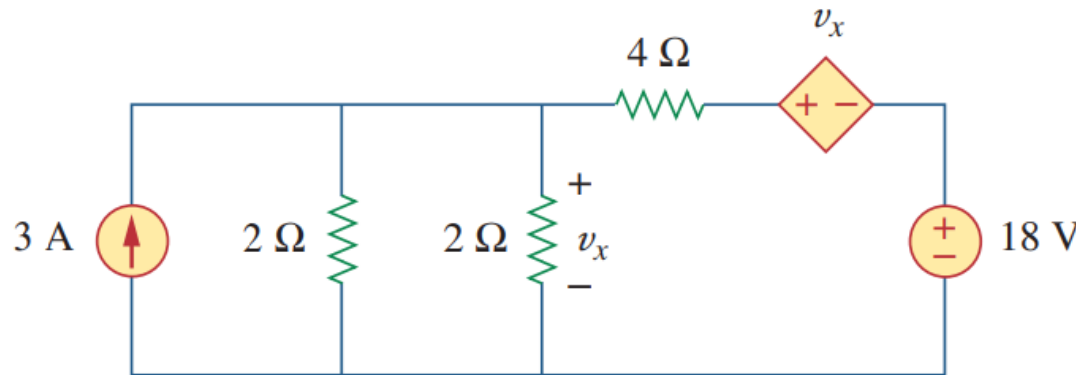

$$-3 + i + 4i + (v_x) + 18 = 0$$


$$-3 + i + 4i + (3 - i) + 18 = 0$$

$$4i = -18$$

$$i = -4.5A$$

Source Transformation

Ex3)

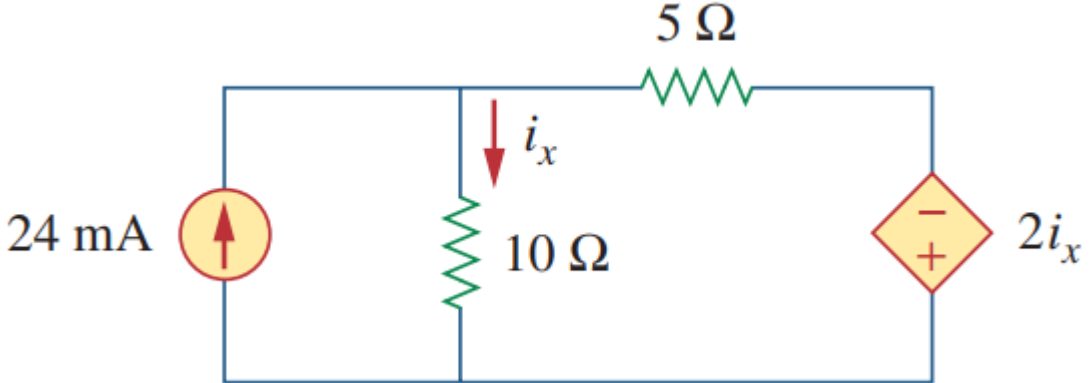


Answer: 7.059 mA.

Source Transformation

$$-24mA + \frac{v}{10} + \frac{v}{5} + 2\frac{v}{10 * 5} = 0$$

$$v = -70.5mV$$

$$i_x = \frac{70.5m}{10} = 7.05 mA$$

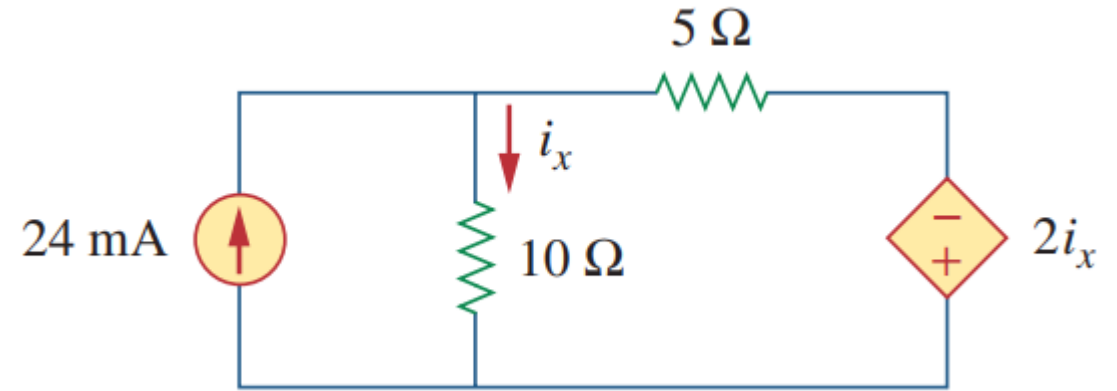

Answer: 7.059 mA.

