

Electrical Circuit (1)



Maximum Power Transfer (week10 class1)

Dr. Akram Al-Mahrouk
Philadelphia University

Chapter 4 Circuit Theorems 127

- 4.1 Introduction 128
- 4.2 Linearity Property 128
- 4.3 Superposition 130
- 4.4 Source Transformation 135
- 4.5 Thevenin's Theorem 139
- 4.6 Norton's Theorem 145
- 4.7 †Derivations of Thevenin's
and Norton's Theorems 149
- 4.8 Maximum Power Transfer 150
- 4.9 Verifying Circuit Theorems
with *PSpice* 152
- 4.10 †Applications 155
 - 4.10.1 Source Modeling
 - 4.10.2 Resistance Measurement
- 4.11 Summary 160
 - Review Questions 161
 - Problems 162
 - Comprehensive Problems 173


Maximum Power Transfer

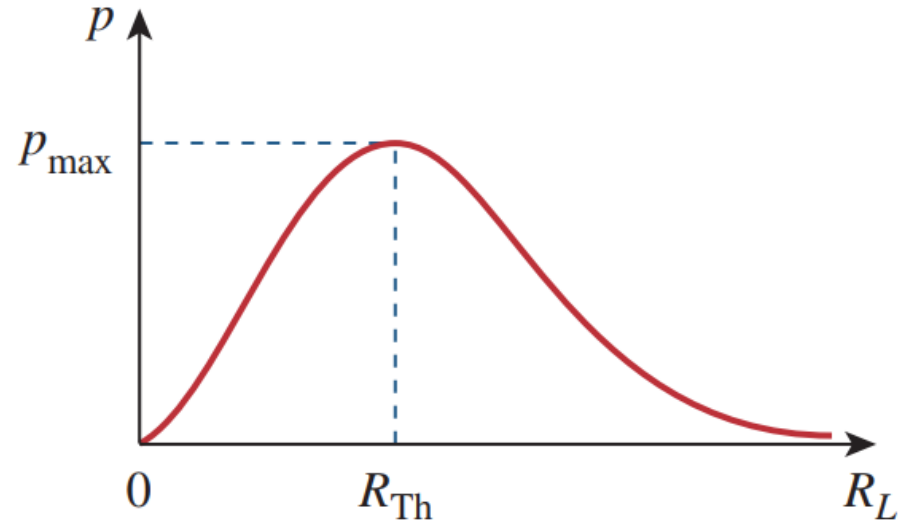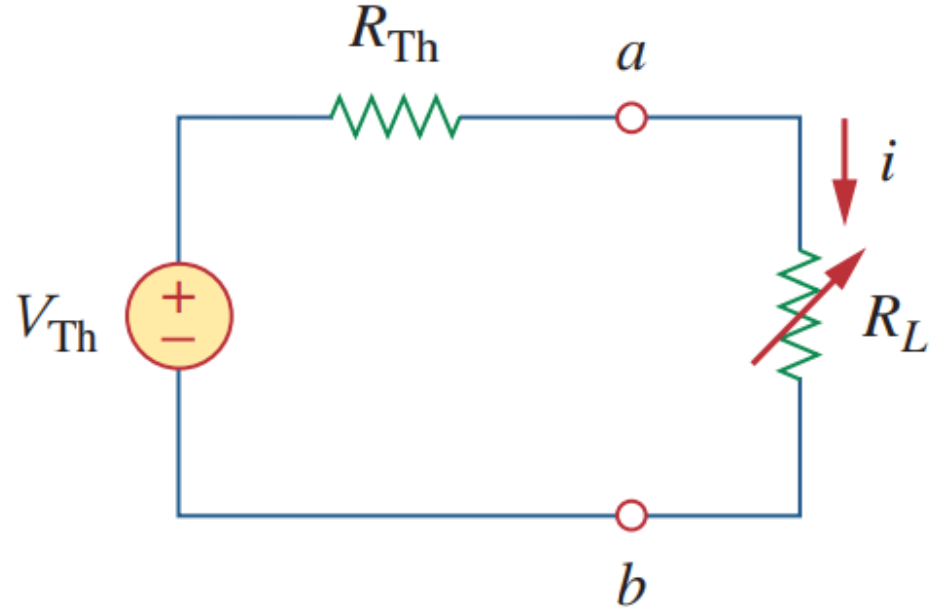

$$p = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$


$$p_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

Maximum Power Transfer

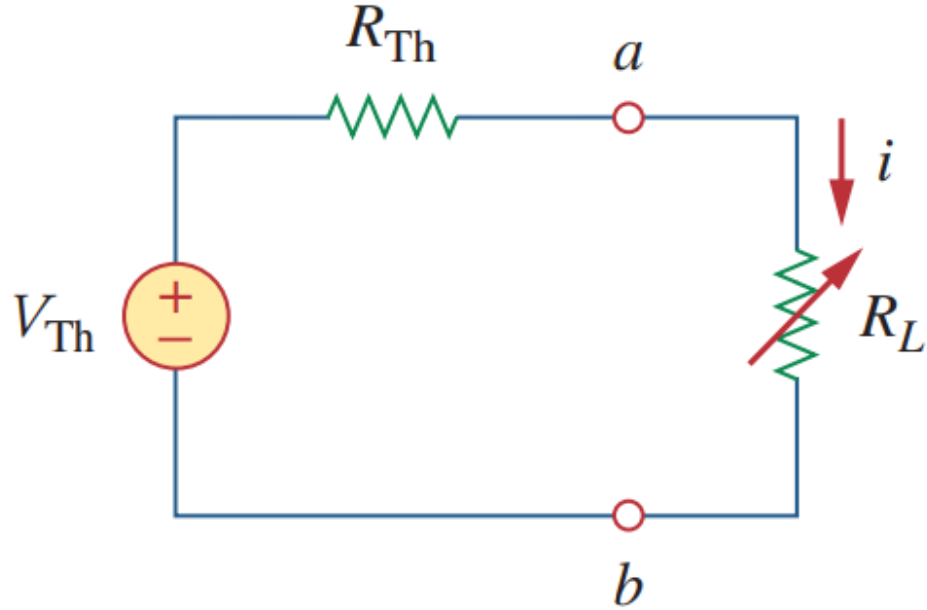



$$p = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

$$p_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

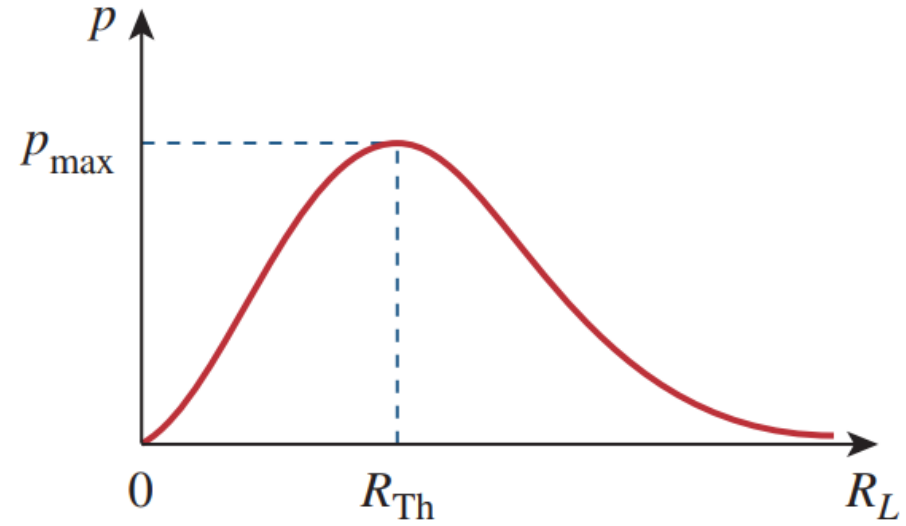


V_{TH}	R_{TH}	R_{LOAD}	P_{LOAD}
4	3	1	1
4	3	2	
4	3	3	1.3
4	3	4	
4	3	5	1.25
4	3	6	
4	3	7	

Maximum Power Transfer

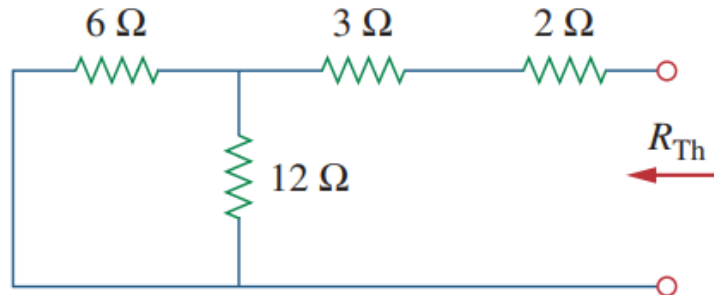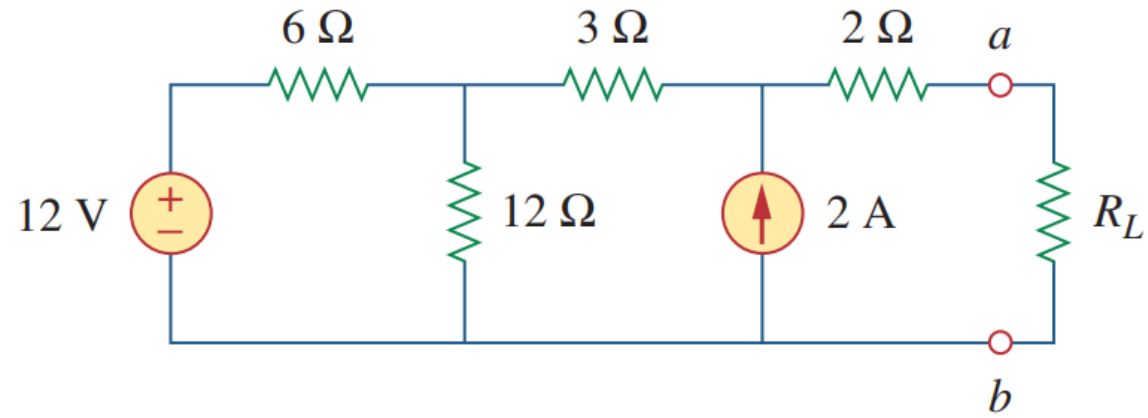
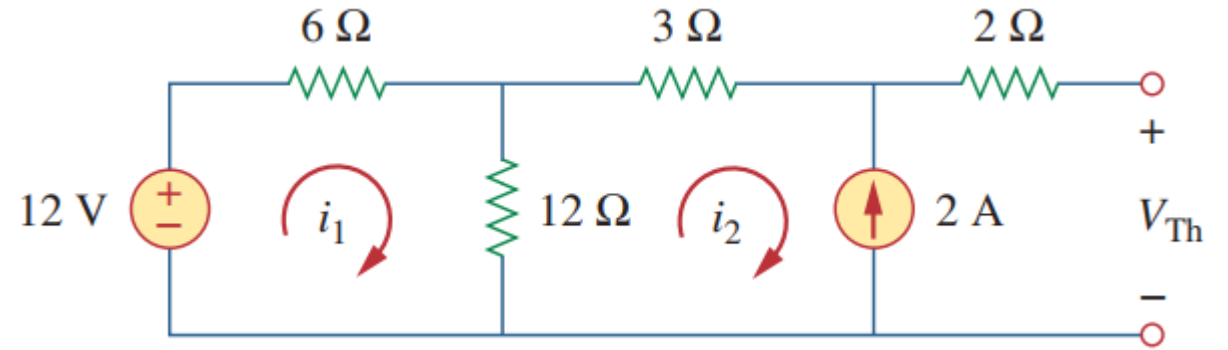
$$R_{Th} = 2 + 3 + 6 \parallel 12 = 5 + \frac{6 \times 12}{18} = 9 \Omega$$



$$V_{Th} = 22 \text{ V}$$

$$R_L = R_{Th} = 9 \Omega$$

$$p_{\max} = \frac{V_{Th}^2}{4R_L} = \frac{22^2}{4 \times 9} = 13.44 \text{ W}$$

