

Electrical Circuit (1)

Discharge RC and RL (week12 class1)


Dr. Akram Al-Mahrouk

Philadelphia University

Chapter 7 First-Order Circuits 253

7.1	Introduction	254
7.2	The Source-Free RC Circuit	254
7.3	The Source-Free RL Circuit	259
7.4	Singularity Functions	265
7.5	Step Response of an RC Circuit	273
7.6	Step Response of an RL Circuit	280
7.7	†First-Order Op Amp Circuits	284
7.8	Transient Analysis with <i>PSpice</i>	289
7.9	†Applications	293
	7.9.1 Delay Circuits	
	7.9.2 Photoflash Unit	
	7.9.3 Relay Circuits	
	7.9.4 Automobile Ignition Circuit	
7.10	Summary	299
	Review Questions	300
	Problems	301
	Comprehensive Problems	311

The Source-Free RC Circuit

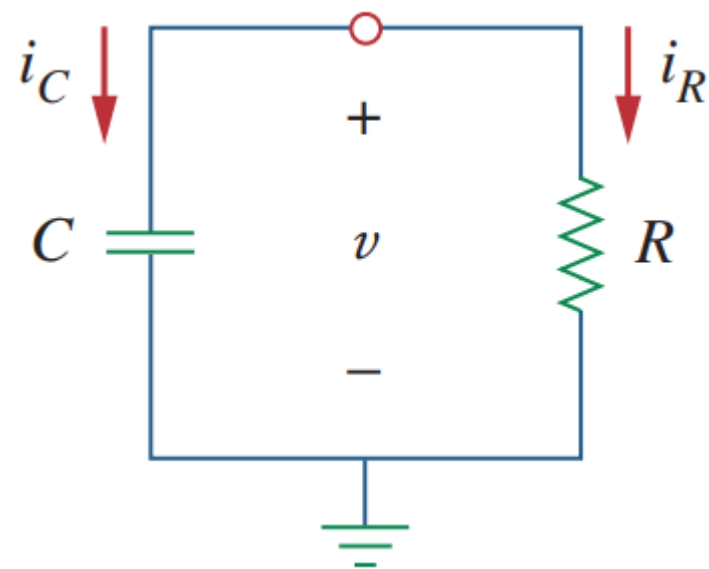

$$v(0) = V_0$$

$$w(0) = \frac{1}{2} CV_0^2$$

$$i_C + i_R = 0$$

$$C \frac{dv}{dt} + \frac{v}{R} = 0$$

$$\frac{dv}{dt} + \frac{v}{RC} = 0$$


$$\frac{dv}{v} = -\frac{1}{RC} dt$$

$$\ln v = -\frac{t}{RC} + \ln A$$

$$v(t) = Ae^{-t/RC}$$

$$v(t) = V_0 e^{-t/RC}$$

The Source-Free RC Circuit

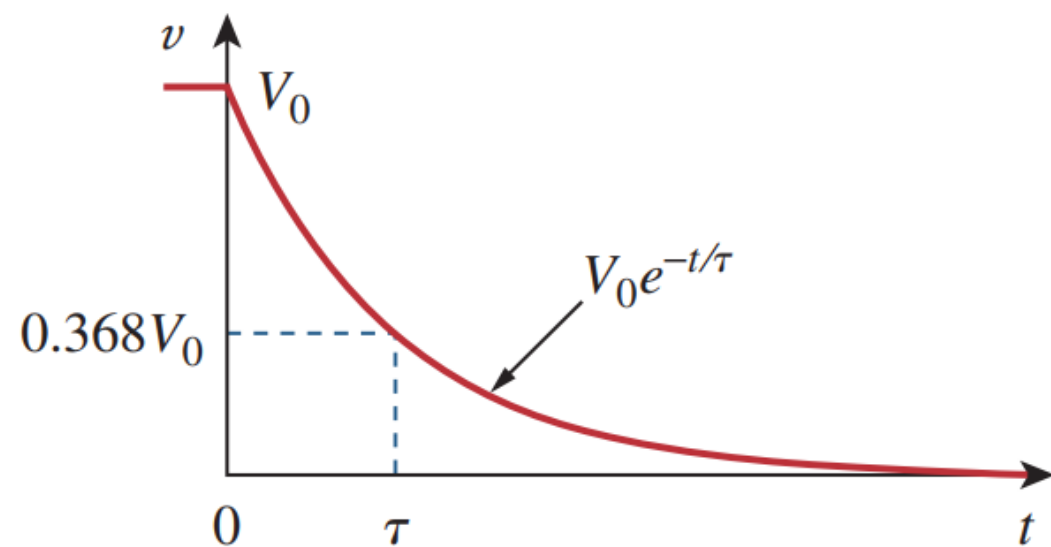


$$\tau = RC$$

TABLE 7.1

Values of $v(t)/V_0 = e^{-t/\tau}$.

t	$v(t)/V_0$
τ	0.36788
2τ	0.13534
3τ	0.04979
4τ	0.01832
5τ	0.00674

The Source-Free RC Circuit

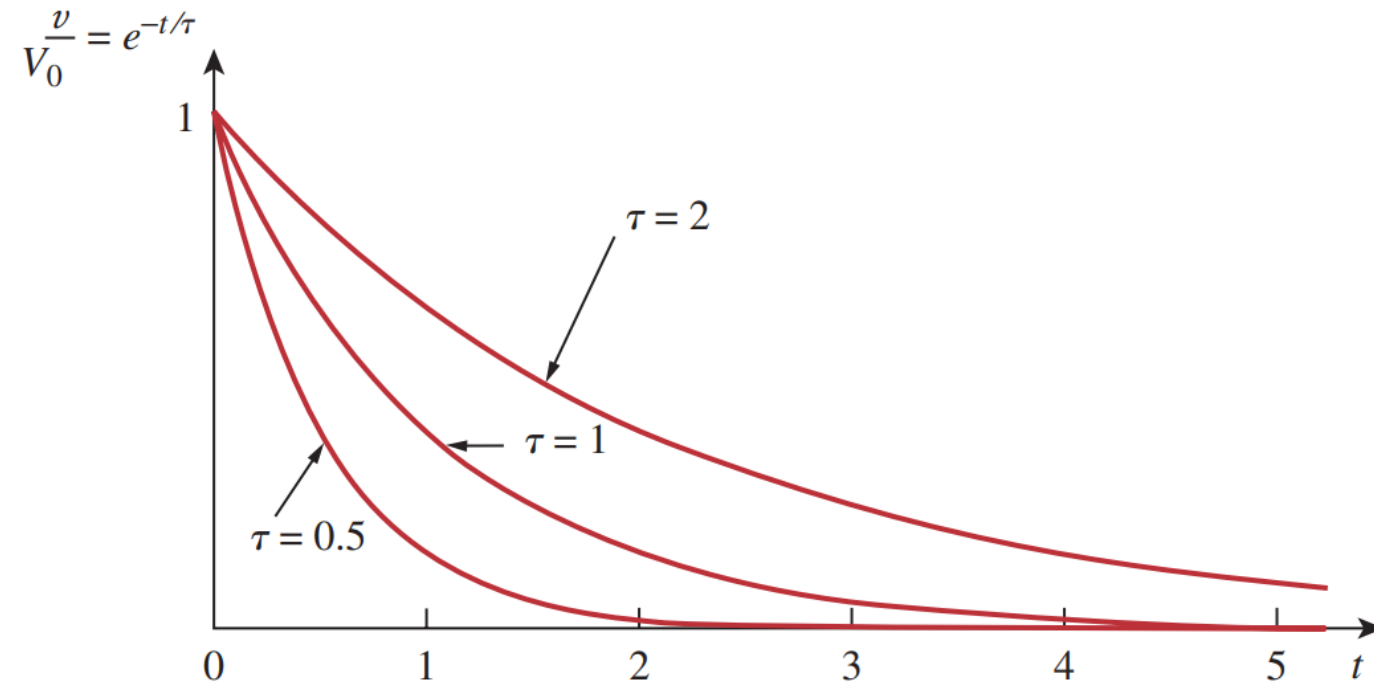


The Key to Working with a Source-Free RC Circuit Is Finding:

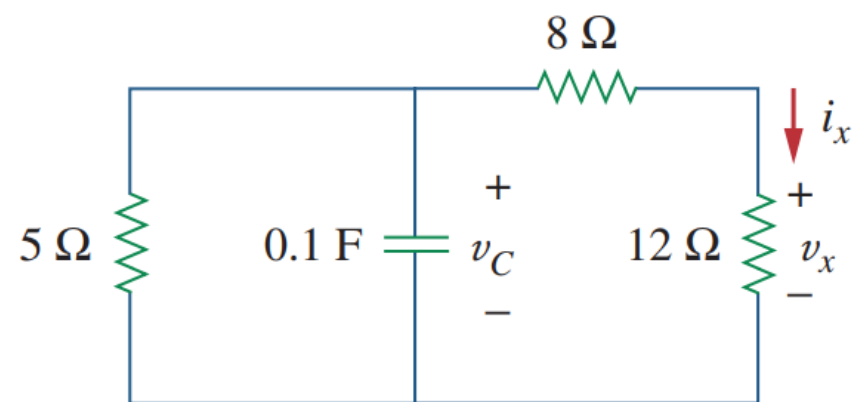1. The initial voltage $v(0) = V_0$ across the capacitor.
2. The time constant τ .

The Source-Free RC Circuit

In Fig. 7.5, let $v_C(0) = 15$ V. Find v_C , v_x , and i_x for $t > 0$.



$$R_{\text{eq}} = \frac{20 \times 5}{20 + 5} = 4\ \Omega$$

$$\tau = R_{\text{eq}}C = 4(0.1) = 0.4\ \text{s}$$

Figure 7.5

For Example 7.1.


$$v = v(0)e^{-t/\tau} = 15e^{-t/0.4}\ \text{V}, \quad v_C = v = 15e^{-2.5t}\ \text{V}$$

$$v_x = \frac{12}{12 + 8}v = 0.6(15e^{-2.5t}) = 9e^{-2.5t}\ \text{V}$$

$$i_x = \frac{v_x}{12} = 0.75e^{-2.5t}\ \text{A}$$

The Source-Free RC Circuit

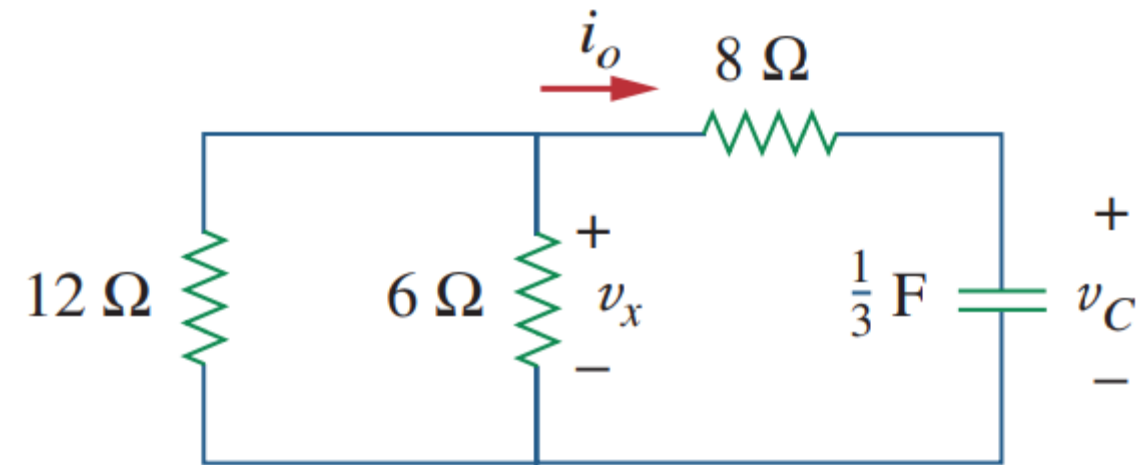Refer to the circuit in Fig. 7.7. Let $v_C(0) = 60$ V. Determine v_C , v_x , and i_o for $t \geq 0$.



$$60e^{-0.25t}\text{ V}, 20e^{-0.25t}\text{ V}, -5e^{-0.25t}\text{ A}.$$

$$R_{eq} = \frac{12 * 6}{12 + 6} + 8 = 12$$


$$V_C = 60e^{\frac{-1}{12 * \frac{1}{3}}t} = 60e^{-0.25t}$$

$$V_x = \frac{4}{8 + 4} * 60 * e^{\frac{-1}{12 * \frac{1}{3}}t} = 20e^{-0.25t}$$


$$i_o = \frac{-60}{12} * e^{\frac{-1}{12 * \frac{1}{3}}t} = -5e^{-0.25t}$$

The Source-Free RC Circuit

QUIZZZZ

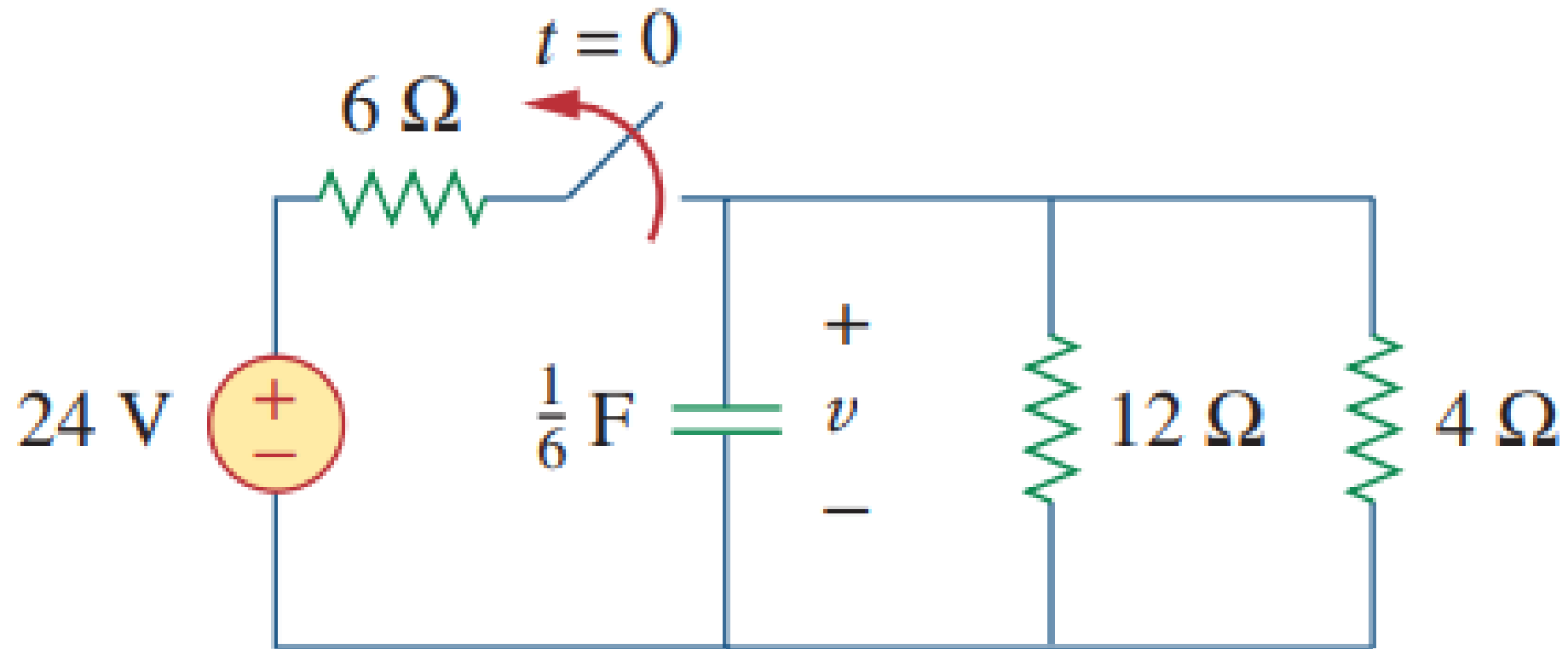

The Source-Free RL Circuit

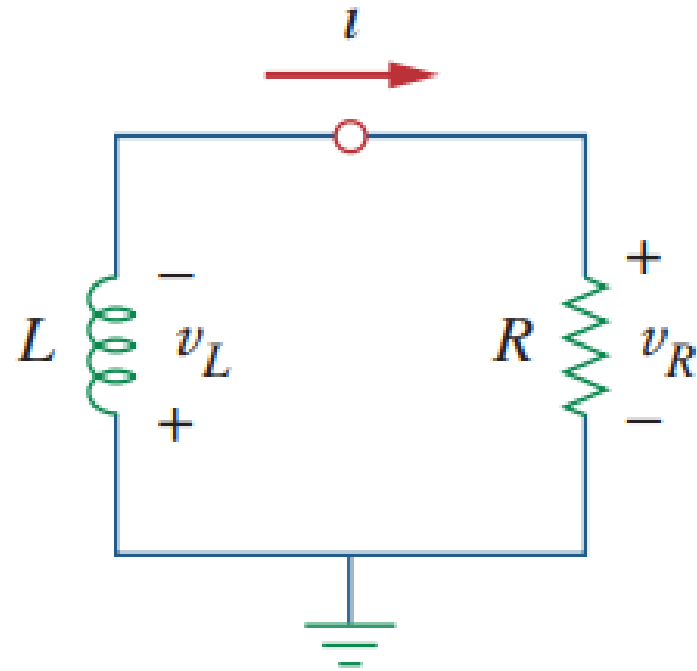

$$i(0) = I_0$$

$$w(0) = \frac{1}{2} L I_0^2$$

$$v_L + v_R = 0$$

$$L \frac{di}{dt} + Ri = 0$$

$$\frac{di}{dt} + \frac{R}{L} i = 0$$

$$\int_{I_0}^{i(t)} \frac{di}{i} = - \int_0^t \frac{R}{L} dt$$


$$\ln \frac{i(t)}{I_0} = - \frac{Rt}{L}$$

$$i(t) = I_0 e^{-Rt/L}$$

$$\tau = \frac{L}{R}$$

$$i(t) = I_0 e^{-t/\tau}$$


The Source-Free RL Circuit

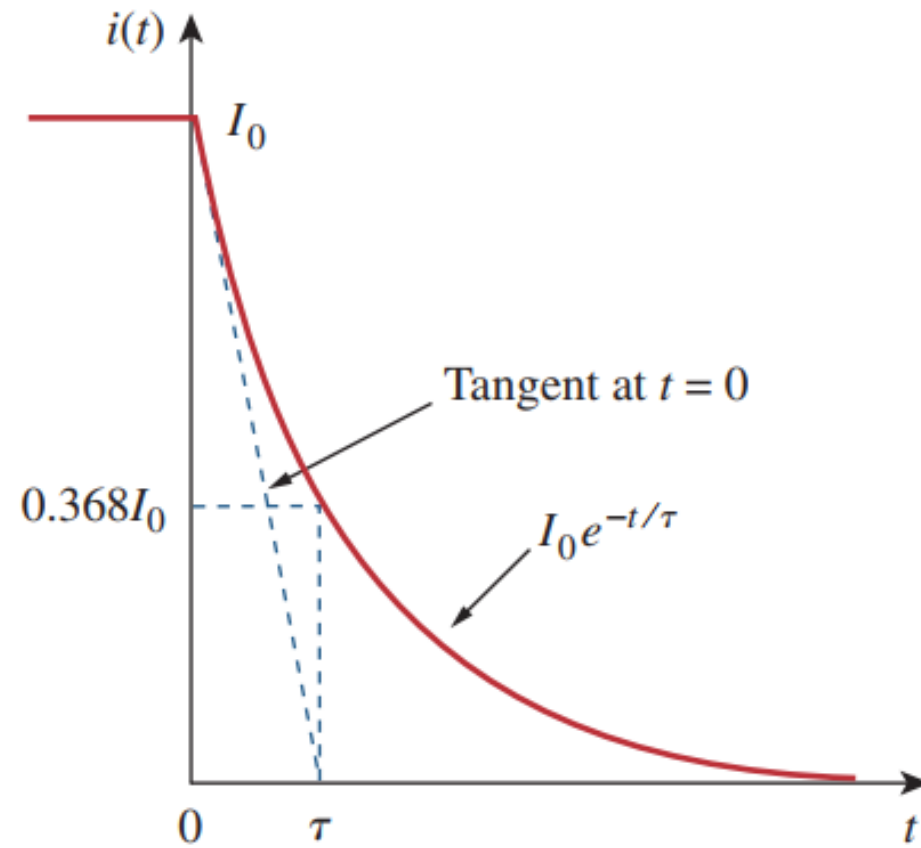

The Key to Working with a Source-Free RL Circuit Is to Find:

1. The initial current $i(0) = I_0$ through the inductor.
2. The time constant τ of the circuit.

The Source-Free RL Circuit

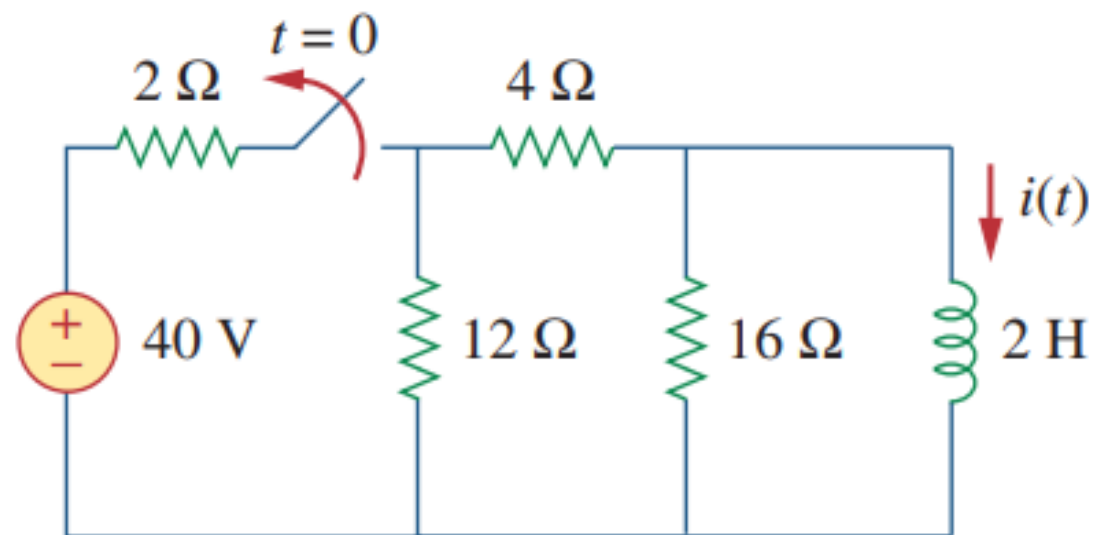

$$\frac{4 \times 12}{4 + 12} = 3 \Omega$$

$$i_1 = \frac{40}{2 + 3} = 8 \text{ A}$$

$$i(t) = \frac{12}{12 + 4} i_1 = 6 \text{ A}, \quad t < 0$$

$$R_{\text{eq}} = (12 + 4) \parallel 16 = 8 \Omega$$

$$\tau = \frac{L}{R_{\text{eq}}} = \frac{2}{8} = \frac{1}{4} \text{ s}$$

$$i(t) = i(0)e^{-t/\tau} = 6e^{-4t} \text{ A}$$

The Source-Free RL Circuit


$$R_{eq} = 24 \parallel 12 \parallel 8 = 8 \parallel 8 = 4 \text{ ohm}$$

$$\tau = \frac{L}{R} = \frac{2}{4} = 0.5$$

$$R_{24 \parallel 8} = \frac{24 * 8}{24 + 8} = 6 \text{ ohm}$$

$$i(t)_{t=0} = 15 \frac{6 * 12}{6 + 12} = 5 \text{ A}$$

$$i(t) = 5e^{-2t} \text{ A}$$

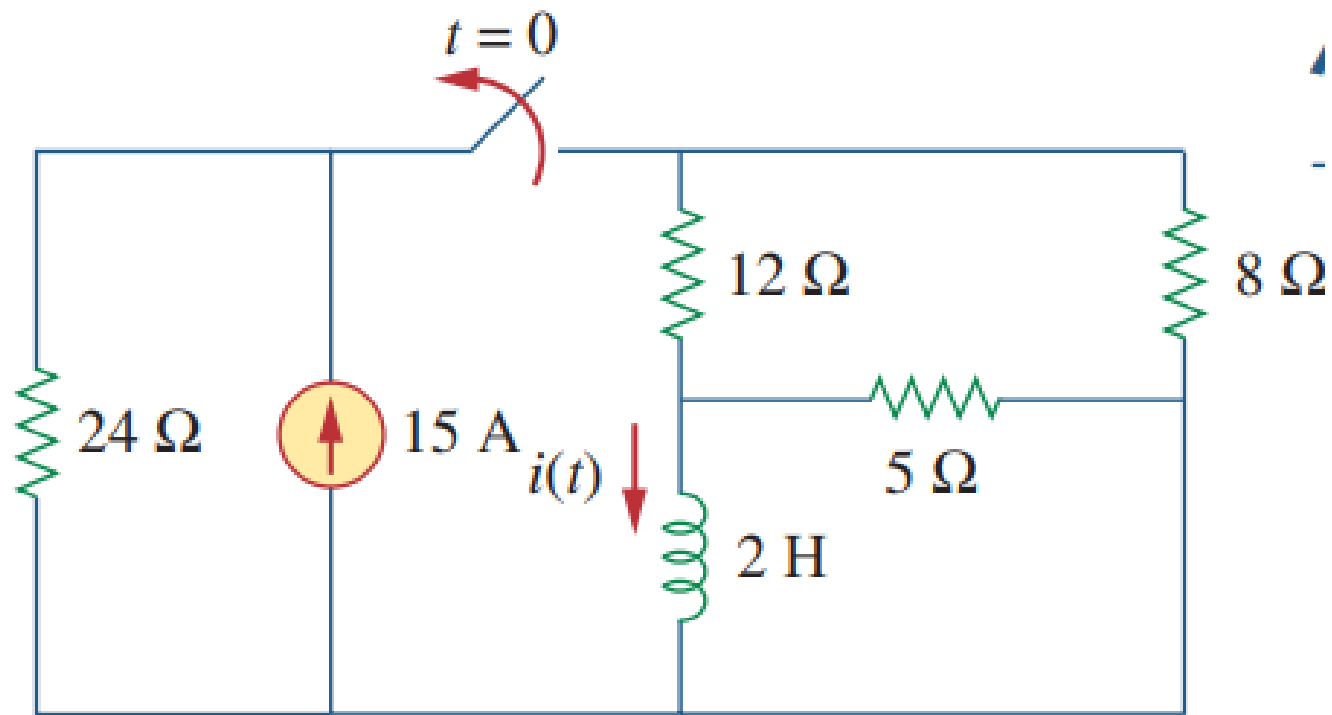

Answer: $5e^{-2t} \text{ A}, t > 0.$

The Source-Free RL Circuit

$$R_{eq} = 6 \parallel 3 = 2 \text{ ohm}$$

$$\tau = \frac{L}{R} = \frac{2}{2} = 1 \text{ sec}$$

$$i(t)_{t=0} = \frac{10}{2 + 3} = 2 \text{ A}$$

$$i(t) = 2e^{-t} \text{ A}$$

