

Electrical Circuit (1)

Discharge RC and RL (week13 class1)

Dr. Akram Al-Mahrouk

Philadelphia University

Chapter 7 First-Order Circuits 253


7.1	Introduction	254
7.2	The Source-Free RC Circuit	254
7.3	The Source-Free RL Circuit	259
7.4	Singularity Functions	265
7.5	Step Response of an RC Circuit	273
7.6	Step Response of an RL Circuit	280
7.7	†First-Order Op Amp Circuits	284
7.8	Transient Analysis with <i>PSpice</i>	289
7.9	†Applications	293
	7.9.1 Delay Circuits	
	7.9.2 Photoflash Unit	
	7.9.3 Relay Circuits	
	7.9.4 Automobile Ignition Circuit	
7.10	Summary	299
	Review Questions	300
	Problems	301
	Comprehensive Problems	311

Step Response of an RC Circuit

The **step response** of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.

$$\text{Complete response} = \underset{\text{stored energy}}{\text{natural response}} + \underset{\text{independent source}}{\text{forced response}}$$
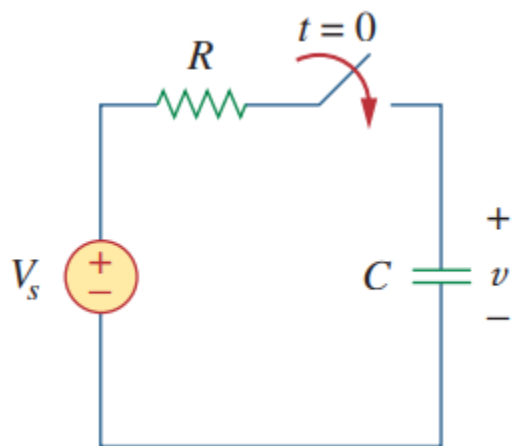
$$\text{Complete response} = \underset{\text{temporary part}}{\text{transient response}} + \underset{\text{permanent part}}{\text{steady-state response}}$$



The **transient response** is the circuit's temporary response that will die out with time.

The **steady-state response** is the behavior of the circuit a long time after an external excitation is applied.

Step Response of an RC Circuit

1. The initial capacitor voltage $v(0)$.
2. The final capacitor voltage $v(\infty)$.
3. The time constant τ .

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$

Step Response of an RC Circuit


$$v(\infty) = 30 \text{ V}$$

$$v(0) = 24 \frac{5k}{3k + 5k} = 15 \text{ V}$$

$$R_{eq} = 4 \text{ ohm}$$

$$\tau = RC = 0.5 * 4 = 2$$
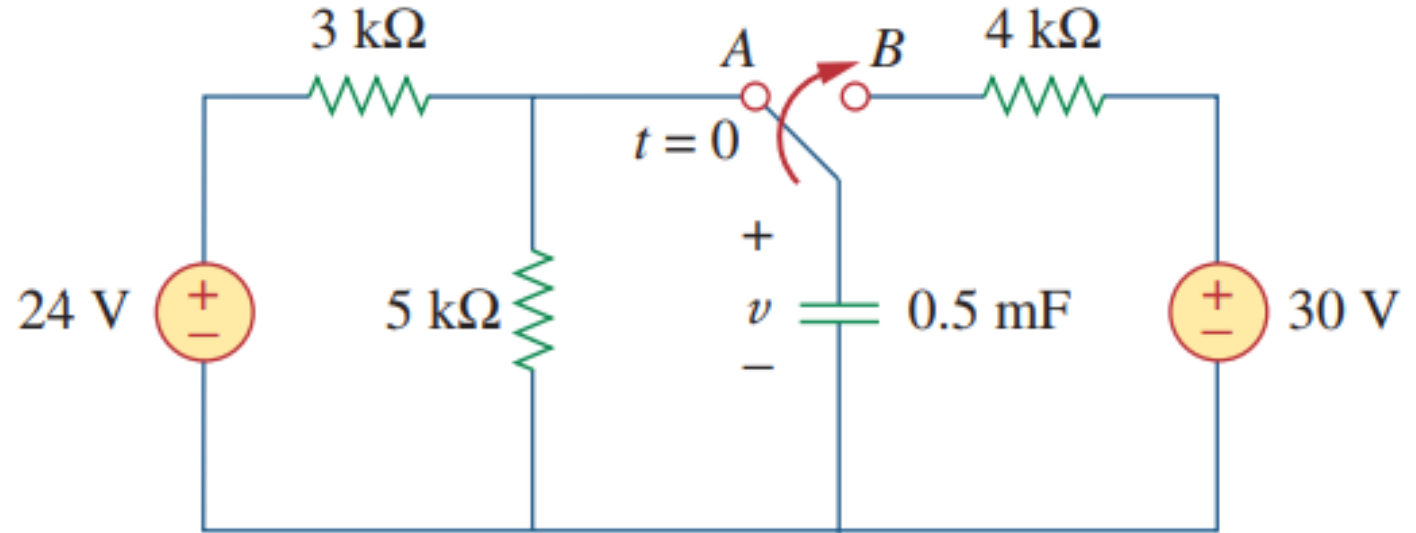
$$v(t) = 30 + [15 - 30]e^{\frac{-t}{2}} \text{ V}$$



$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{\frac{-t}{\tau}} \text{ V}$$

Step Response of an RC Circuit

Find $v(t)$ for $t > 0$ in the circuit of Fig. 7.44. Assume the switch has been open for a long time and is closed at $t = 0$. Calculate $v(t)$ at $t = 0.5$.


$$v(\infty) = \frac{v - 15}{2} + \frac{v + 7.5}{6} = 0 \rightarrow v(\infty) = 9.375 \text{ V}$$

$$v(0) = 15 \text{ V}$$

$$R_{eq} = 2 || 6 = \frac{3}{2} \text{ ohm}$$

$$\tau = RC = \frac{3}{2} * \frac{1}{3} = 0.5 \text{ sec}$$
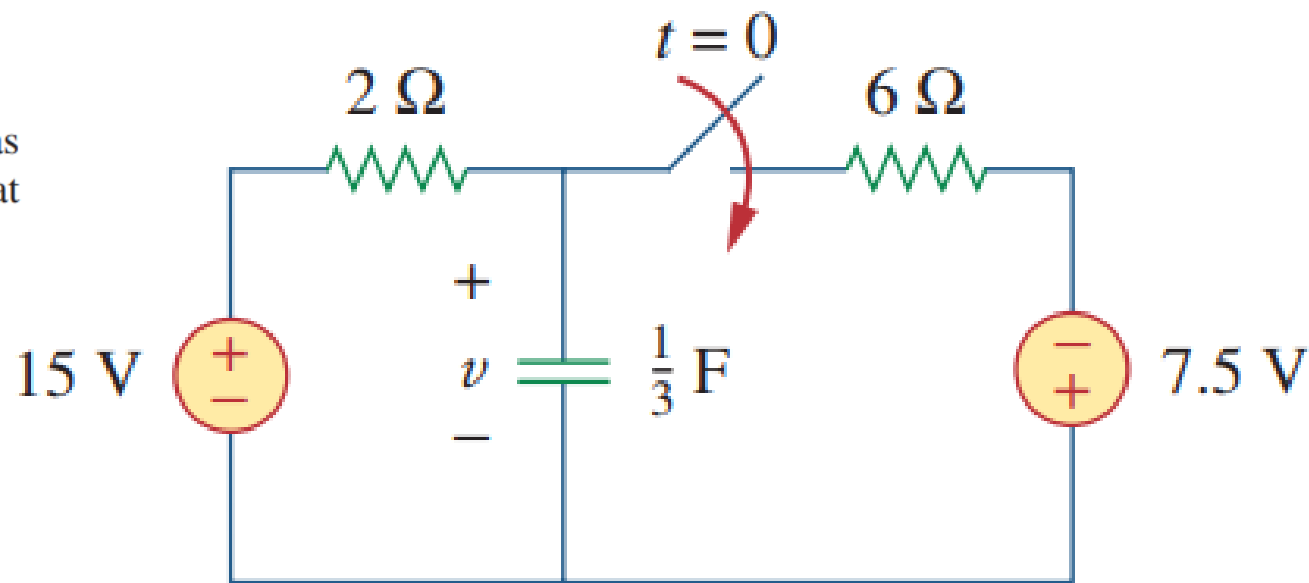
$$v(t) = 9.375 + [15 - 9.375]e^{-2t} \text{ V}$$



Answer: $(9.375 + 5.625e^{-2t})$ V for all $t > 0$, 7.63 V.

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{\frac{-t}{\tau}} \text{ V}$$

Step Response of an RC Circuit


$$v(\infty) = 30 \frac{20}{10 + 20} = 20V$$

$$v(0) = 10V$$

$$R_{eq} = 20 || 10 = 6.666 \text{ ohm}$$

$$\tau = RC = 6.666 * \frac{1}{4} = 1.66 \text{ sec}$$
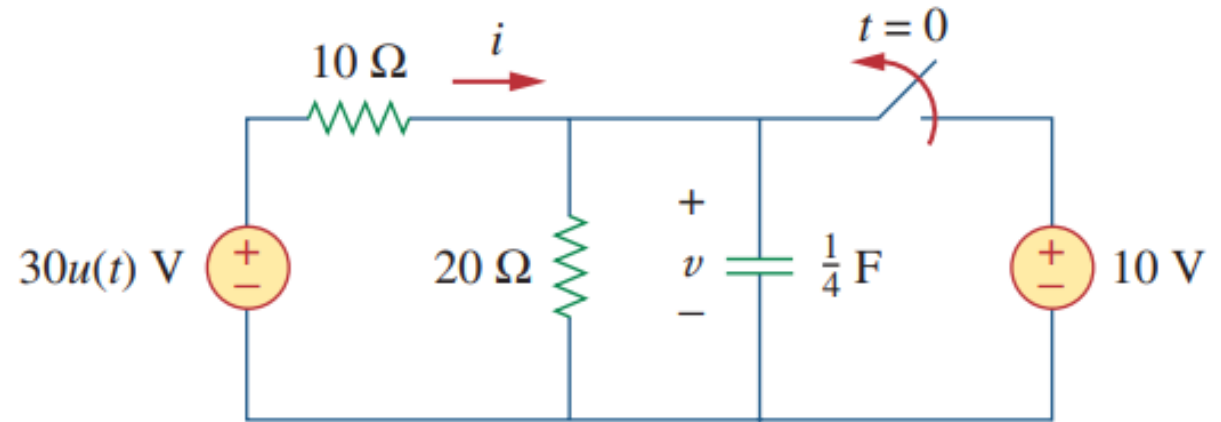
$$v(t) = 20 + [10 - 20]e^{\frac{-t}{1.66}} V$$



$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{\frac{-t}{\tau}} V$$

Step Response of an RL Circuit

1. The initial inductor current $i(0)$ at $t = 0$.
2. The final inductor current $i(\infty)$.
3. The time constant τ .

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

Step Response of an RL Circuit


$$i(\infty) = \frac{10}{2 + 3} = 2A$$

$$i(0) = \frac{10}{2} = 5A$$

$$R_{eq} = 2 + 3 = 5 \text{ ohm}$$

$$\tau = \frac{L}{R} = \frac{\frac{1}{3}}{5} = \frac{1}{15} \text{ sec}$$

$$i(t) = 2 + [5 - 2]e^{-15t} A$$

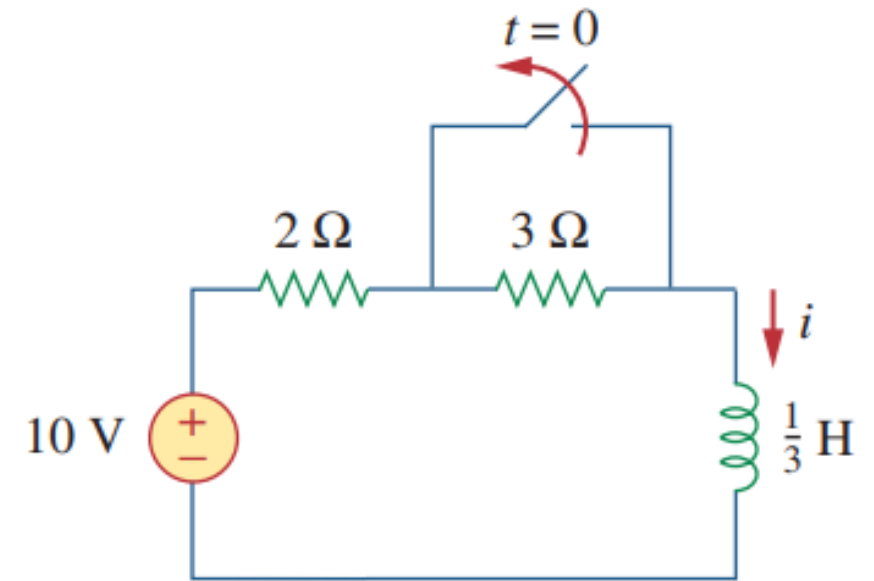

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{\frac{-t}{\tau}} A$$

Step Response of an RL Circuit

$$i(t)_{t < 0} = 0A$$

$$i(0)_{0 < t < 4} = 0A$$

$$i(\infty)_{0 < t < 4} = \frac{40}{10} = 4A$$

$$R_{eq(0 < t < 4)} = 4 + 6 = 10 \text{ ohm}$$

$$\tau_{(0 < t < 4)} = \frac{L}{R} = \frac{5}{10} = 0.5 \text{ sec}$$

$$i(t)_{0 < t < 4} = 4 + (0 - 4) e^{-2t} A$$

$$i(0)_{4 < t} = 4 + (0 - 4) e^{-2t} A = 4A$$

$$i(\infty)_{4 < t} \rightarrow \frac{v - 40}{4} + \frac{v - 10}{2} + \frac{v}{6} = 0$$


$$v = 16.36V$$

$$i(\infty)_{4 < t} = \frac{16.36}{6} = 2.72A$$

$$R_{eq(4 < t)} = 4 || 2 + 6 = \frac{22}{3} \text{ ohm}$$

$$\tau_{(4 < t)} = \frac{L}{R} = \frac{5}{\frac{22}{3}} = \frac{15}{22} = 0.681 \text{ sec}$$
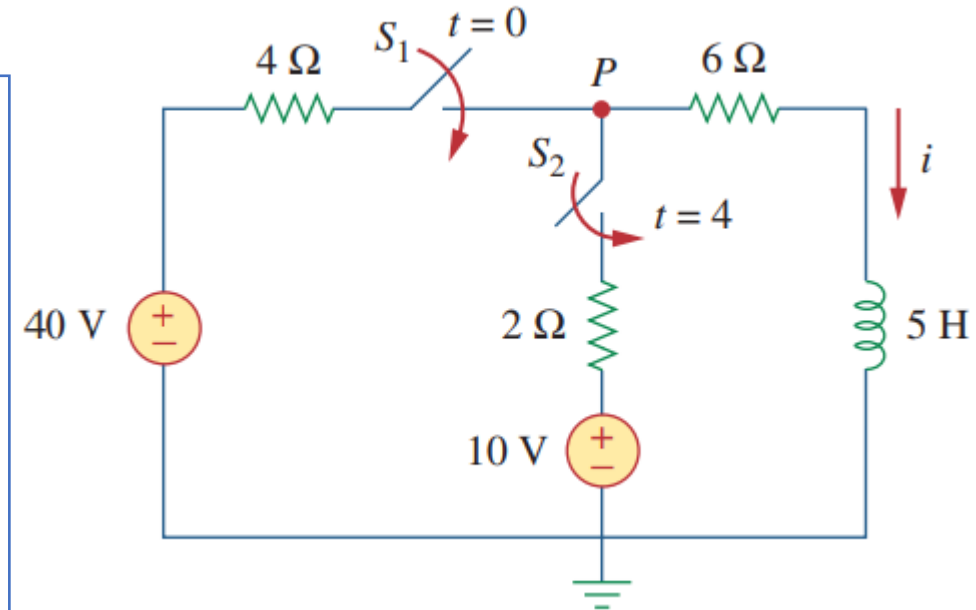
$$i(t)_{4 < t} = 2.72 + (4 - 2.72) e^{\frac{-t}{0.681}} A$$



$$i(t) = \begin{cases} t < 0 & 0 \\ 0 < t < 4 & 4 + (0 - 4) e^{-2t} \\ 4 < t & 2.72 + (4 - 2.72) e^{\frac{-t}{0.681}} A \end{cases}$$

