



جامعة الطفيلة التقنية
Tafila Technical University



3416

Wind Energy Systems



Chapter 3: Power Electronics

Dr. Abdullah Awad


Email:

abdullah.awad@ttu.edu.jo


Ideal Switch

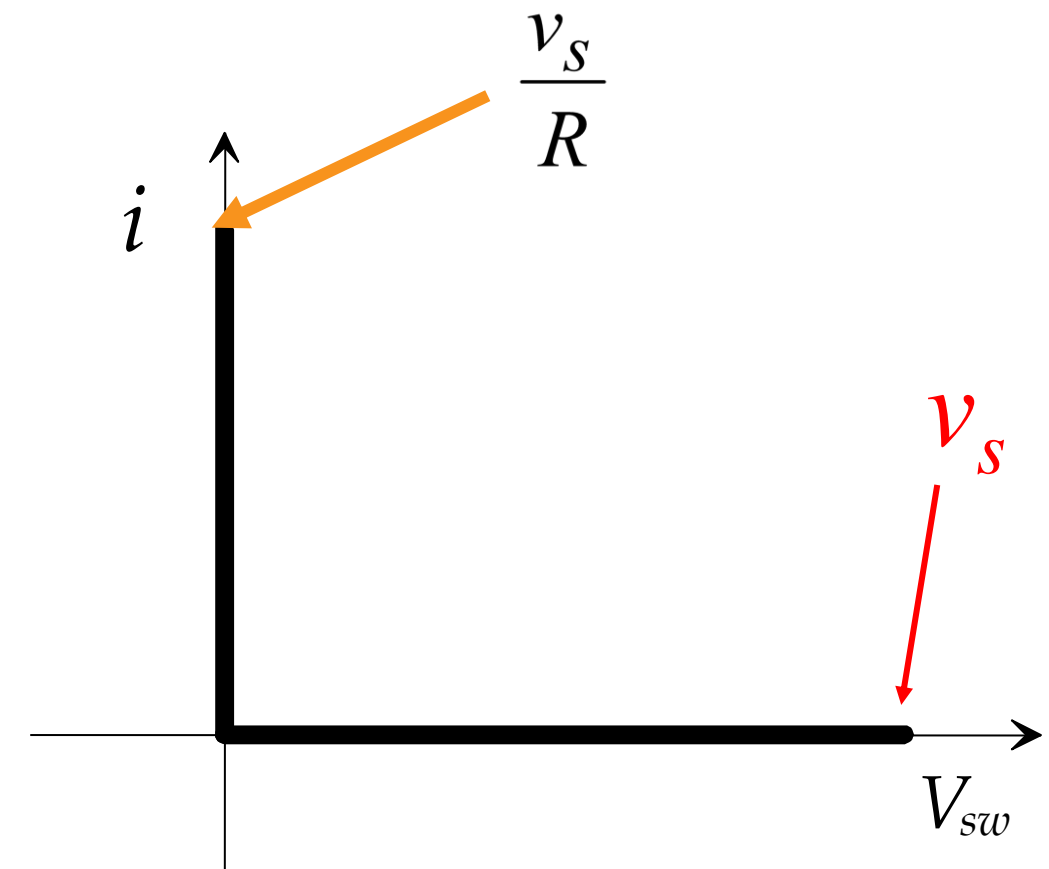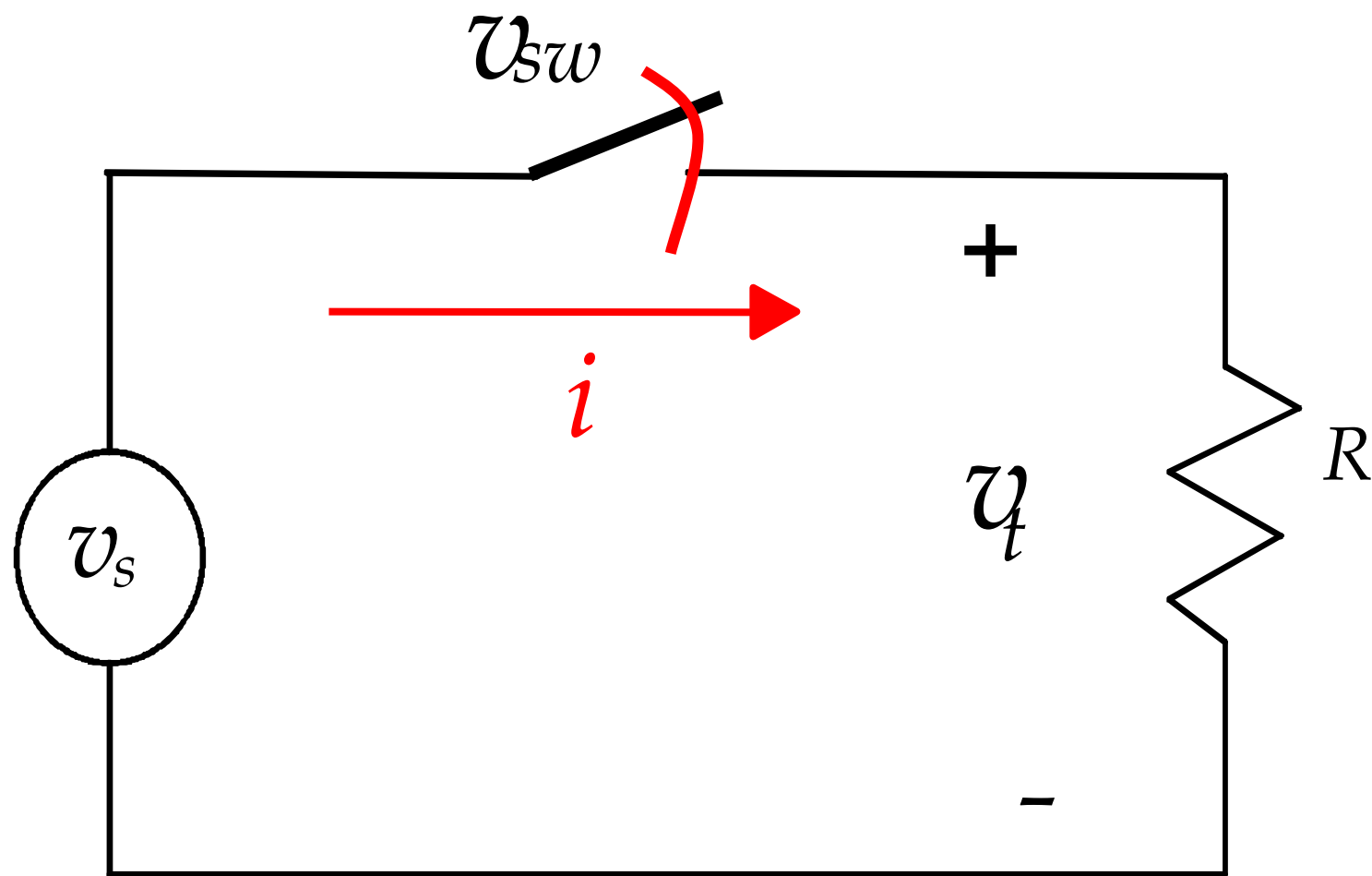

Power Control

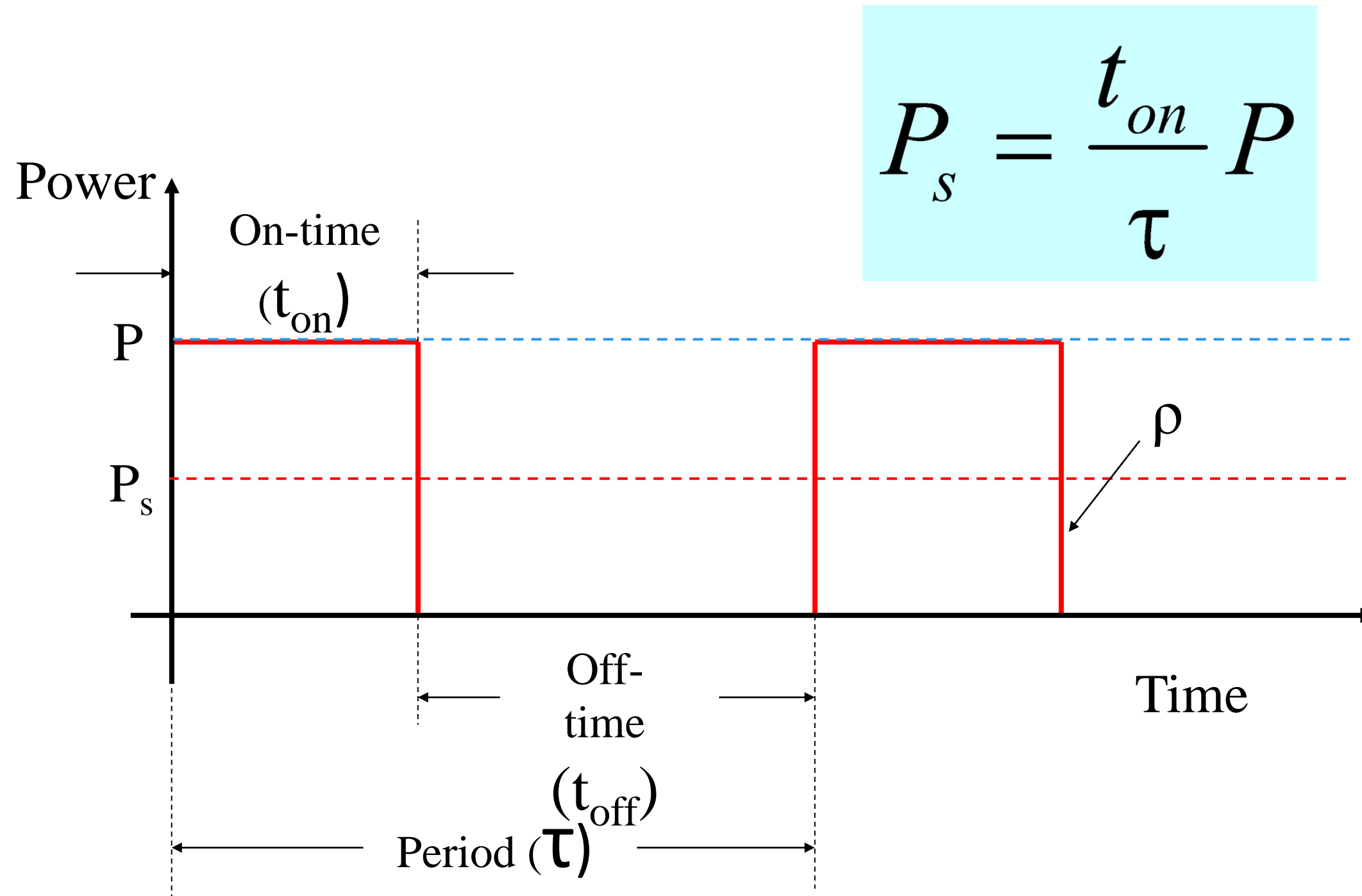

Energy Consumption (E)

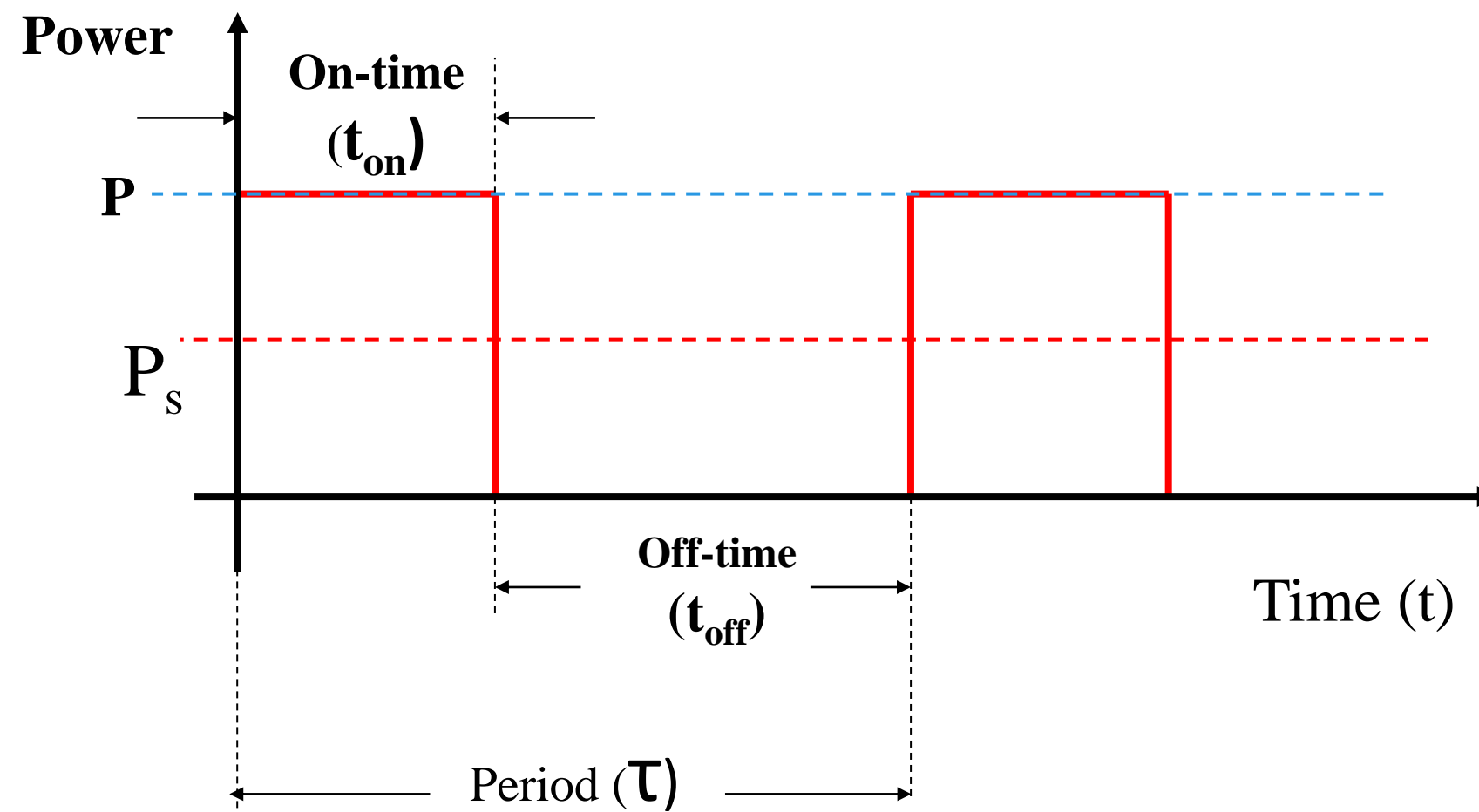


Duty Ratio (K)

$$E \equiv P t$$

$$E_s = P_s t = \frac{t_{on}}{\tau} P t$$




Types of Converters

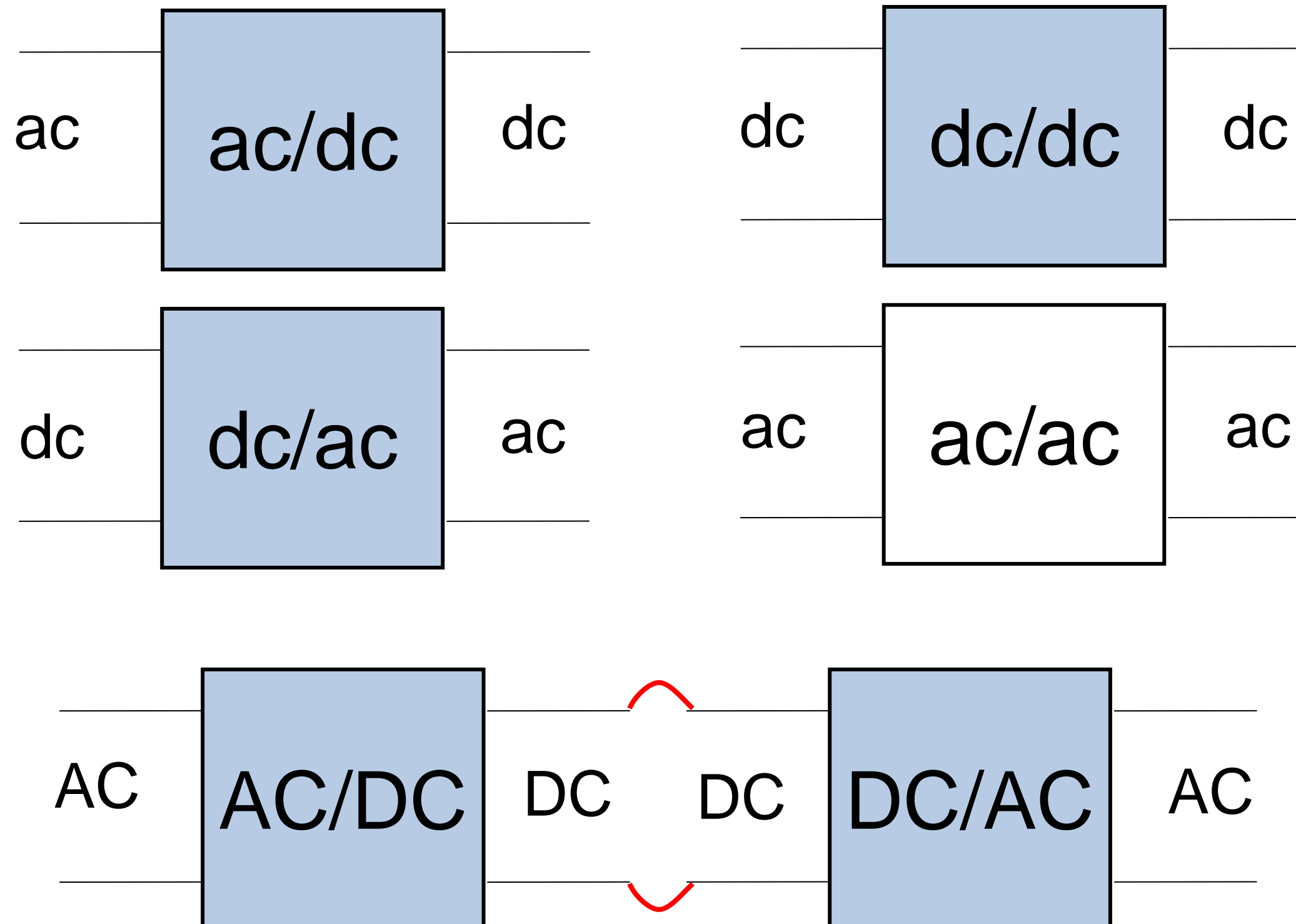




AC/DC Converters

Single-Phase, Half-Wave

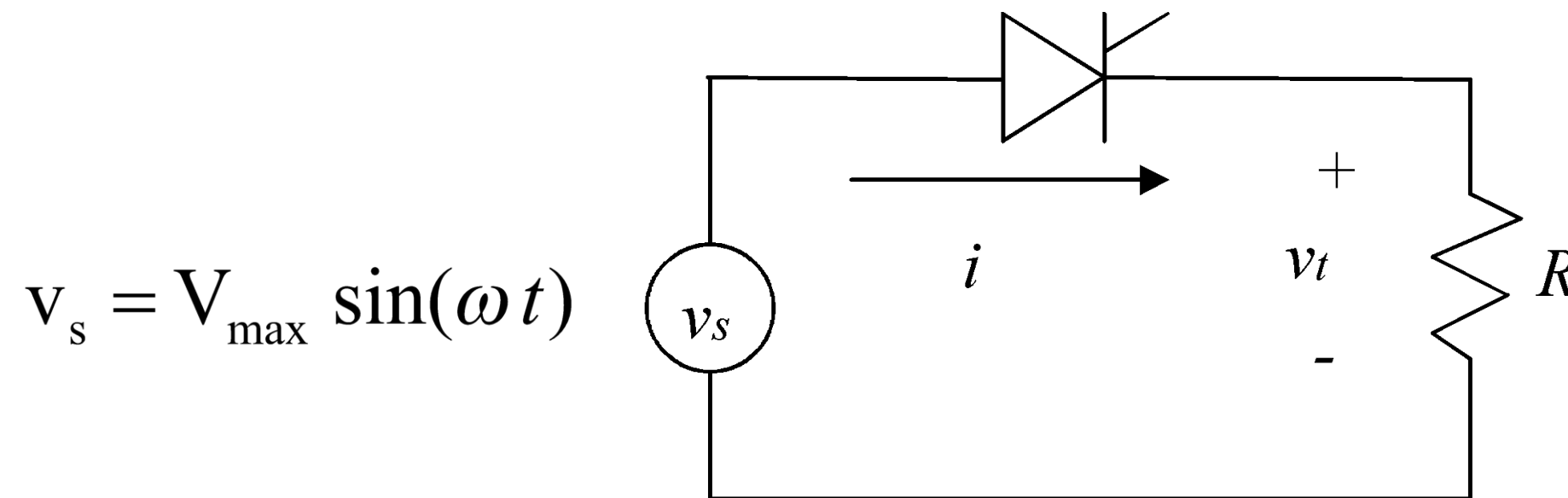



$$i = \frac{v_s}{R} \text{ (only when SCR is closed)}$$

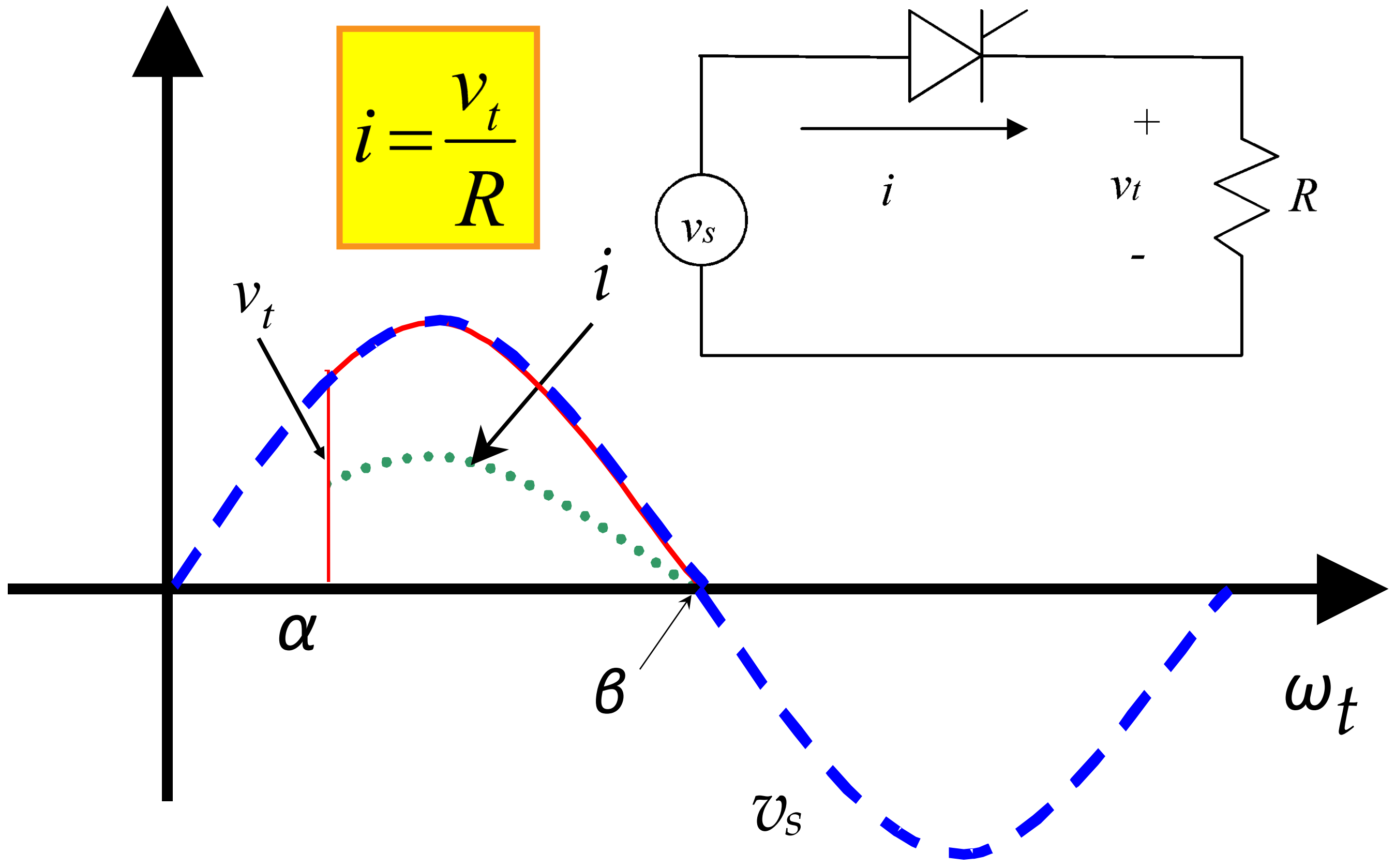
$$v_t = i R = v_s \text{ (only when SCR is closed)}$$




Average Voltage Across the Load

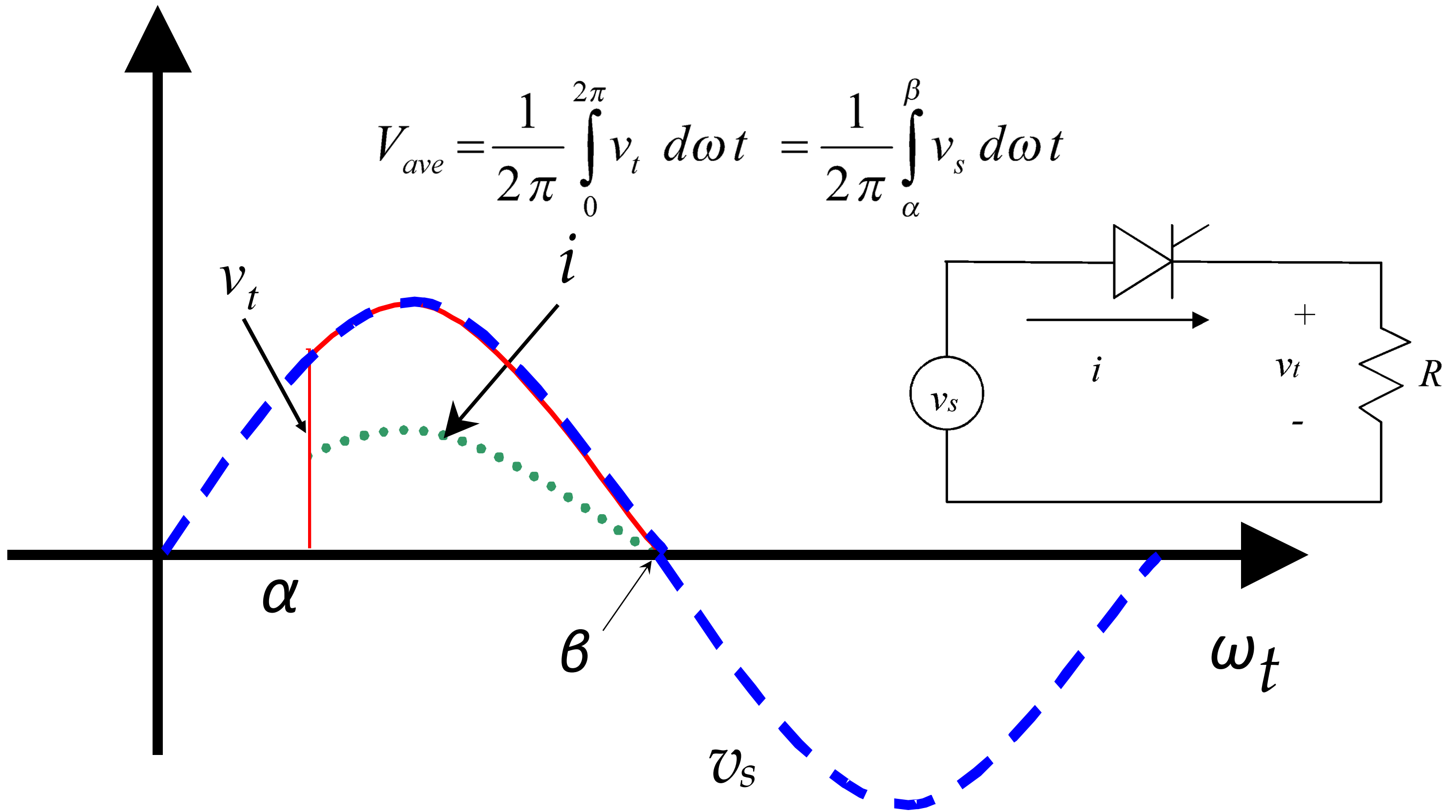

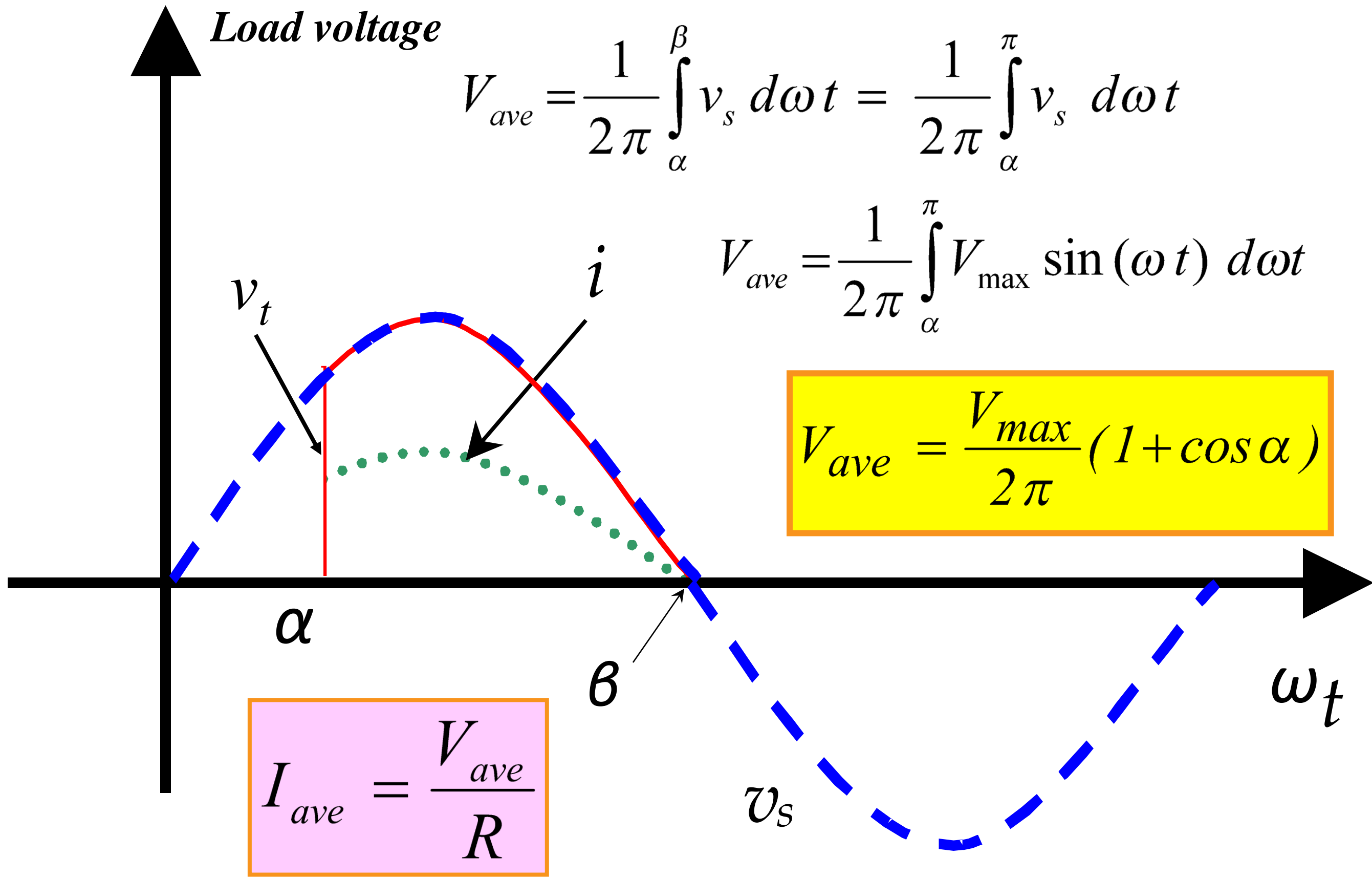

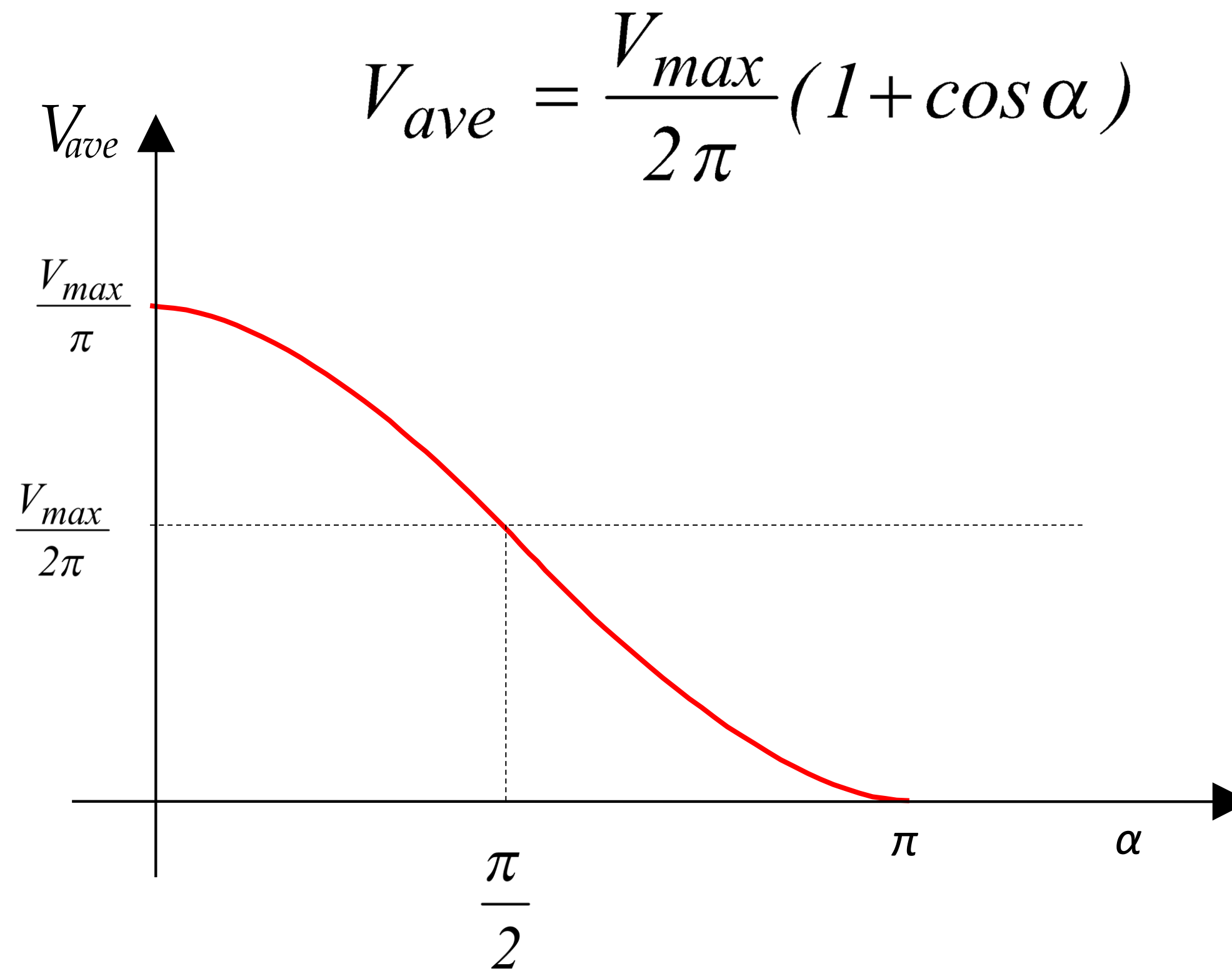

RMS of load voltage

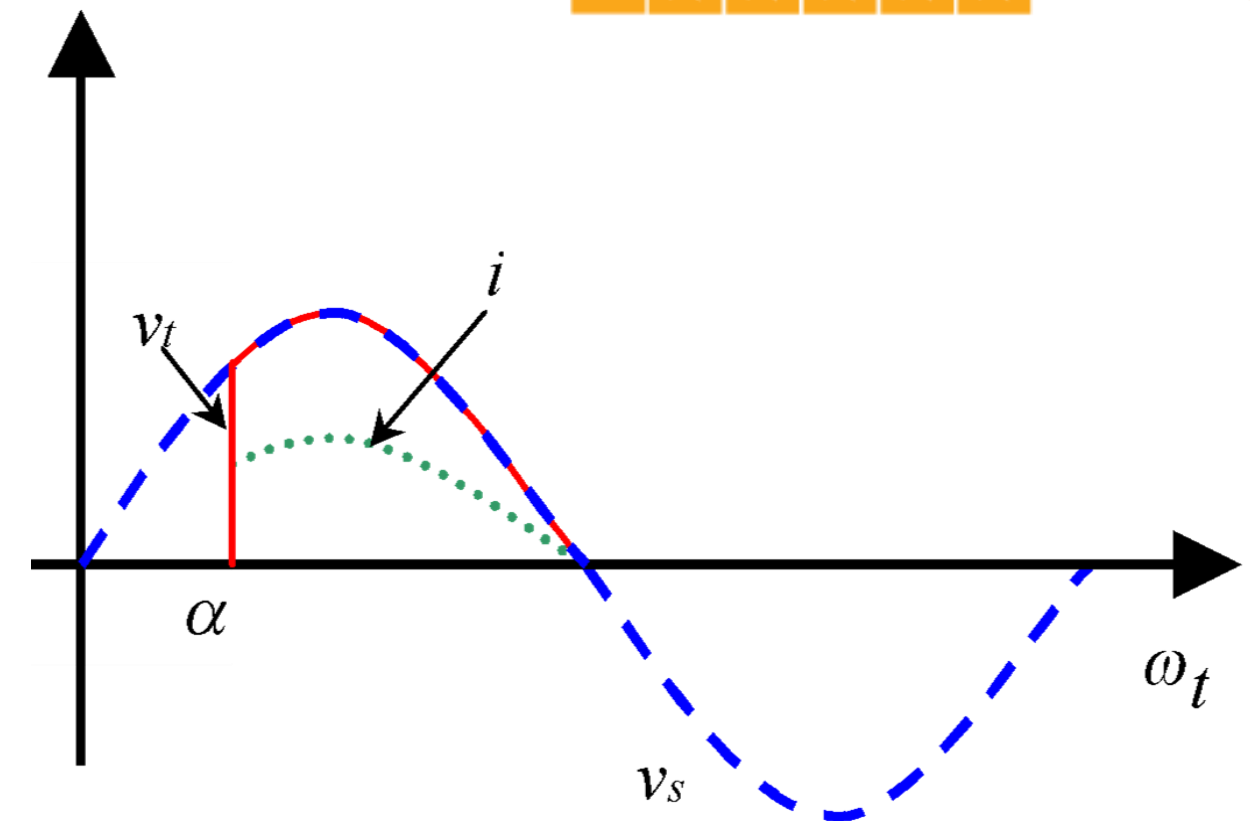


$$V_{rms} = \sqrt{\frac{V_{max}^2}{2\pi} \int_{\alpha}^{\pi} [\sin(\omega t)]^2 d\omega t} = \sqrt{\frac{V_{max}^2}{4\pi} \int_{\alpha}^{\pi} [1 - \cos(2\omega t)] d\omega t}$$

$$V_{rms} = \frac{V_{max}}{2} \sqrt{\left[1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}\right]}$$

$$V_{max} = \sqrt{2} V_{s_{rms}}$$

RMS of Supply Voltage

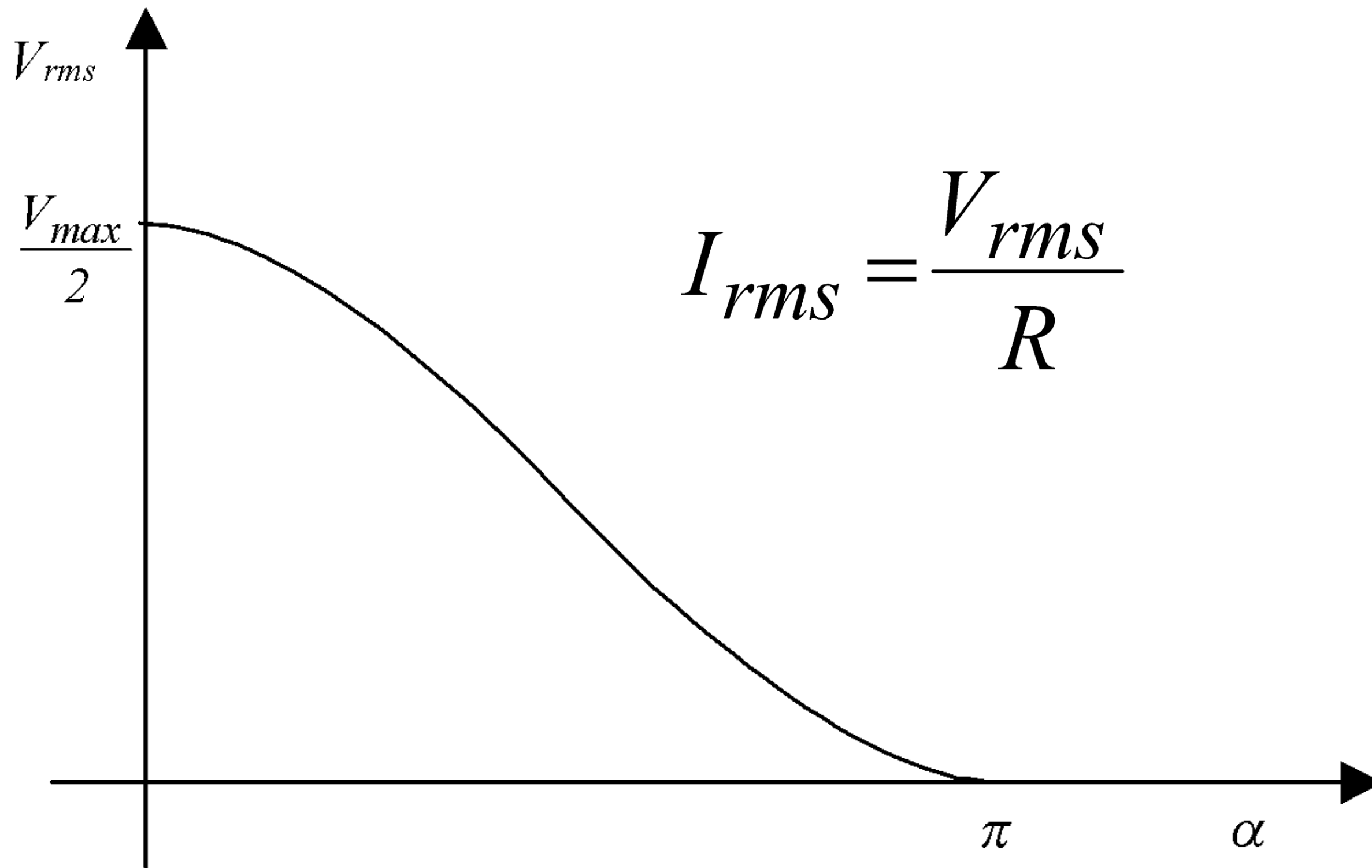

$$I_{rms} = \frac{V_{rms}}{R}$$




Electric Power




$$P = \frac{V_{rms}^2}{R} = I_{rms}^2 R$$

$$P = \frac{V_{max}^2}{8\pi R} [2(\pi - \alpha) + \sin(2\alpha)]$$

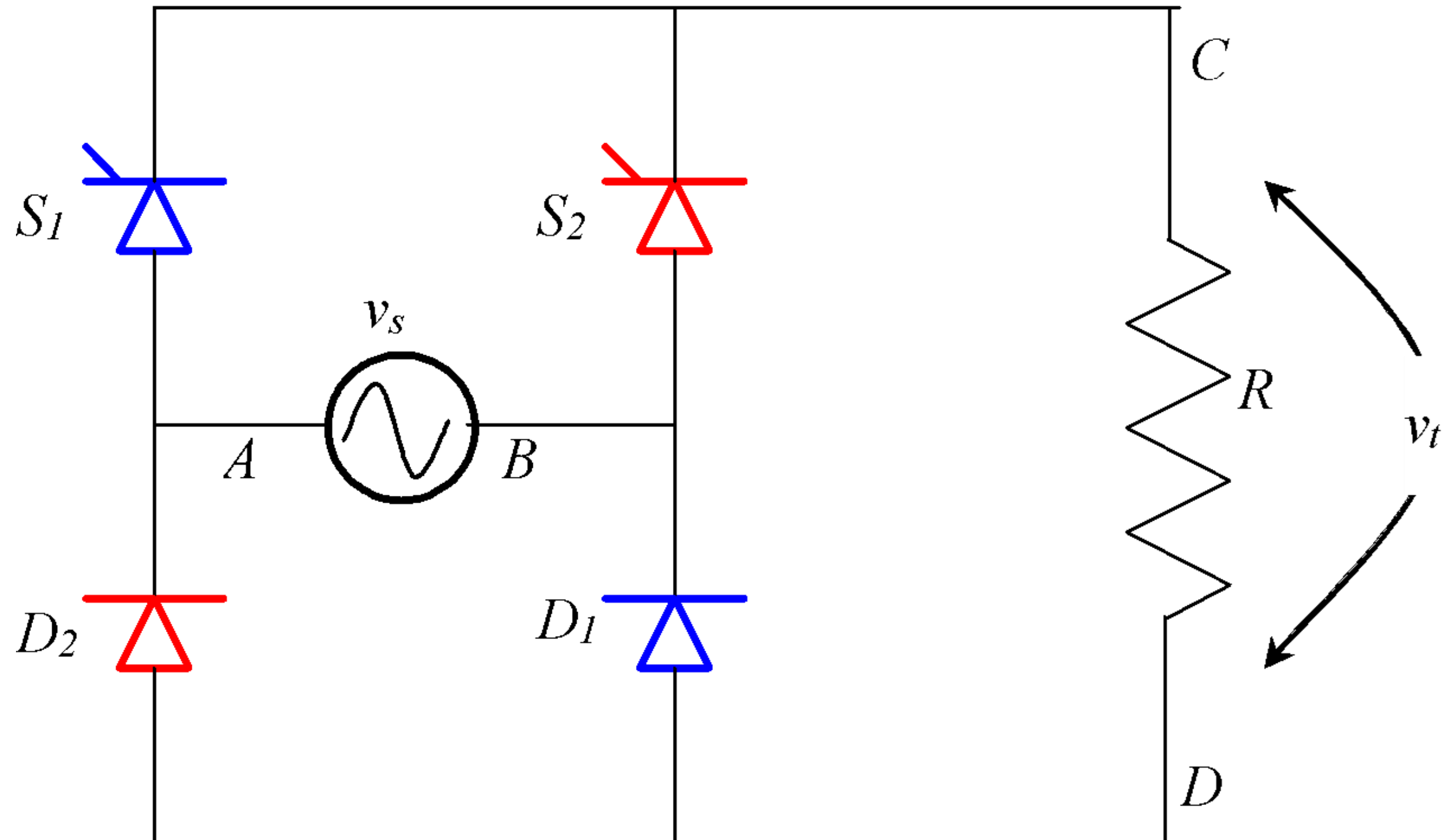
Single-Phase, Full-Wave, AC-to-DC 2-SCRs and 2 Diodes




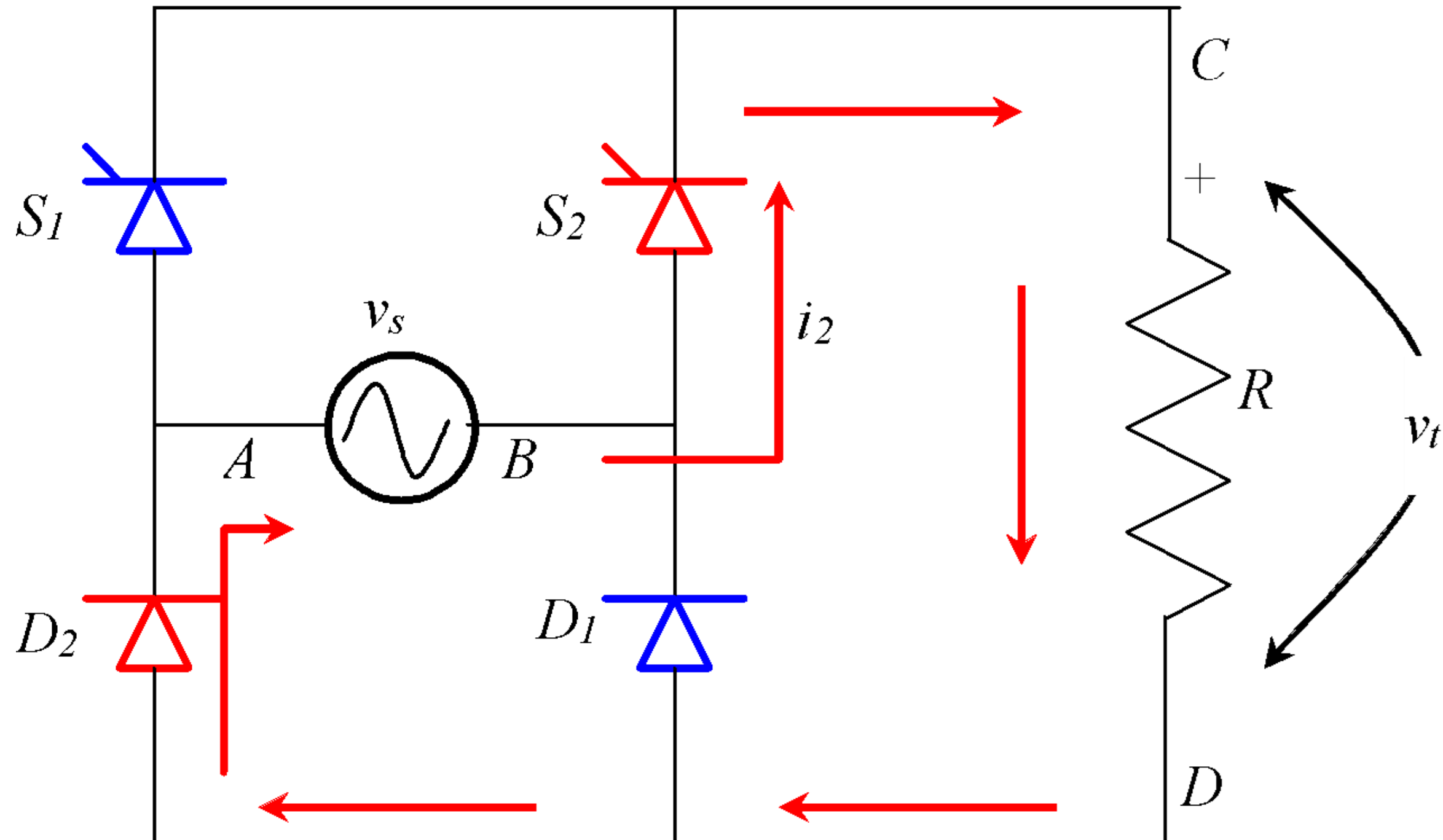
Single-Phase, Full-Wave, AC-to-DC 2-SCRs and 2 Diodes



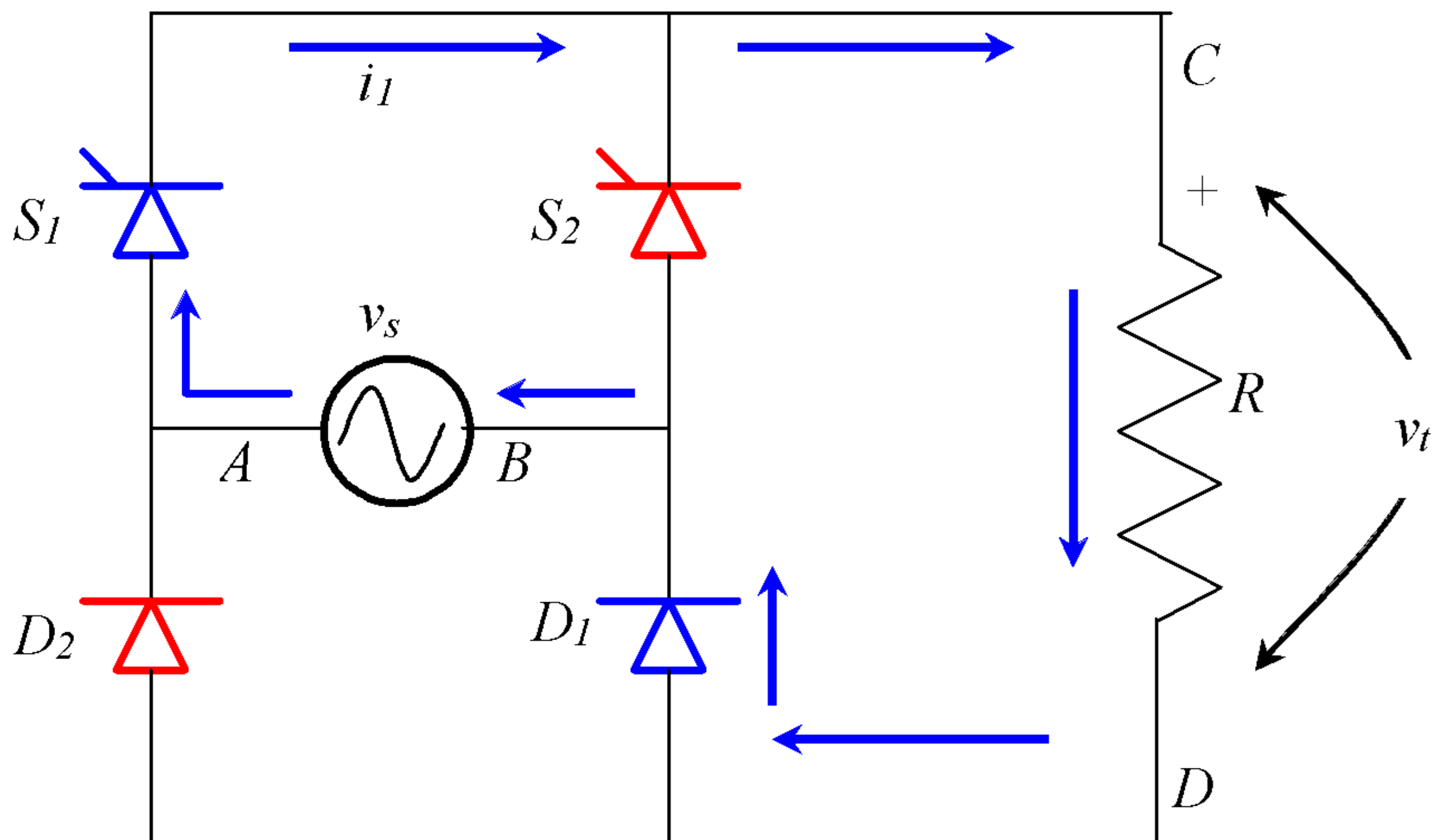Single-Phase, Full-Wave, AC-to-DC 2-SCRs and 2 Diodes



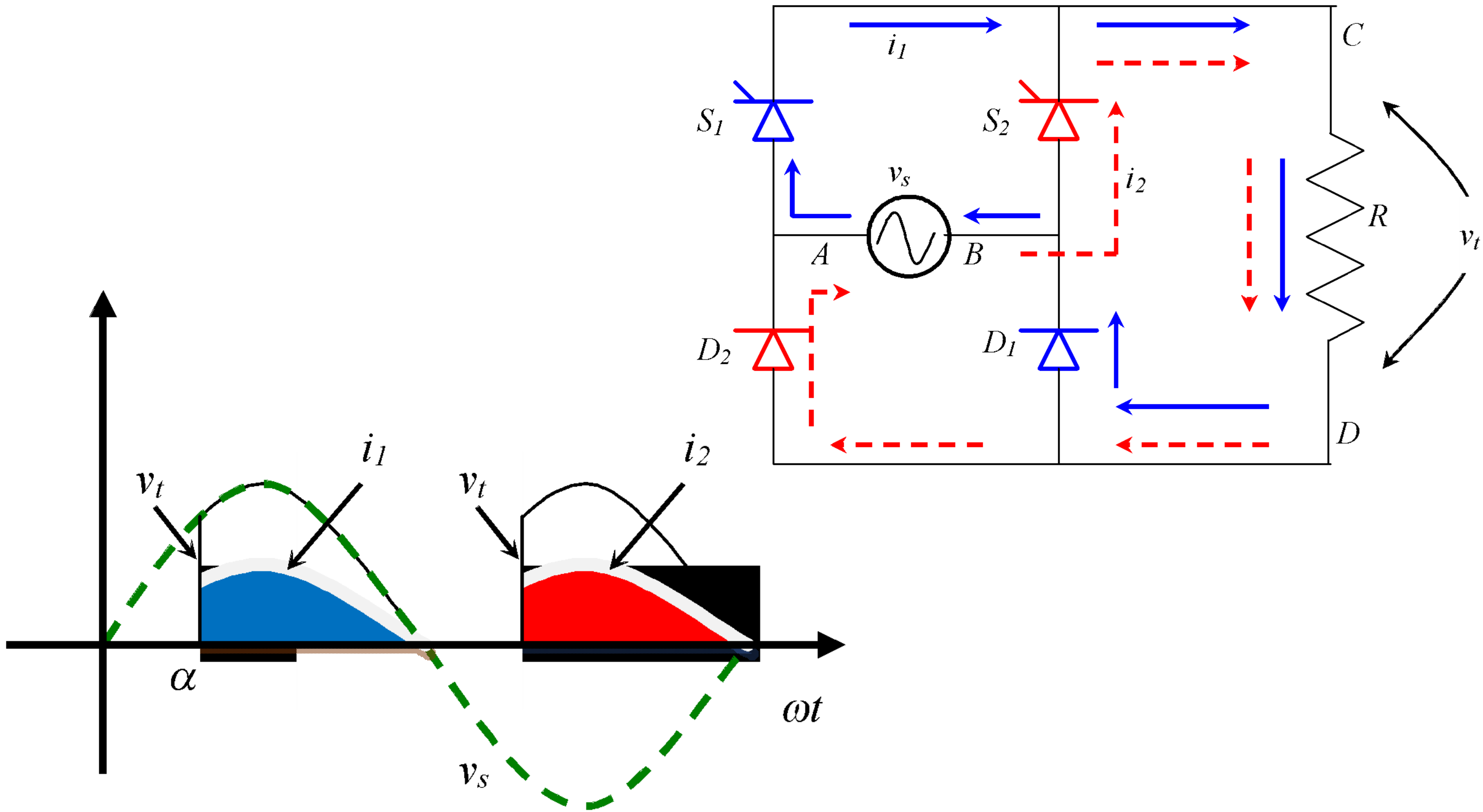

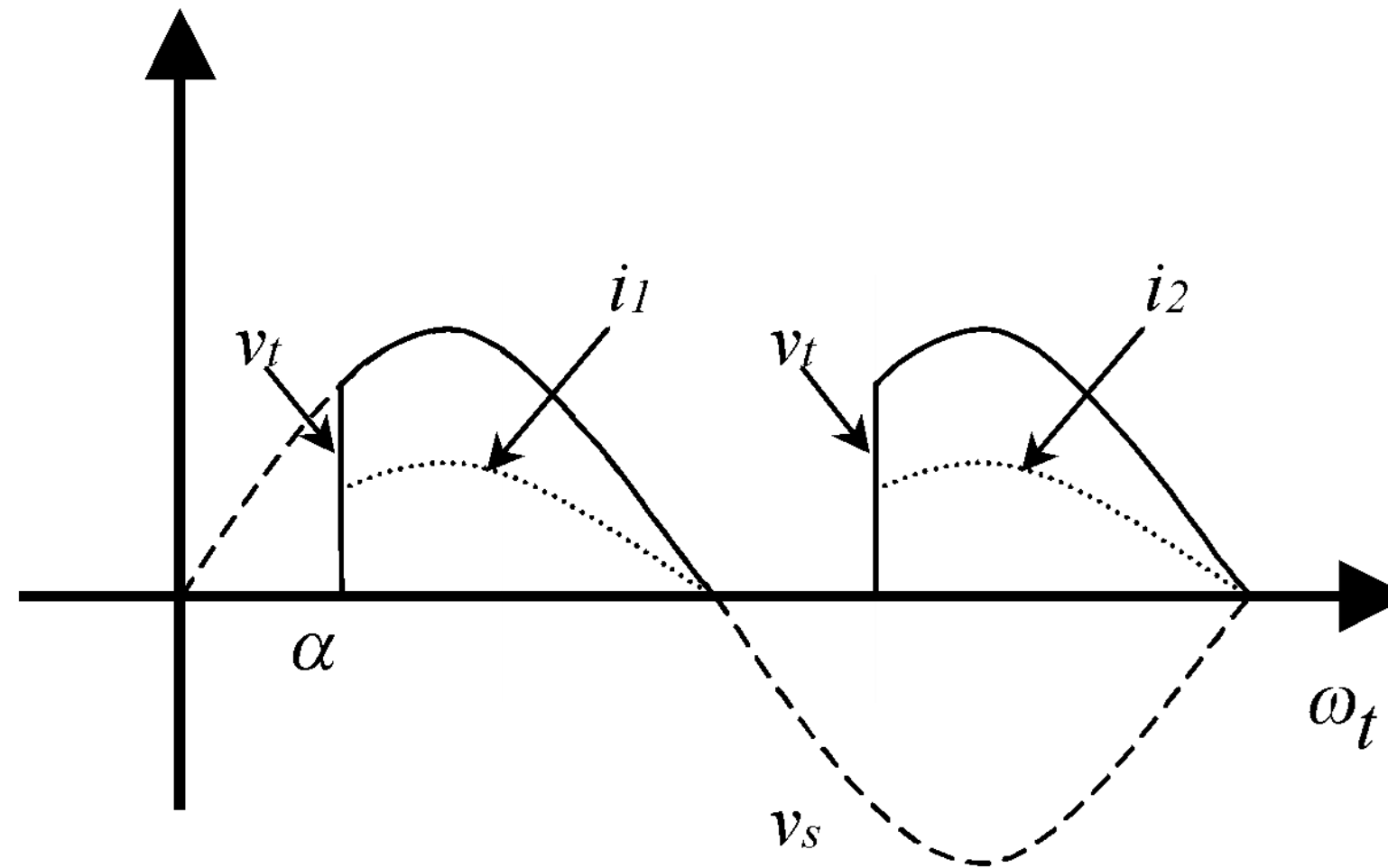

$$V_{ave} = \frac{1}{\pi} \int_{\alpha}^{\pi} v_t d\omega t = \frac{1}{\pi} \int_{\alpha}^{\pi} V_{max} \sin(\omega t) d\omega t = \frac{V_{max}}{\pi} (1 + \cos \alpha)$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v(t)^2 d\omega t} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} [V_{max} \sin(\omega t)]^2 d\omega t}$$

$$V_{rms} = \sqrt{\frac{V_{max}^2}{\pi} \int_{\alpha}^{\pi} \sin(\omega t)^2 d\omega t} = \sqrt{\frac{V_{max}^2}{2\pi} \int_{\alpha}^{\pi} [1 - \cos(2\omega t)] d\omega t}$$


$$V_{rms} = \frac{V_{max}}{\sqrt{2}} \sqrt{\left[1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}\right]}$$

$$P = \frac{V_{rms}^2}{R} = \frac{V_{max}^2}{4\pi R} [2(\pi - \alpha) + \sin(2\alpha)]$$


Half Wave Versus Full Wave

	<i>Half Wave</i>	<i>Full Wave</i>
Average Voltage	$V_{ave} = \frac{V_{max}}{2\pi} (1 + \cos \alpha)$	$V_{ave} = \frac{V_{max}}{\pi} (1 + \cos \alpha)$
RMS Voltage	$V_{rms} = \frac{V_{max}}{2} \sqrt{\left[1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}\right]}$	$V_{rms} = \frac{V_{max}}{\sqrt{2}} \sqrt{\left[1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}\right]}$
Power	$P = \frac{V_{max}^2}{8\pi R} [2(\pi - \alpha) + \sin(2\alpha)]$	$P = \frac{V_{max}^2}{4\pi R} [2(\pi - \alpha) + \sin(2\alpha)]$

3-phase, AC/DC Transistor Converter

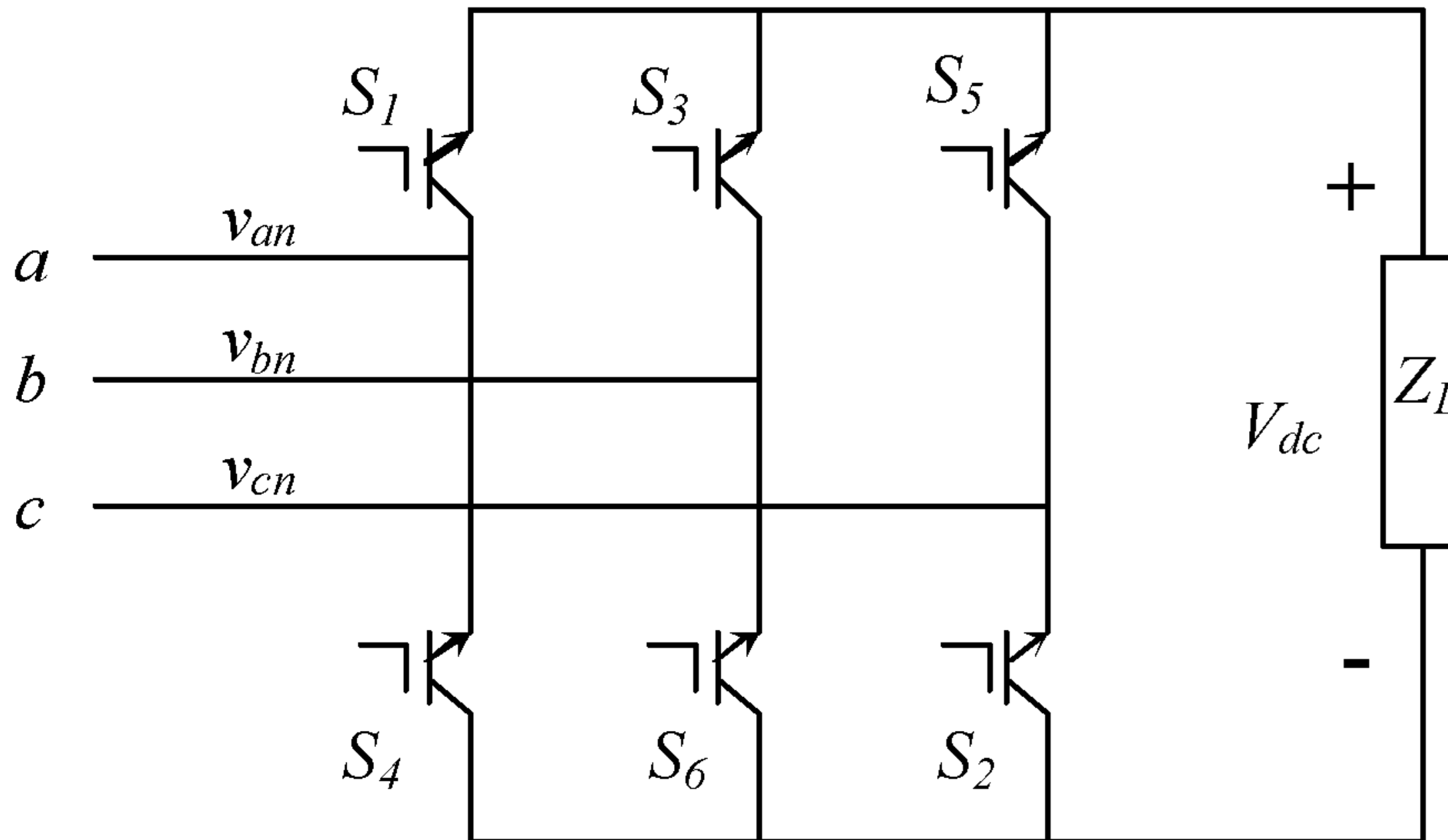


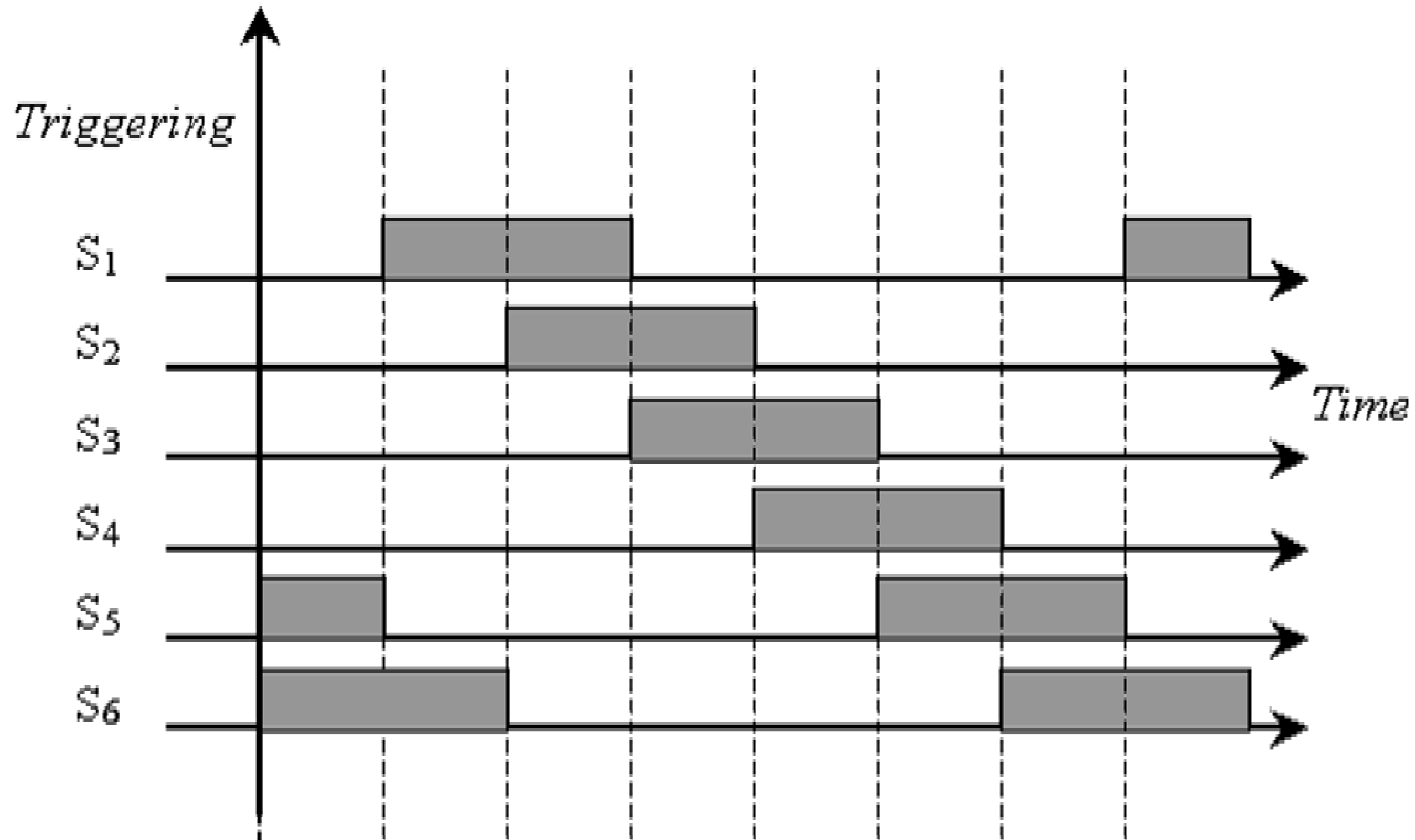3-phase, AC/DC Conversion: Switching Sequence



3-phase AC/DC SCR Converter



when $v_{ab} >$ all other voltages

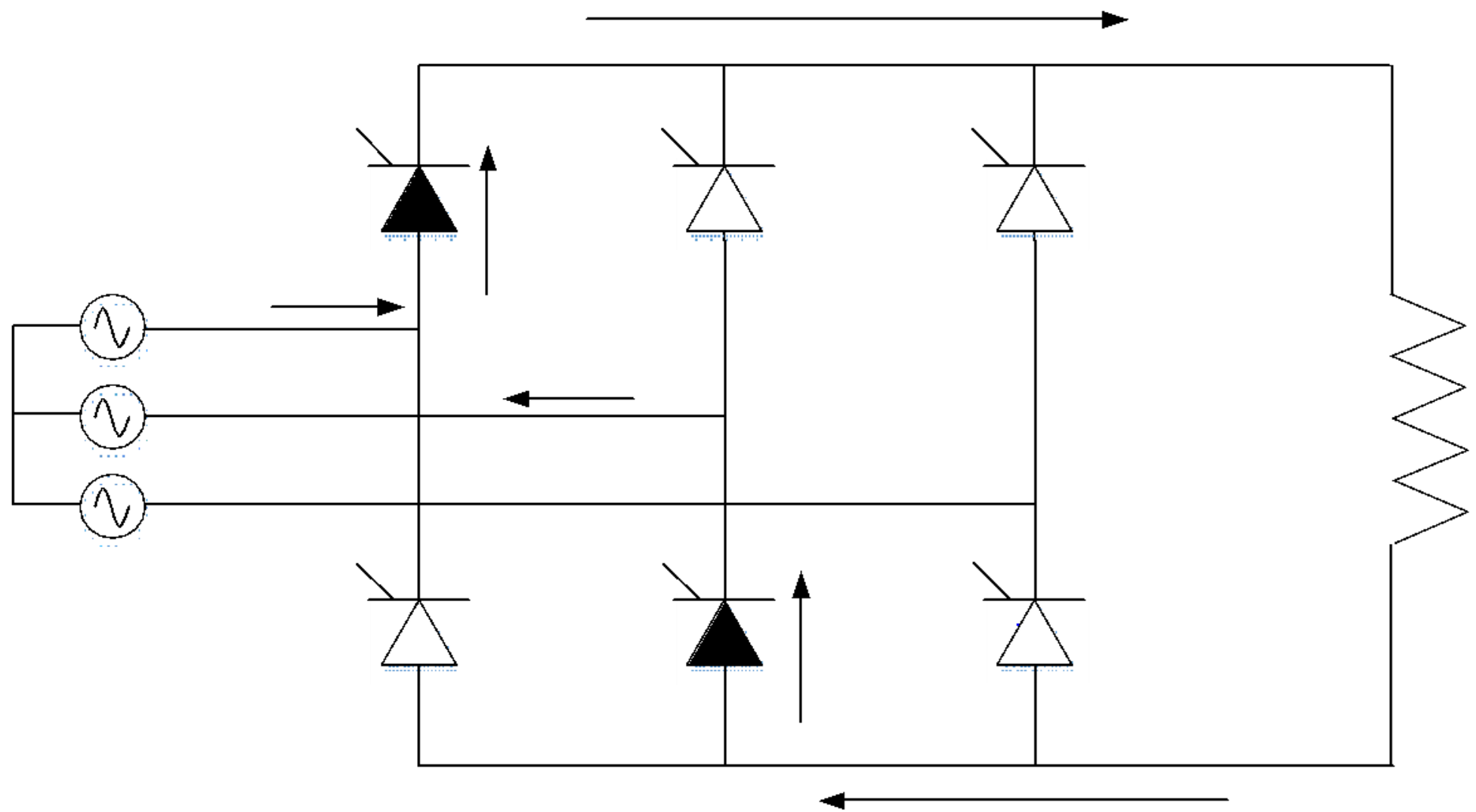

$$V_{ave} = 6 \left(\frac{1}{2\pi} \int_{\alpha_{ab}}^{\alpha_{ab}+60^\circ} v_{ab} d\omega t \right)$$

$$= 6 \left(\frac{1}{2\pi} \int_{\alpha_{ab}}^{\alpha_{ab}+60^\circ} \sqrt{3} V_{max} \sin \omega t d\omega t \right)$$
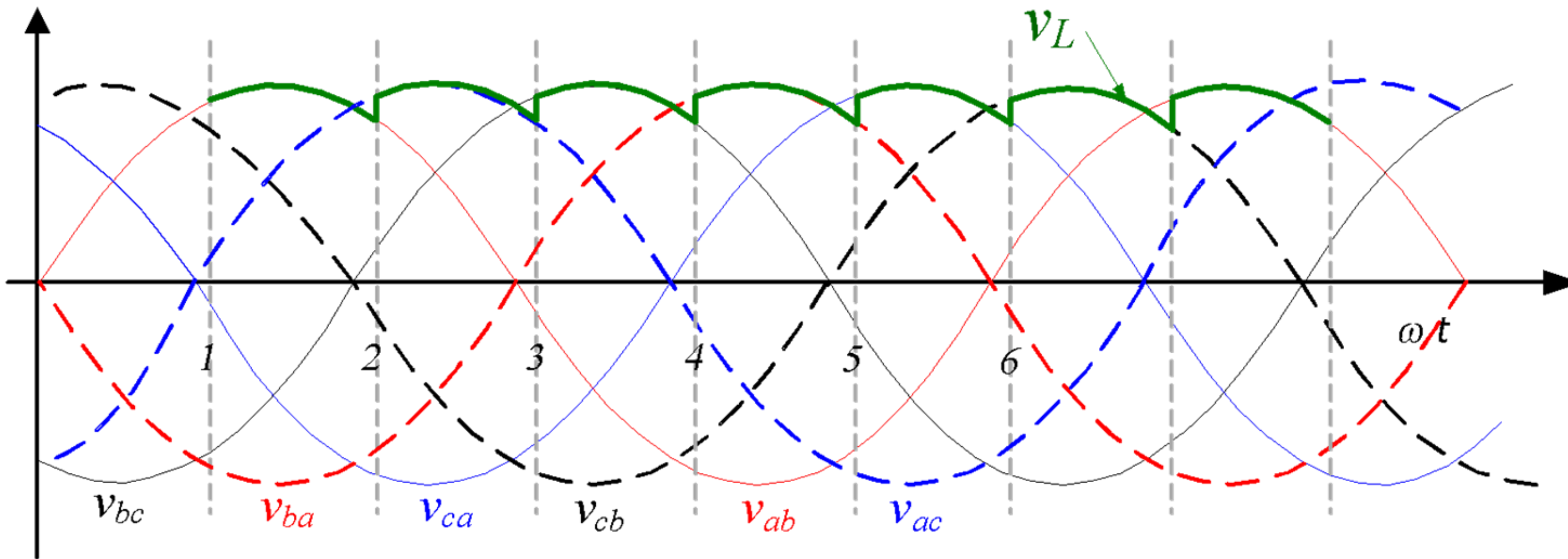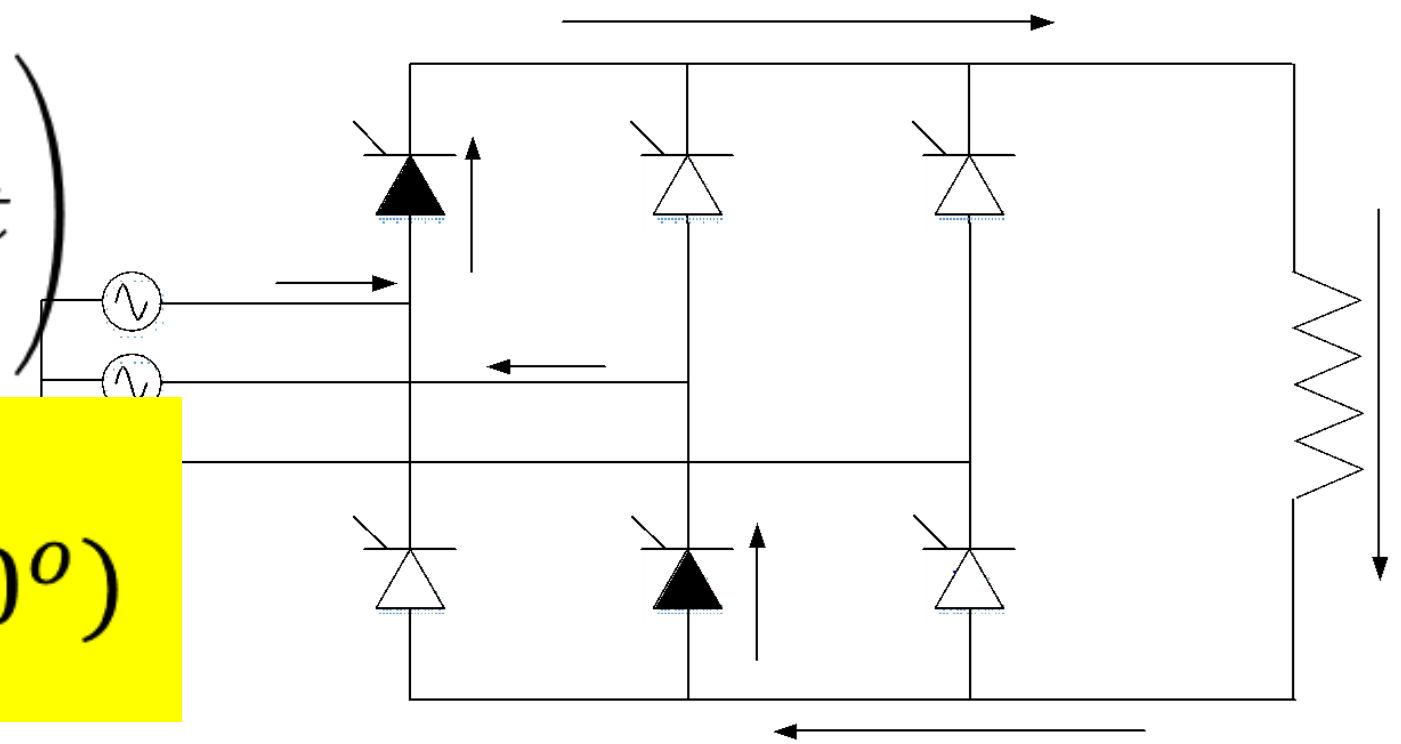
$$V_{ave} = \frac{3\sqrt{3} V_{max}}{\pi} \sin(\alpha_{ab} + 30^\circ)$$



$$V_{rms} = \sqrt{\frac{6}{2\pi} \int_{\alpha_{ab}}^{\alpha_{ab}+60^{\circ}} (\sqrt{3} V_{max} \sin \omega t)^2 d\omega t} = \frac{3 V_{max}}{\sqrt{2}} \sqrt{\frac{1}{3} - \frac{\sqrt{3}}{2\pi} \cos(2\alpha_{ab} + 60^{\circ})}$$



$$120^{\circ} \geq \alpha_{ab} \geq 60^{\circ}$$




DC/AC Converters





DC/AC Conversion


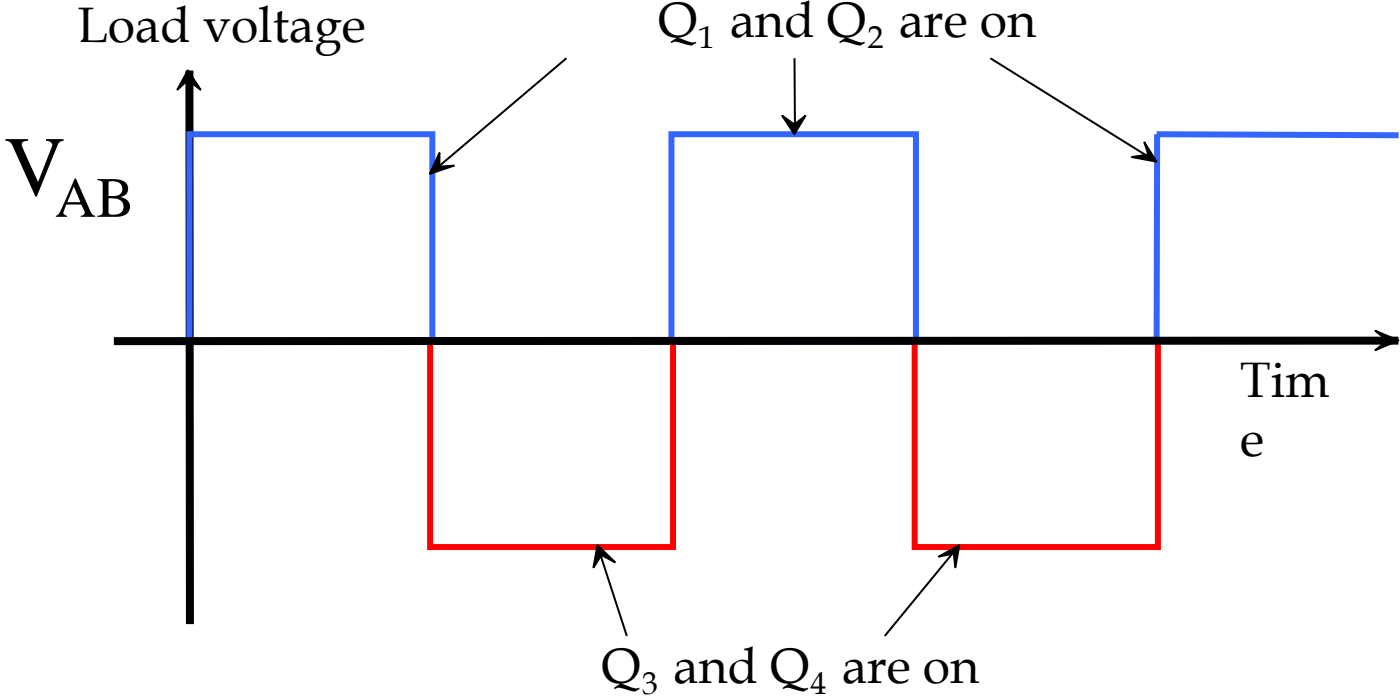
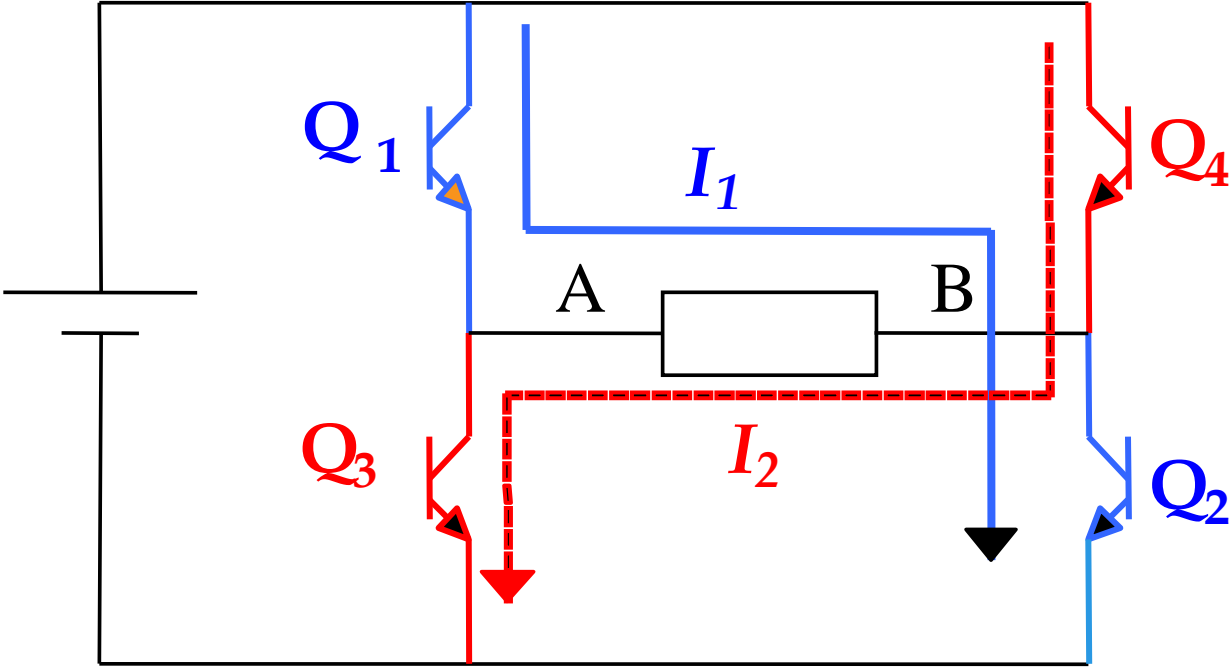


3-Phase DC/AC

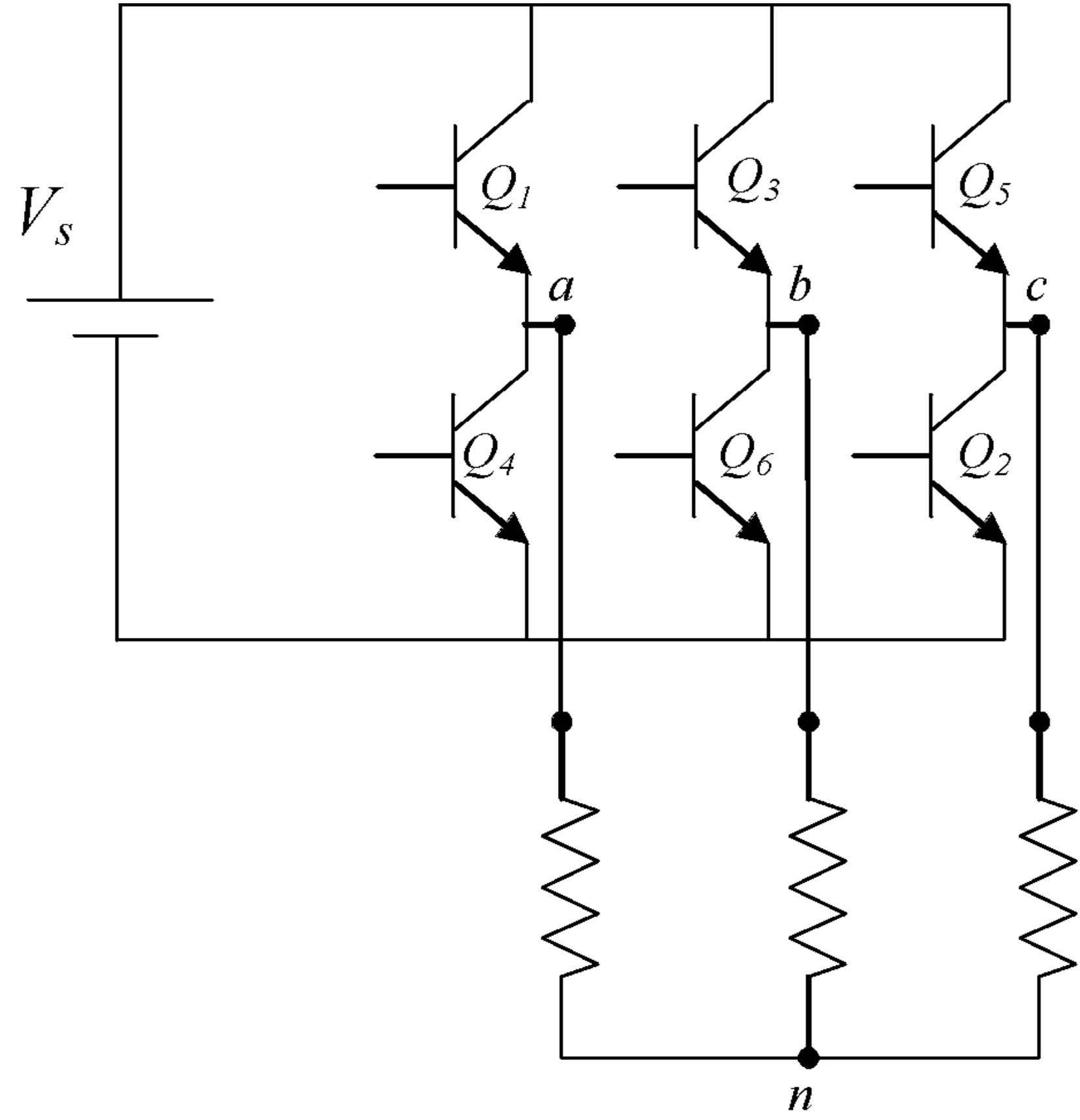

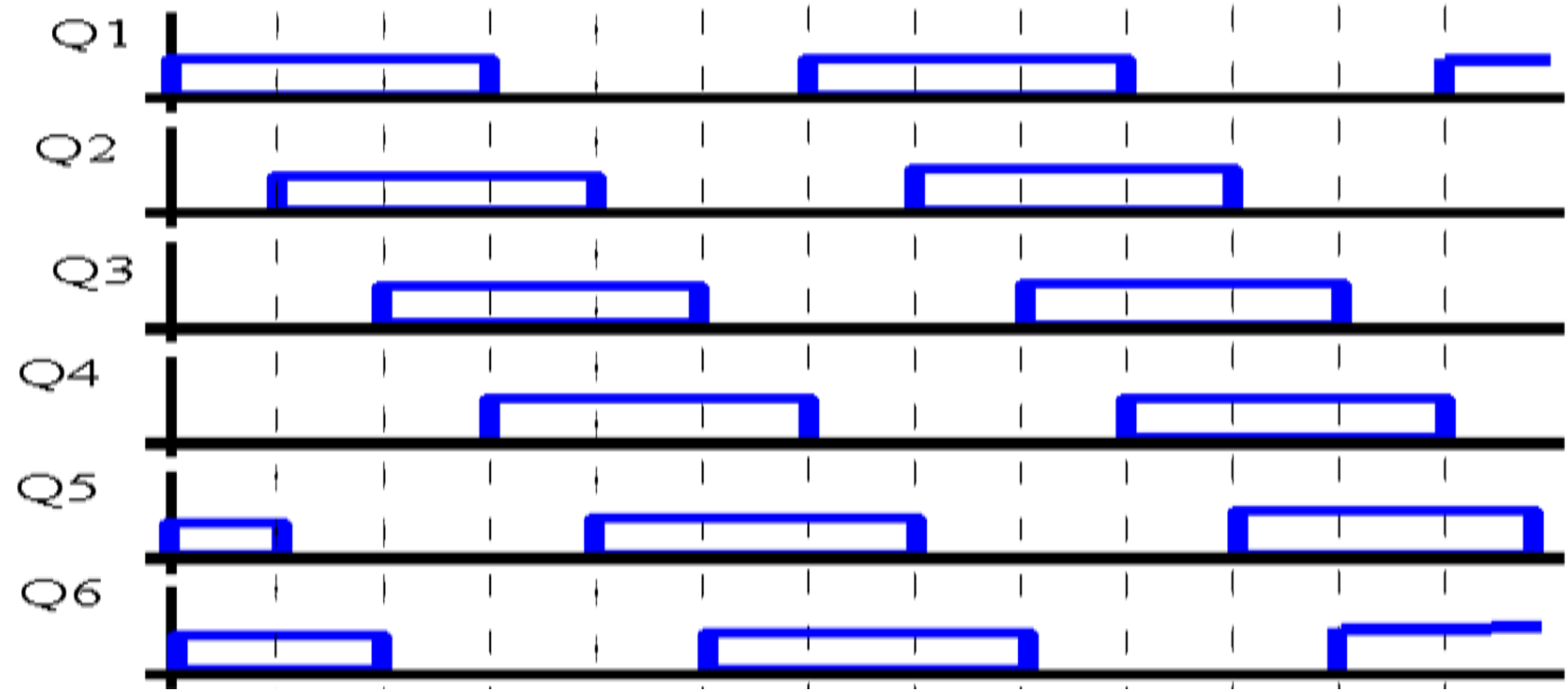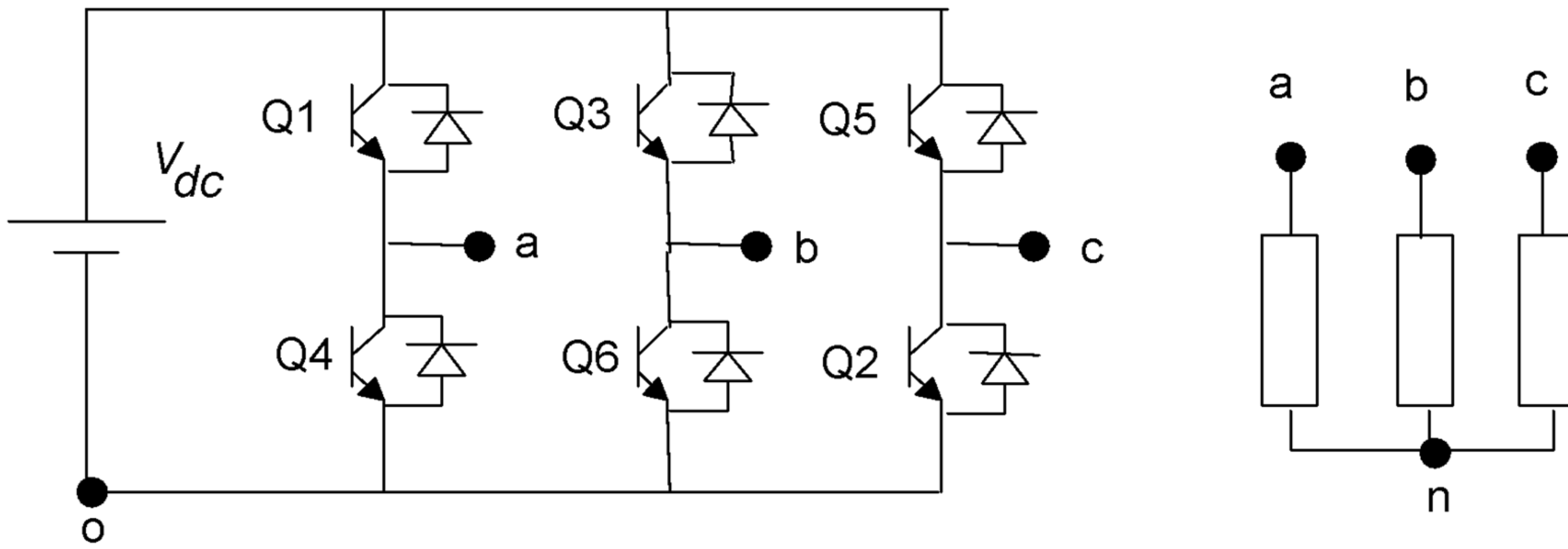


First Time Interval

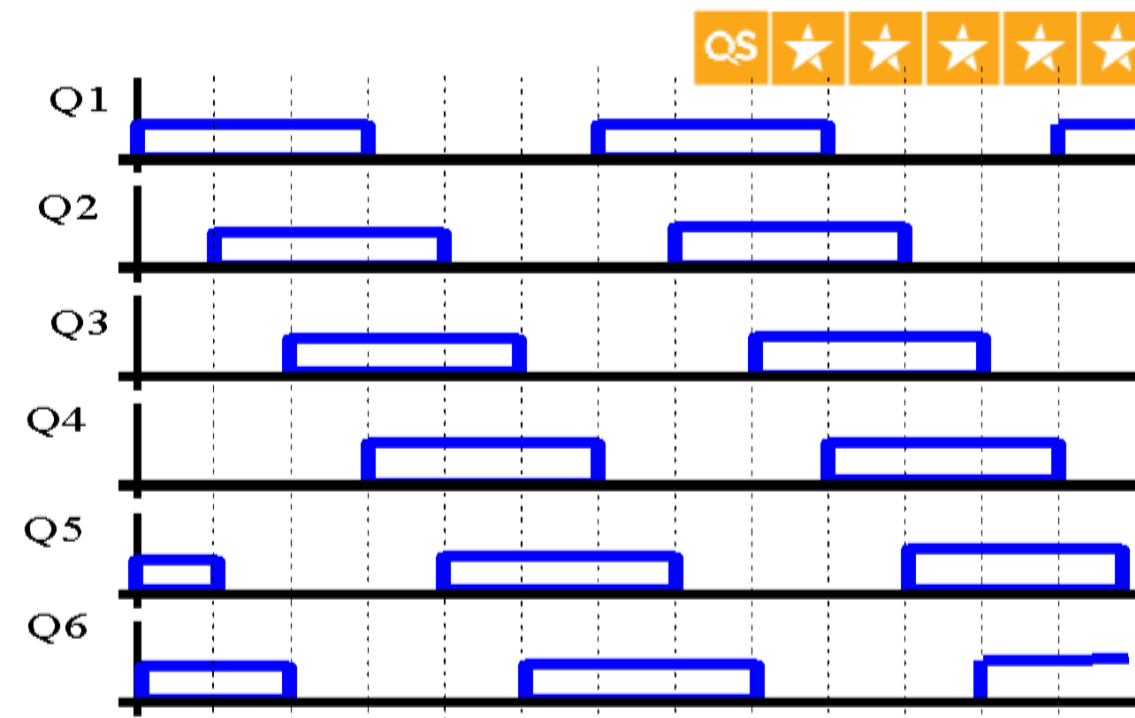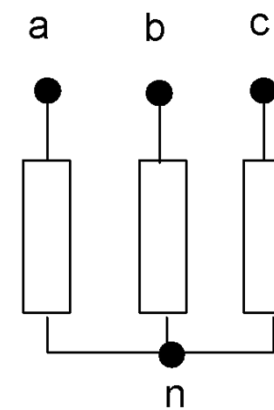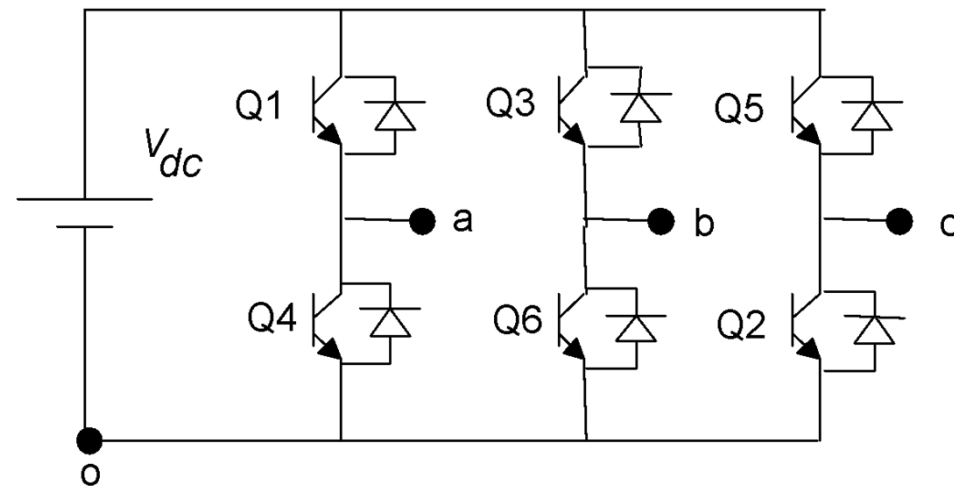




$$v_{ab} = v_a - v_b = V_{dc}$$

$$v_{bc} = v_b - v_c = -V_{dc}$$

$$v_{ca} = v_c - v_a = 0$$

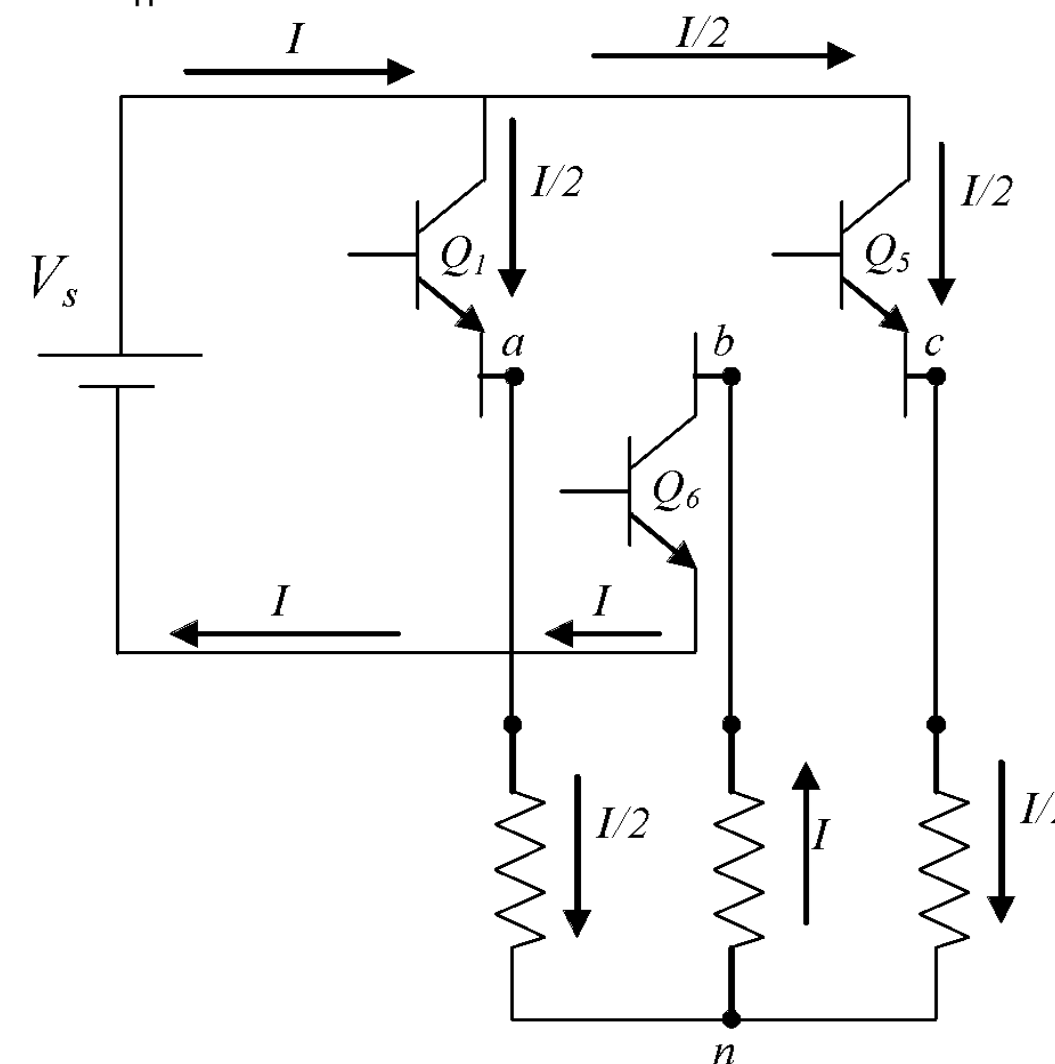


Second Time Interval

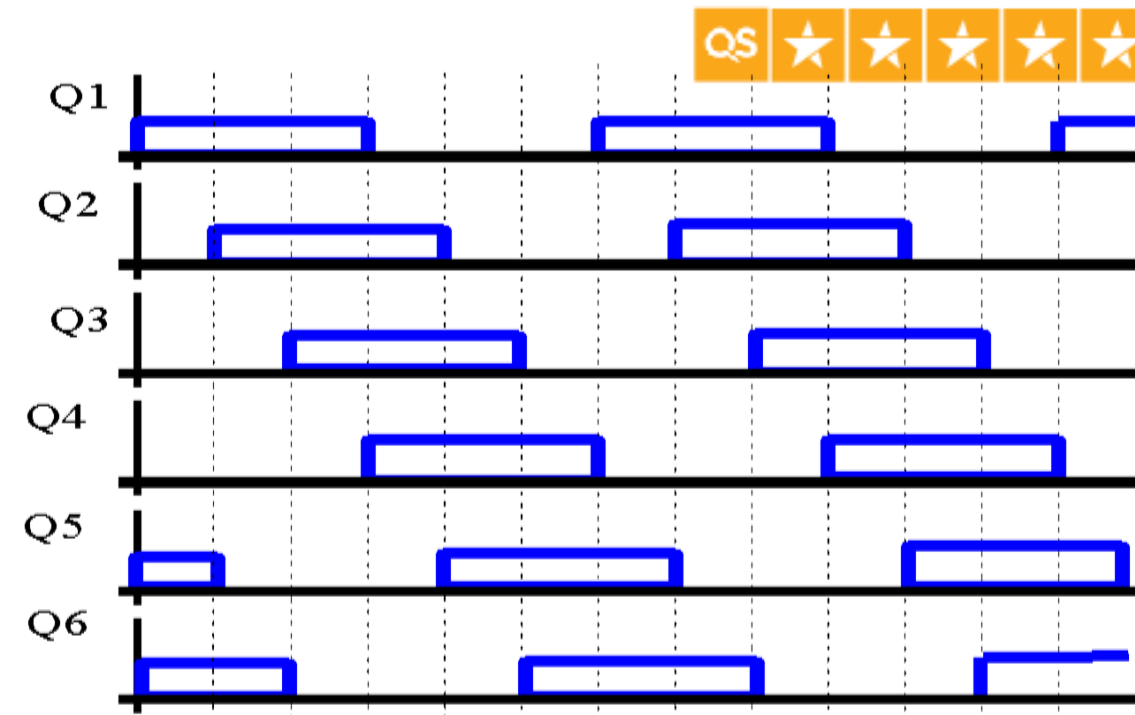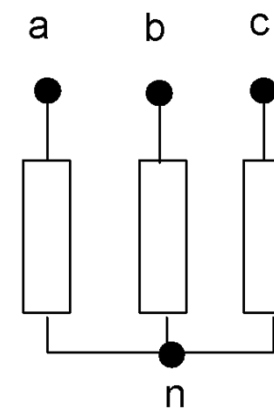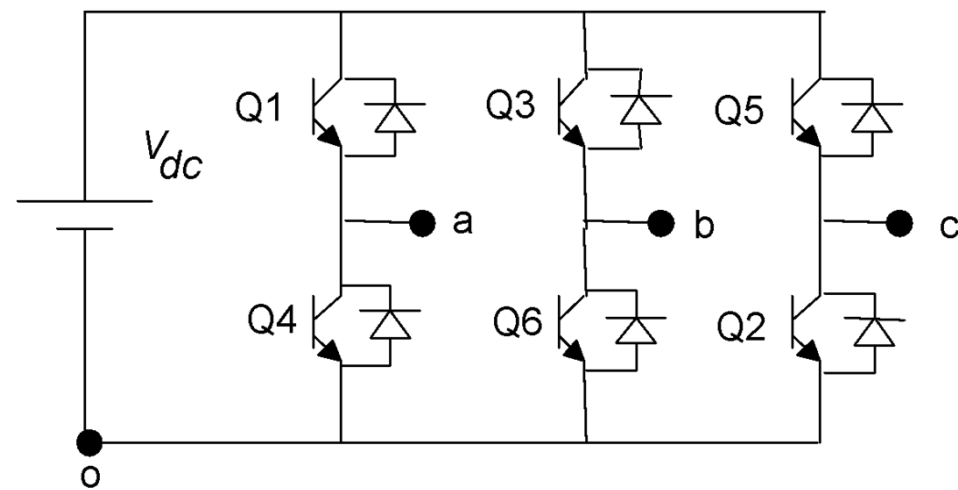


$$v_{ab} = v_a - v_b = V_{dc}$$

$$v_{bc} = v_b - v_c = 0$$

$$v_{ca} = v_c - v_a = -V_{dc}$$

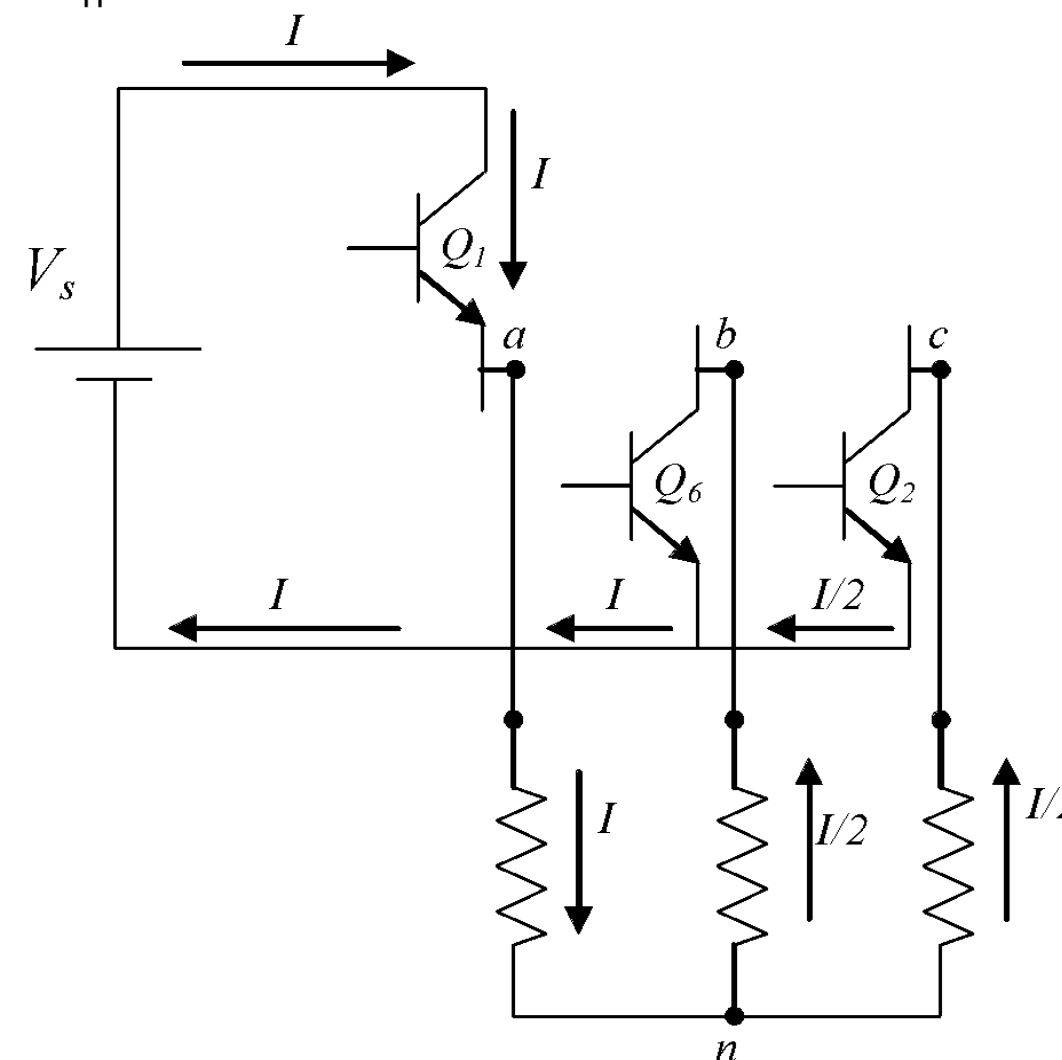


Voltage Waveforms Across Load

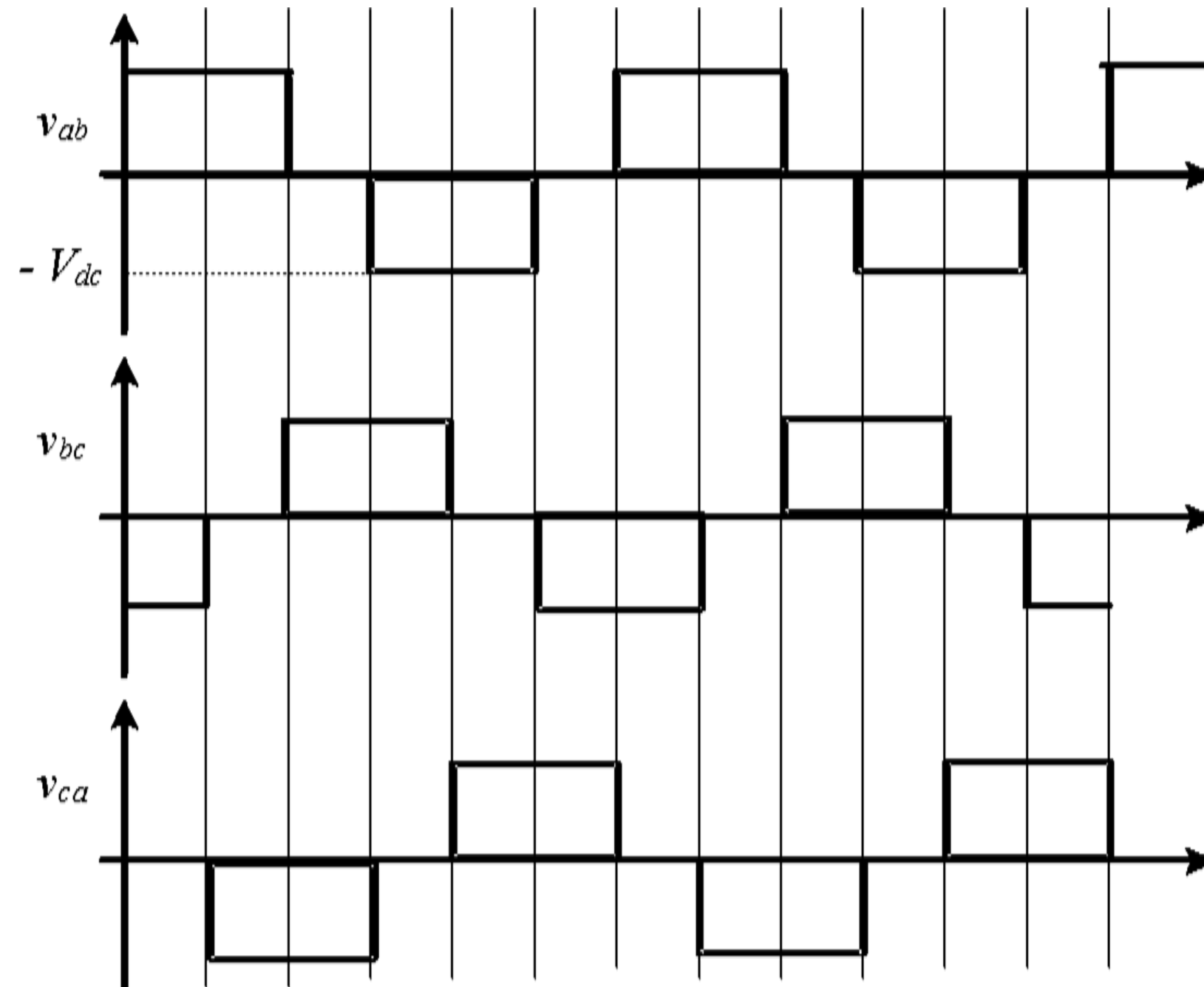

- Waveforms are symmetrical and equal in magnitude
- Waveforms are shifted by 120 degrees

$$V_{rms} = \sqrt{\frac{2}{9}} V_{dc}$$

$$V_{rms} = 0.47 V_{dc}$$

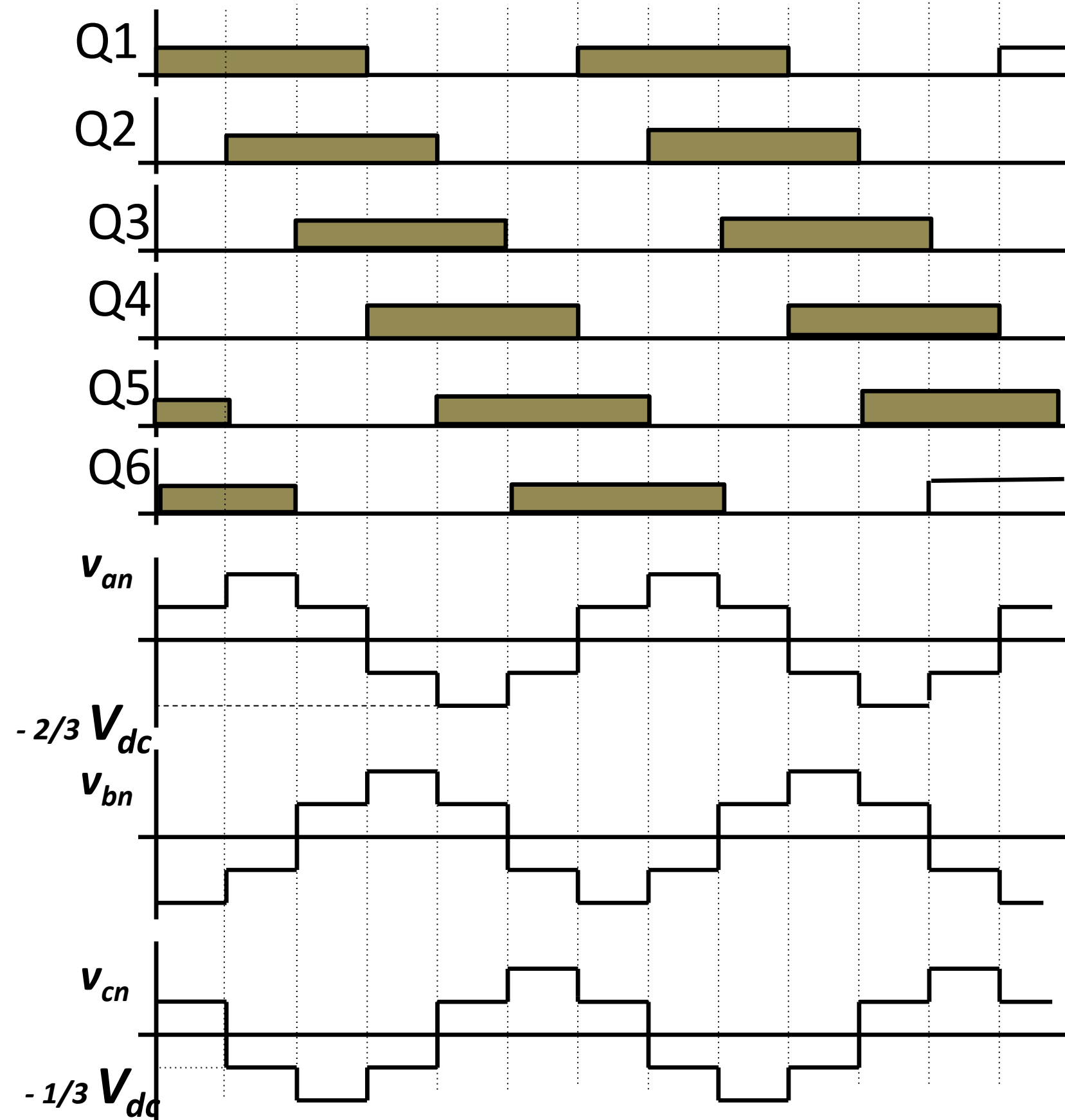




DC/DC Converters



DC-to-DC Conversion

- * **Step-down (Buck)** converter: the output voltage of the converter is lower than the input voltage
- * **Step-up (Boost)** converter: the output voltage is higher than the input voltage.
- * **Step-down/step-up (Buck-Boost)** converter.

Step Down (Buck converter)

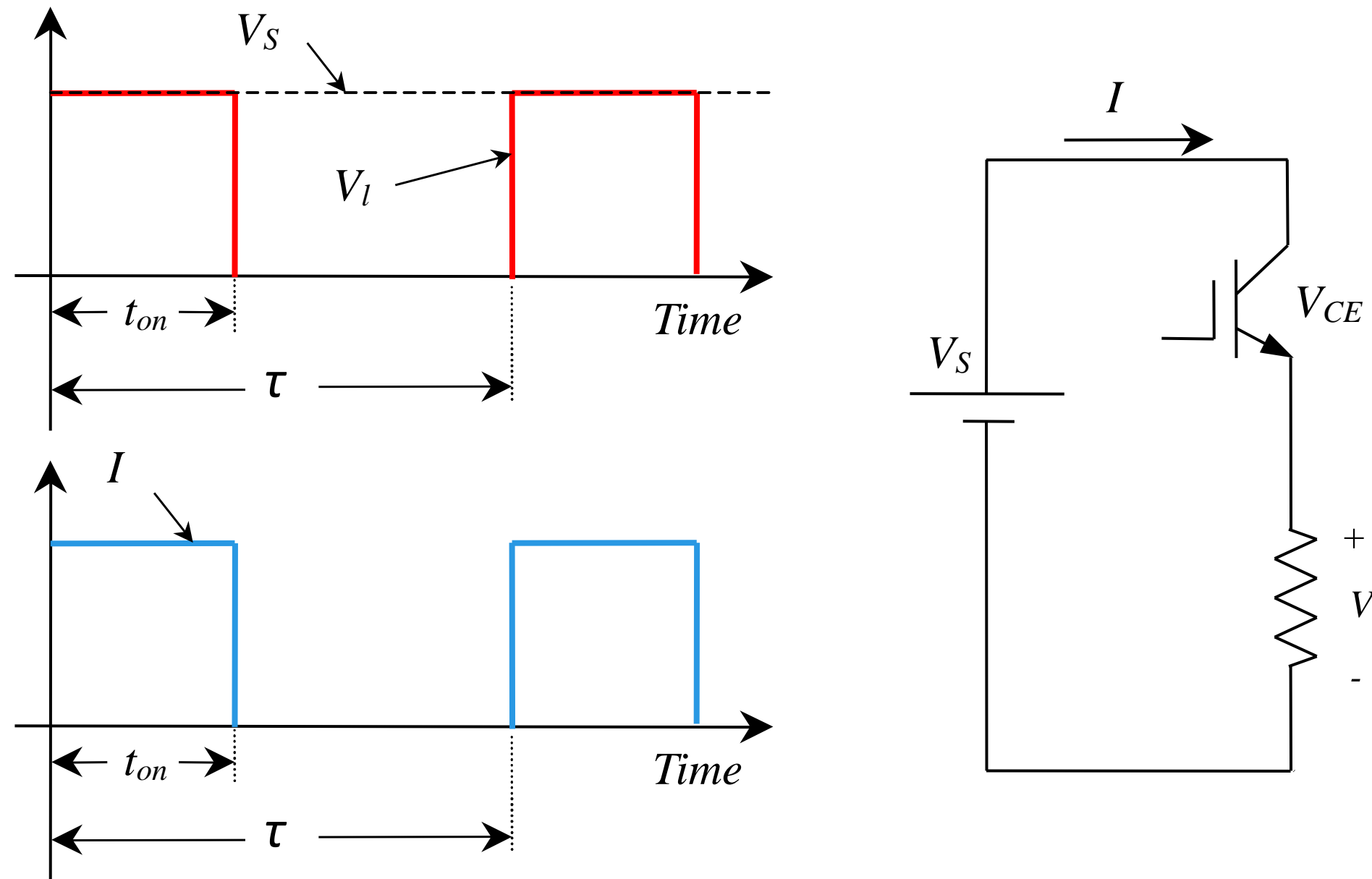

$$V_{ave} = \frac{1}{\tau} \int_0^{t_{on}} V_S dt = \frac{t_{on}}{\tau} V_S = K V_S$$

Example



$$f = 5 \text{ kHz (switching frequency)}$$

$$V_s = 12 \text{ V}; V_{ave} = 5 \text{ V}; t_{on} = ?$$

Solution


$$\tau = \frac{1}{f} = \frac{1}{5} = 0.2 \text{ ms}$$


$$V_{ave} = \frac{t_{on}}{\tau} V_s = K V_s$$

$$K = \frac{5}{12} = 0.417$$

$$t_{on} = 0.417 \times 0.2 = 0.0834 \text{ ms}$$



Step up (Boost converter)

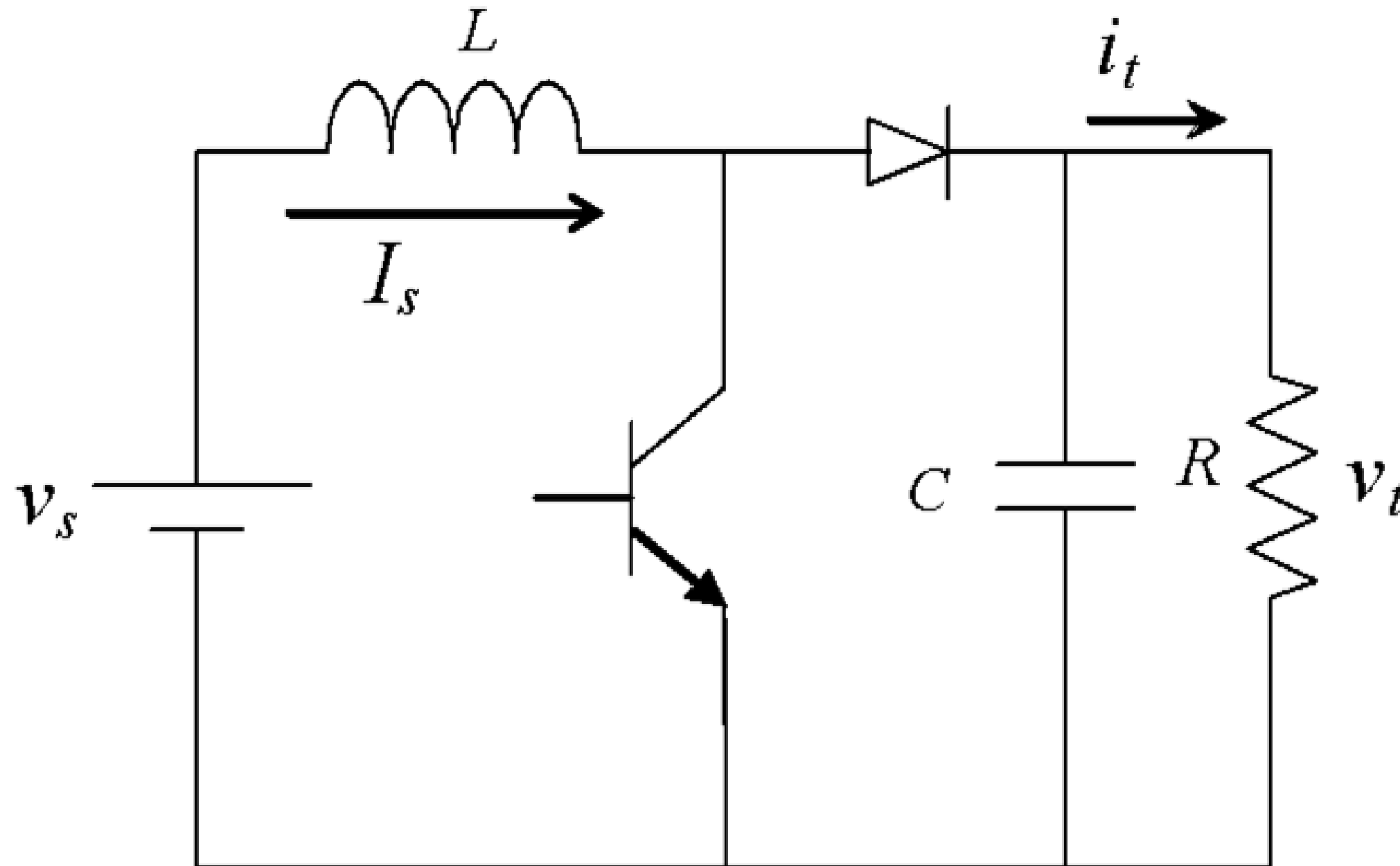


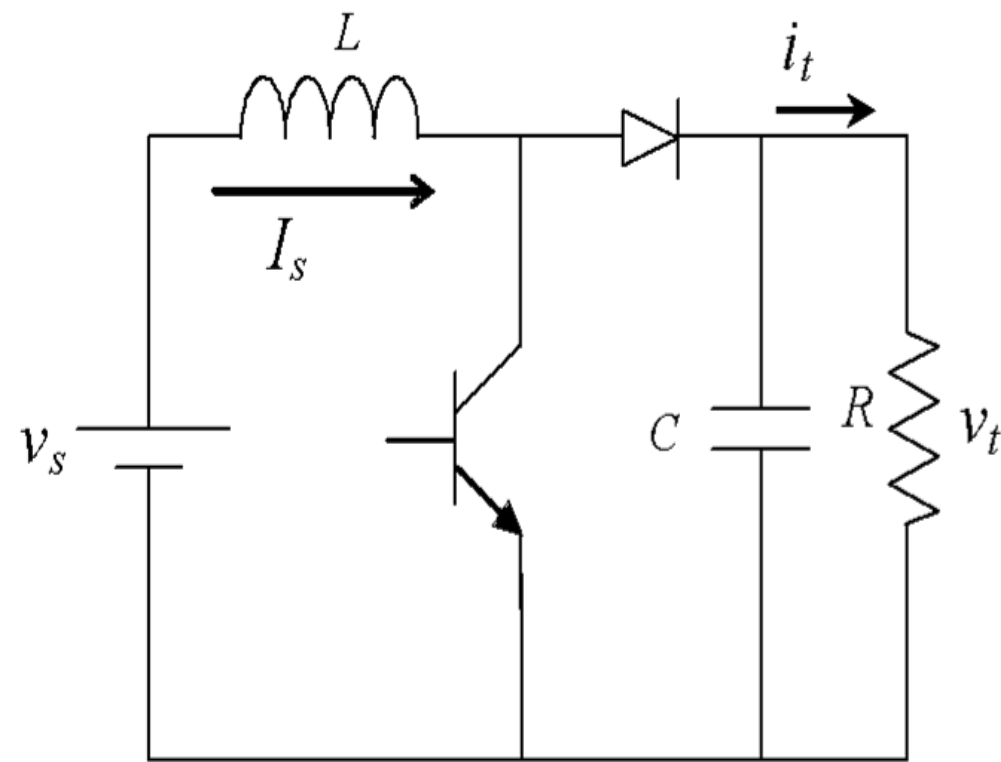


Keep in mind

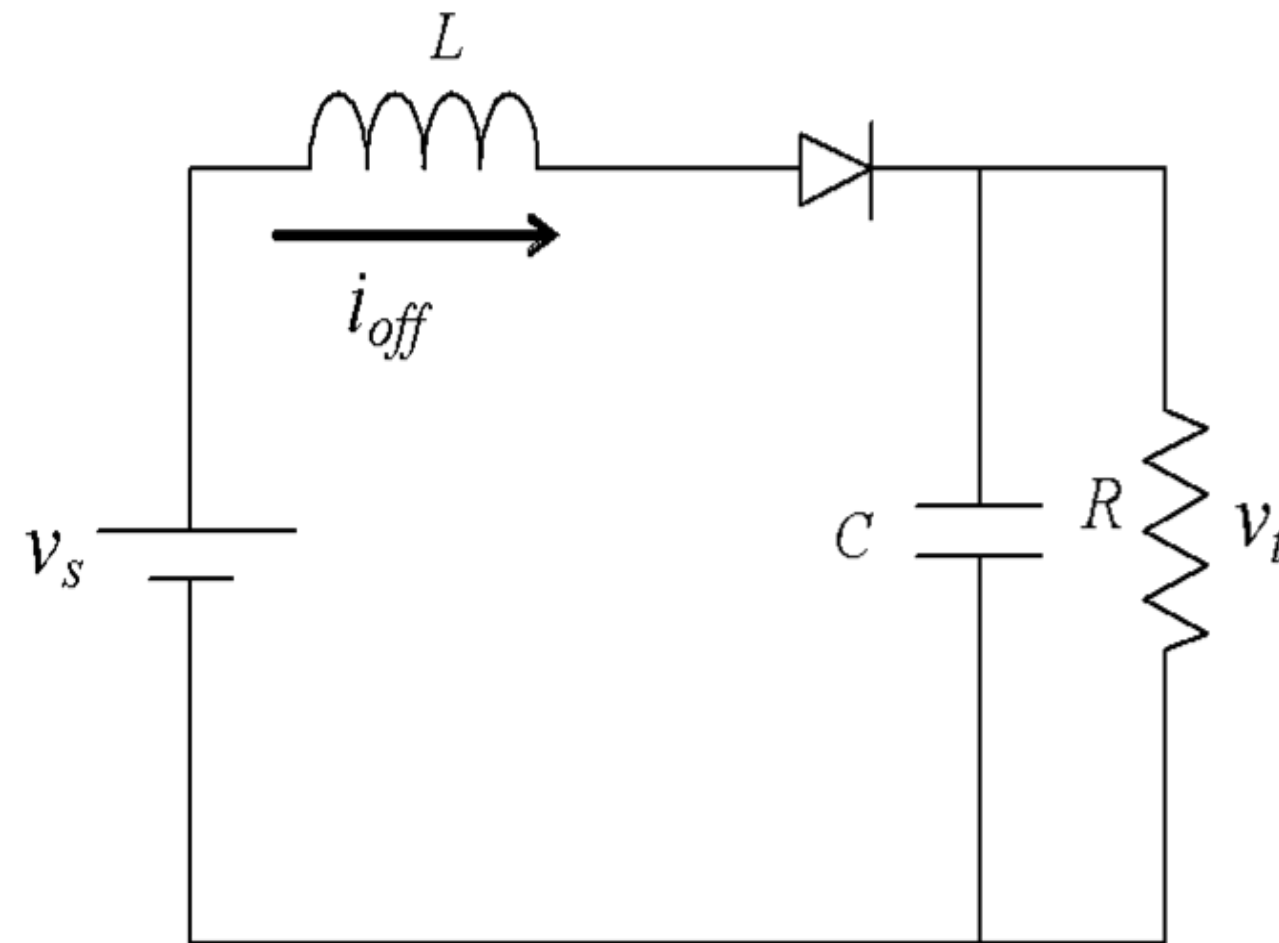
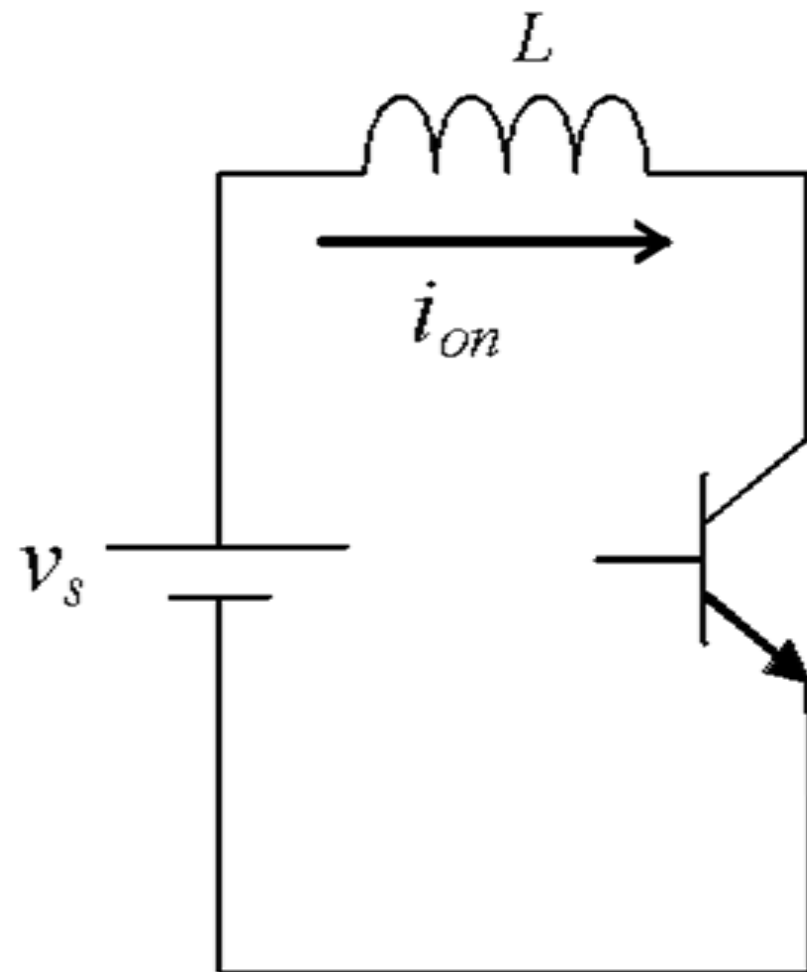
- Inductor current is unidirectional
- Inductor cannot permanently store energy
- Voltage across inductor reverses



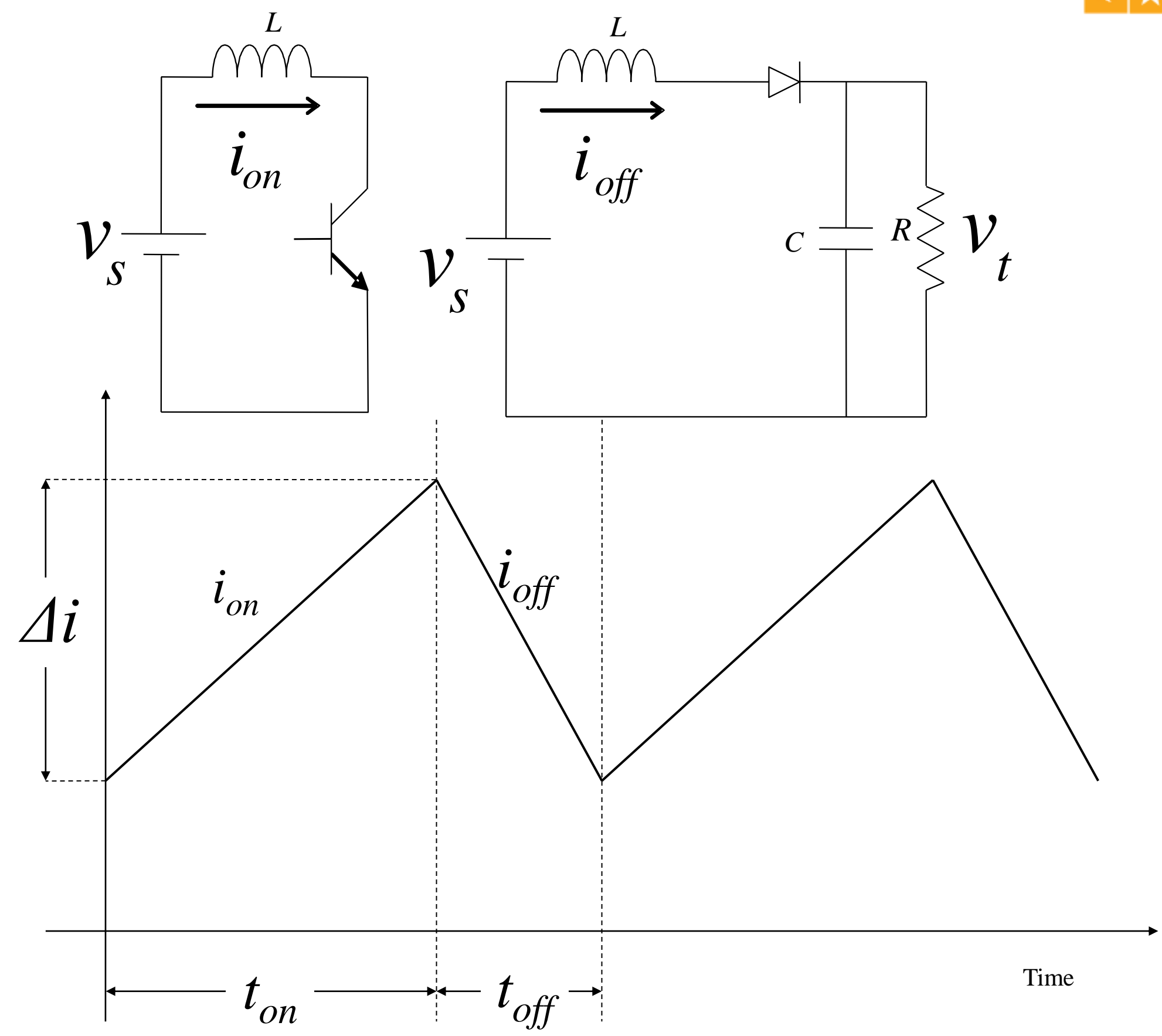

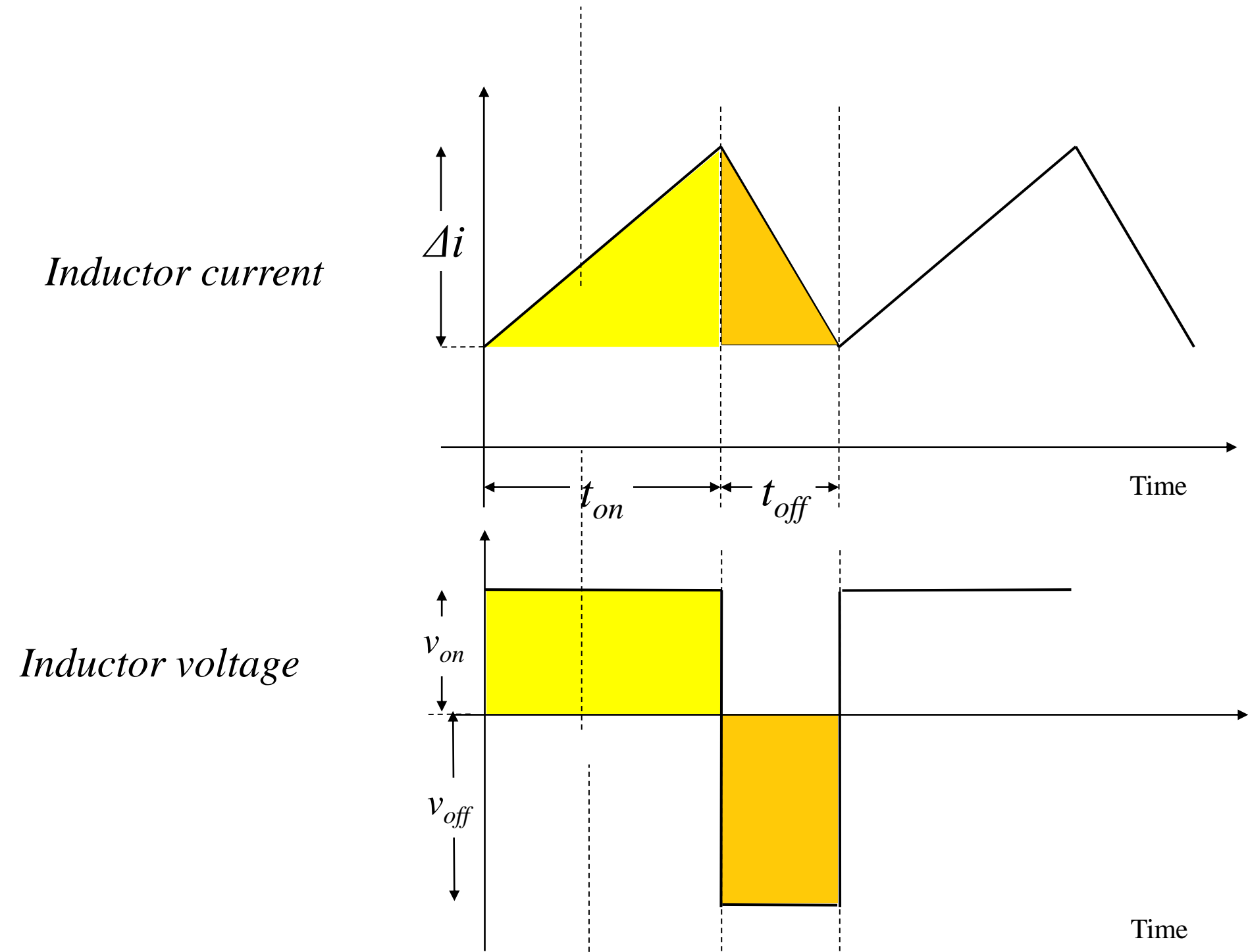

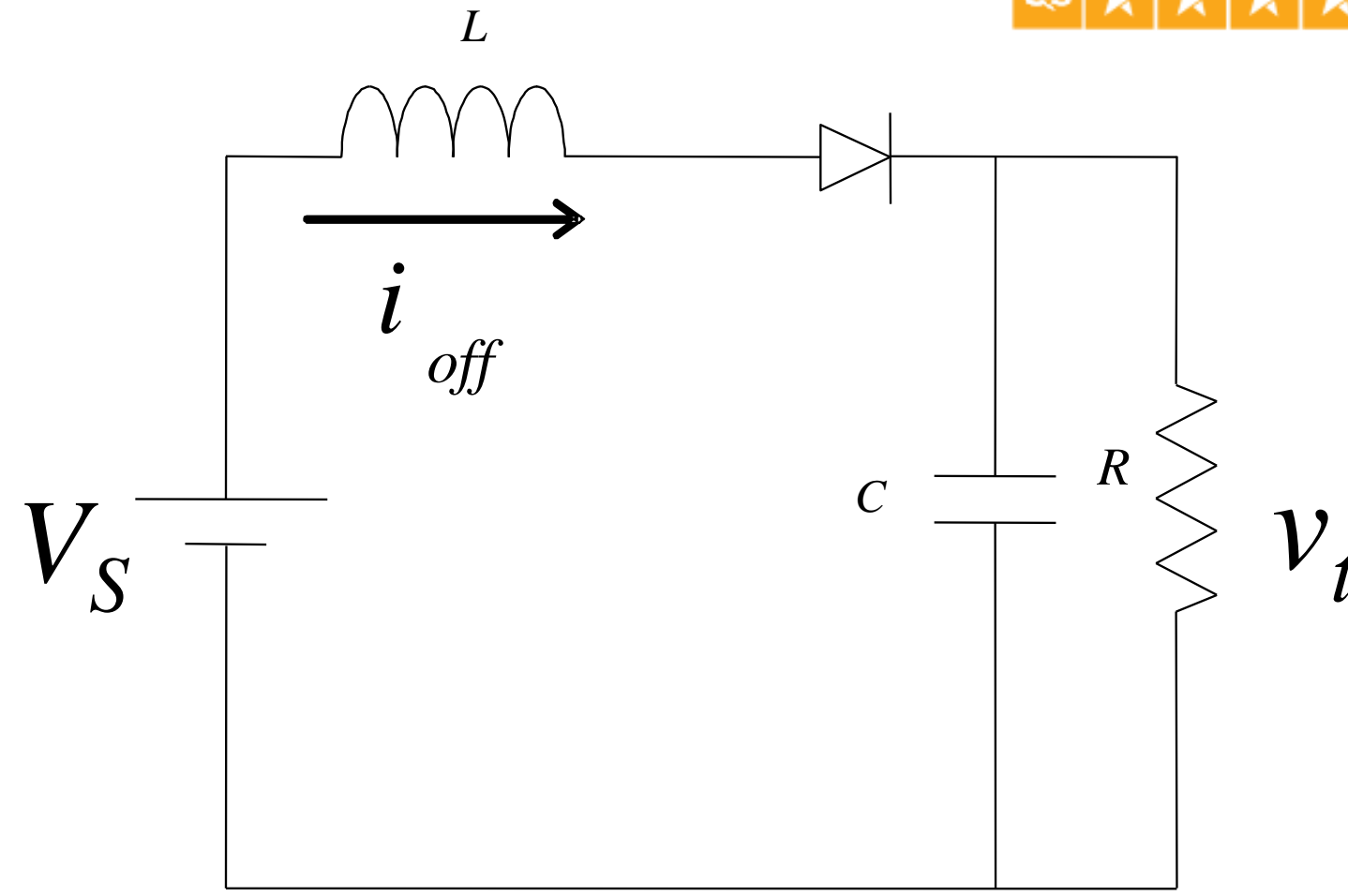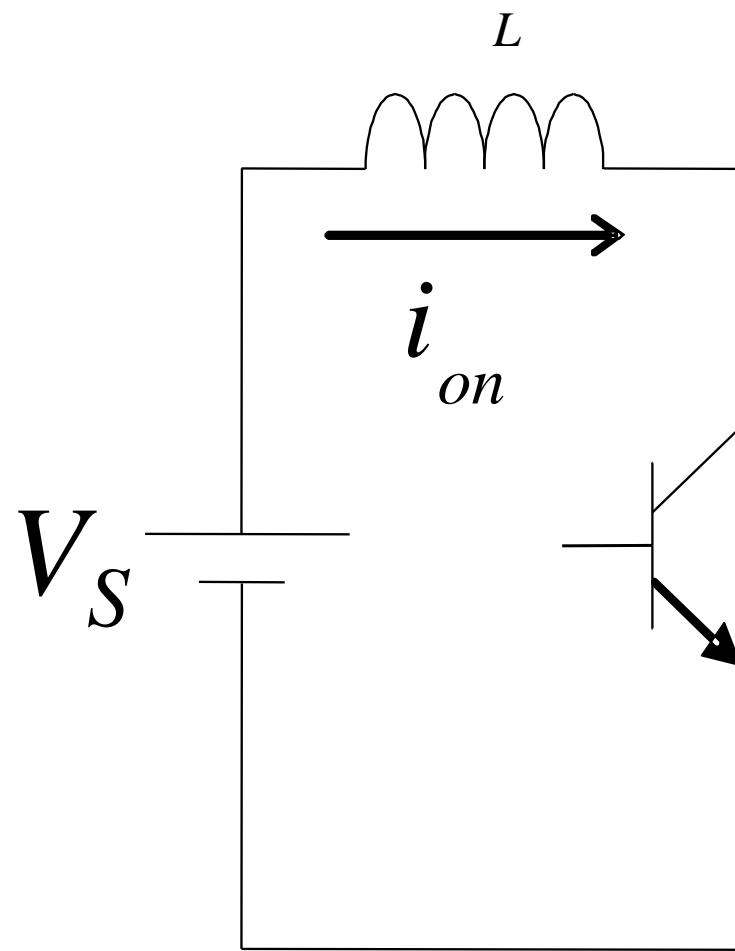- Energy is acquired by inductor
- Energy is released by inductor



$$V_L = L \frac{di}{dt} = L \frac{\Delta i_{on}}{t_{on}} = V_s$$

$$V_s = v_t - L \frac{\Delta i_{off}}{t_{off}}$$

At steady state $\Delta i_{on} = \Delta i_{off}$

$$v_t = V_s + L \frac{\Delta i_{off}}{t_{off}} = V_s \left(1 + \frac{t_{on}}{t_{off}} \right)$$

Example



- A Boost converter is used to step up 20V into 50V. The switching frequency of the transistor is 5kHz, and the load resistance is 10Ω. Compute the following:
 1. The value of the inductance that would limit the current ripple at the source side to 100mA
 2. The average current of the load
 3. The power delivered by the source
 4. The average current of the source

Solution

Part 1

$$V_t = V_s \left(1 + \frac{t_{on}}{t_{off}} \right)$$

$$50 = 20 \left(1 + \frac{t_{on}}{t_{off}} \right)$$

$$t_{on} = 1.5 * t_{off}$$

$$t_{on} + t_{off} = \frac{1}{f} = \frac{1}{5} = 0.2 \text{ ms}$$

$$\begin{aligned} t_{on} &= 1.5 * t_{off} = 1.5 * (0.2 - t_{on}) \\ &= 0.12 \text{ ms} \end{aligned}$$

$$V_L = L \frac{\Delta i_{on}}{t_{on}} = V_s$$

$$20 = L \frac{100}{0.12} \quad L = 24 \text{ mH}$$

Part 2

$$I_t = \frac{V_t}{R} = \frac{50}{10} = 5 \text{ A}$$


Part 3


$$P = V_t * I_t = 50 * 5 = 250 \text{ W}$$

Part 4

$$I_s = \frac{P}{V_s} = \frac{250}{20} = 12.5 \text{ A}$$


Buck-Boost converter

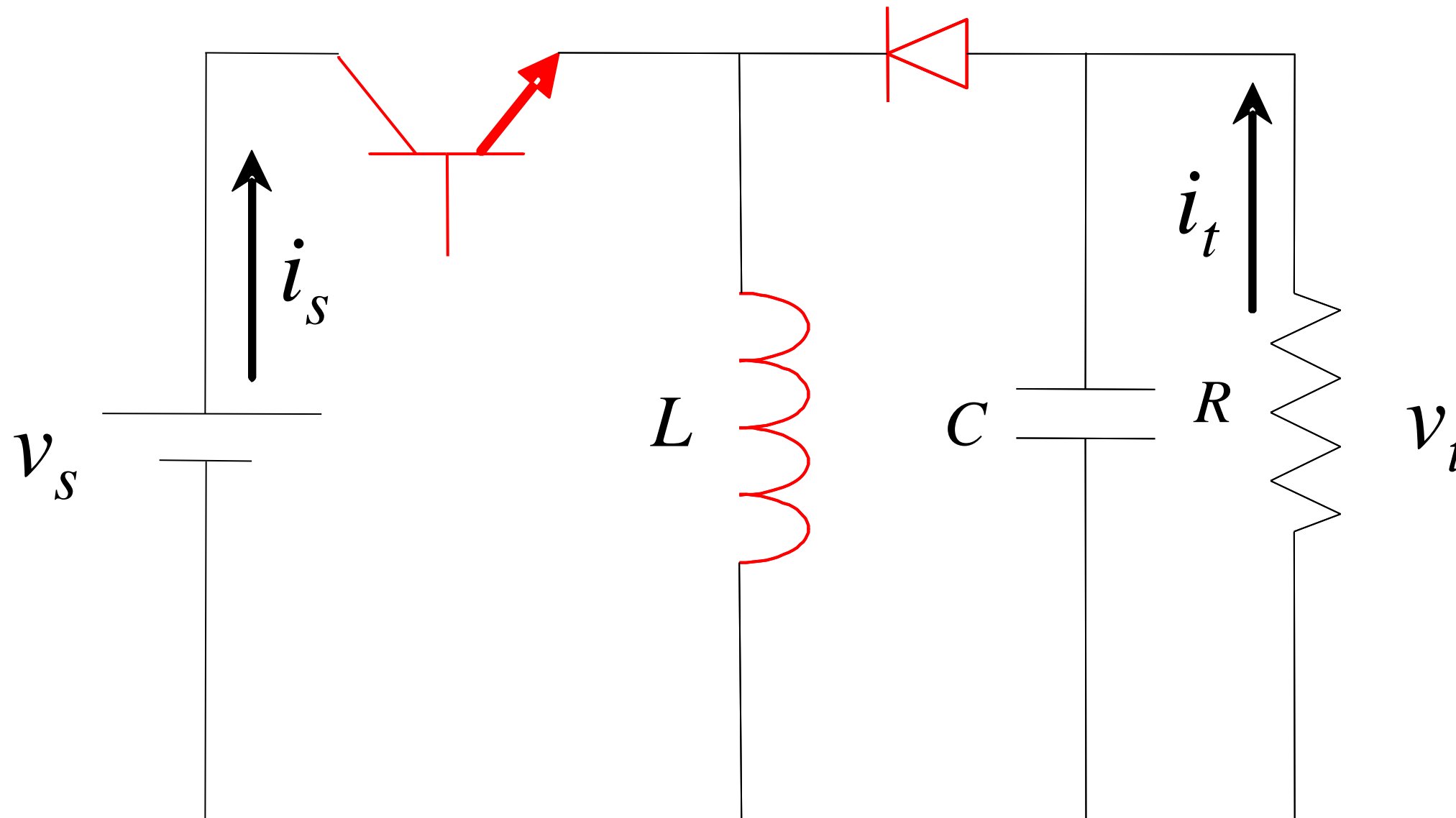

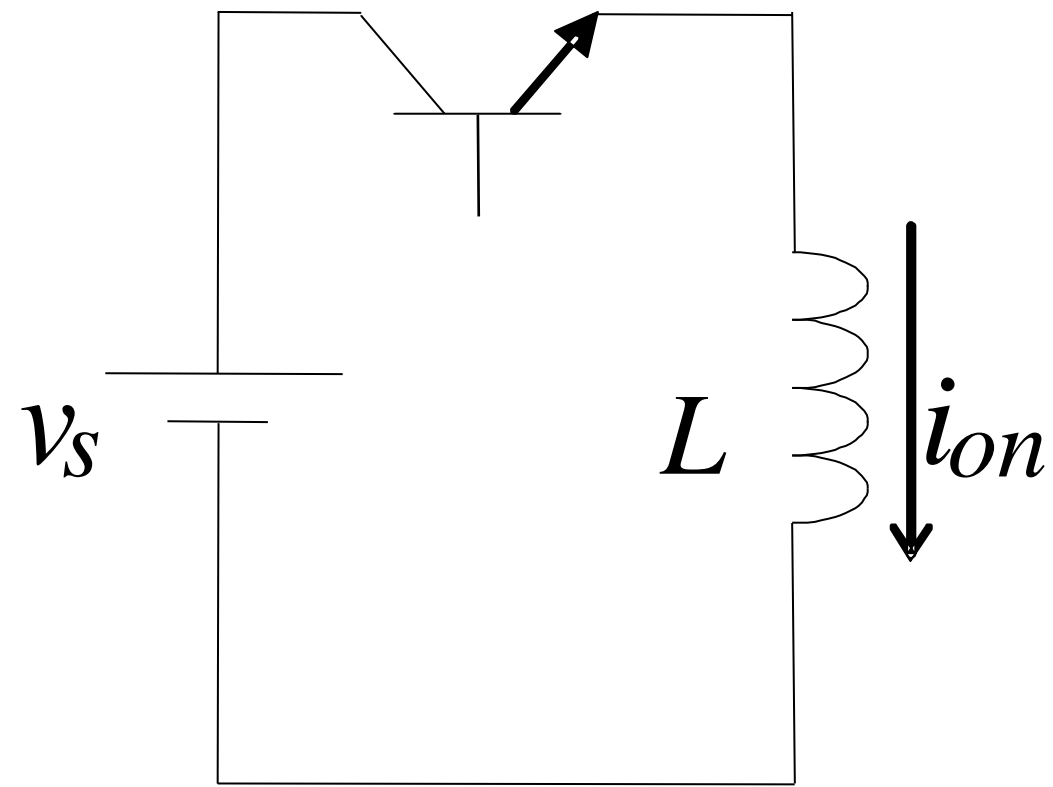

$$v_L = L \frac{\Delta i_{on}}{t_{on}} = v_s$$

if $\Delta i_{on} = \Delta i_{off}$

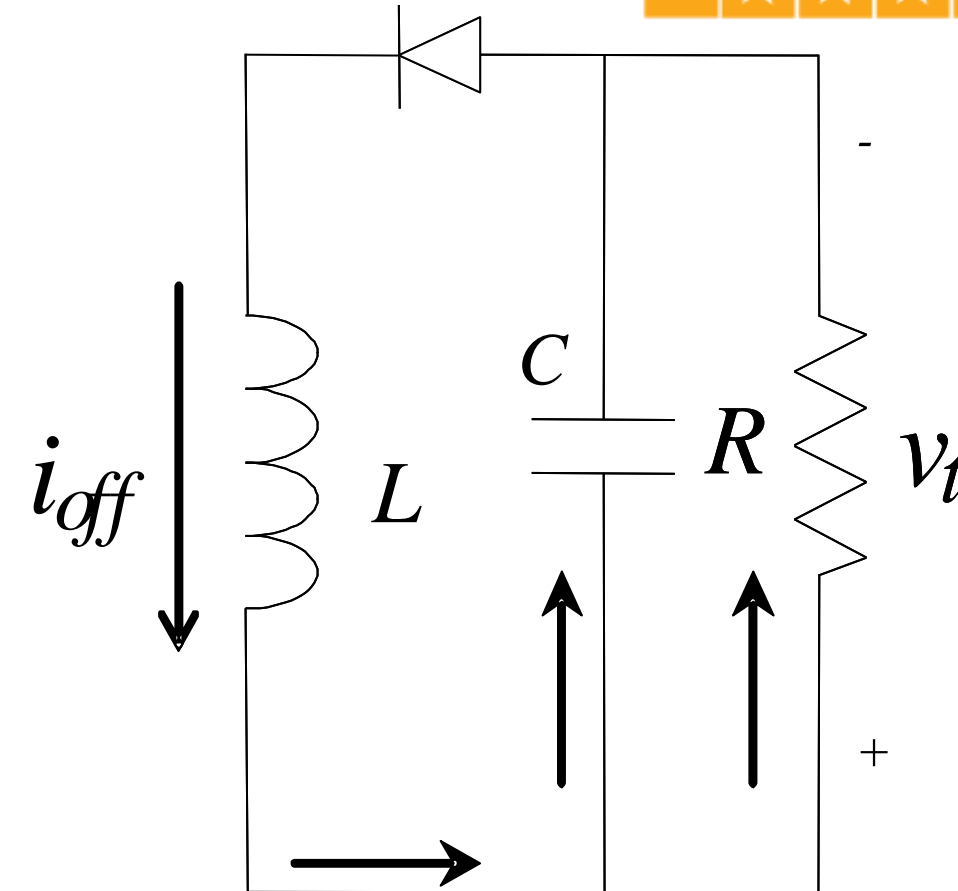


$$v_L = -L \frac{\Delta i_{off}}{t_{off}} = v_t$$

$$v_t = -v_s \frac{t_{on}}{t_{off}}$$




AC/AC Converters

AC/AC Converter

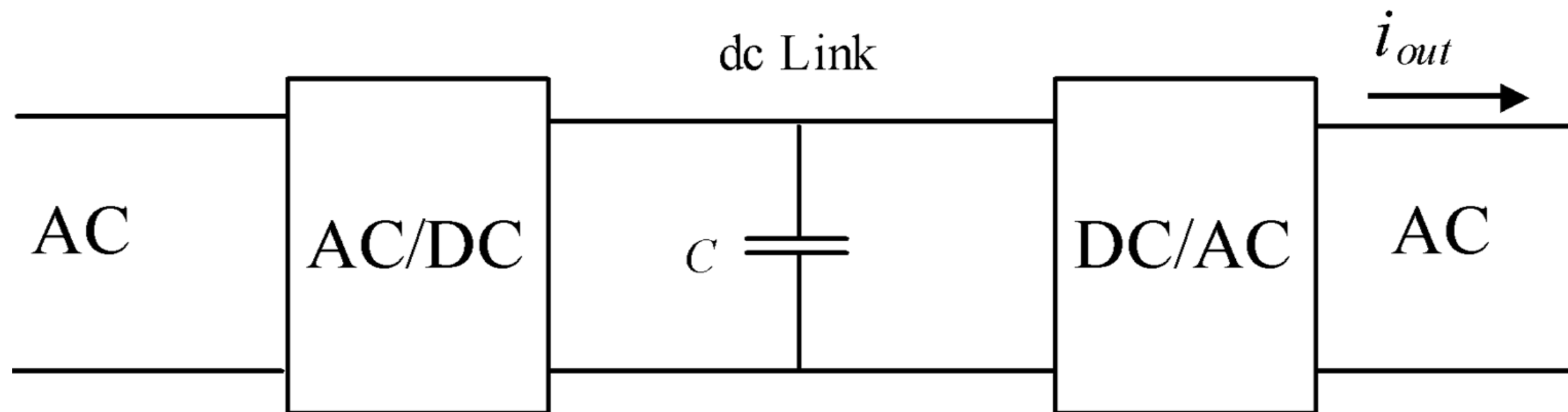



AC/DC Converter

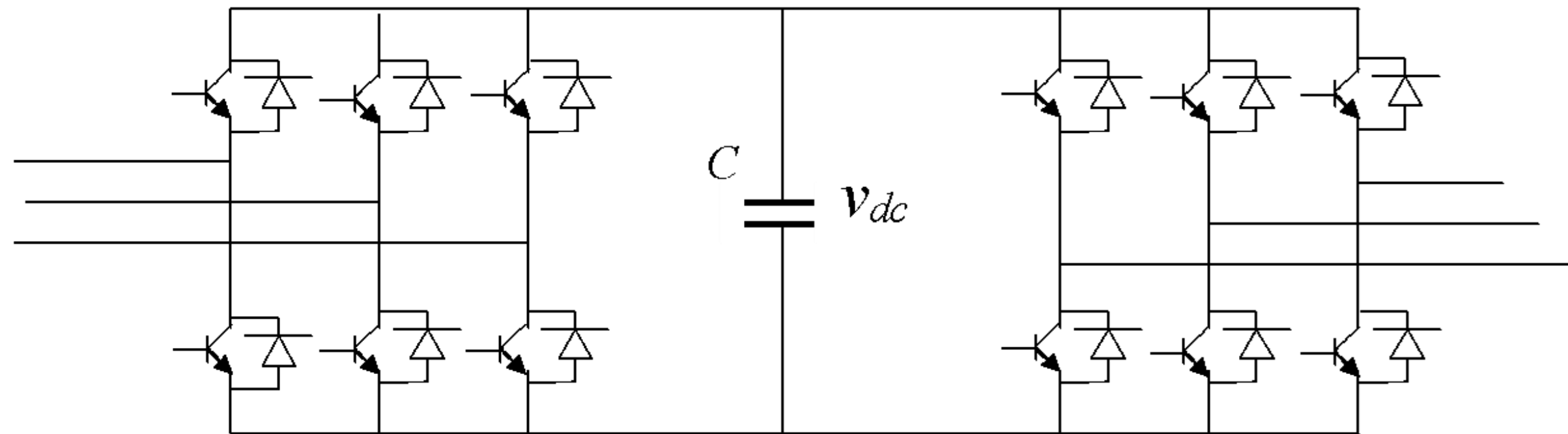





Control Parameters

- *Frequency*
- *Voltage*
- *Phase shift*
- *Sequence*

Pulse-Width Modulation (PWM)

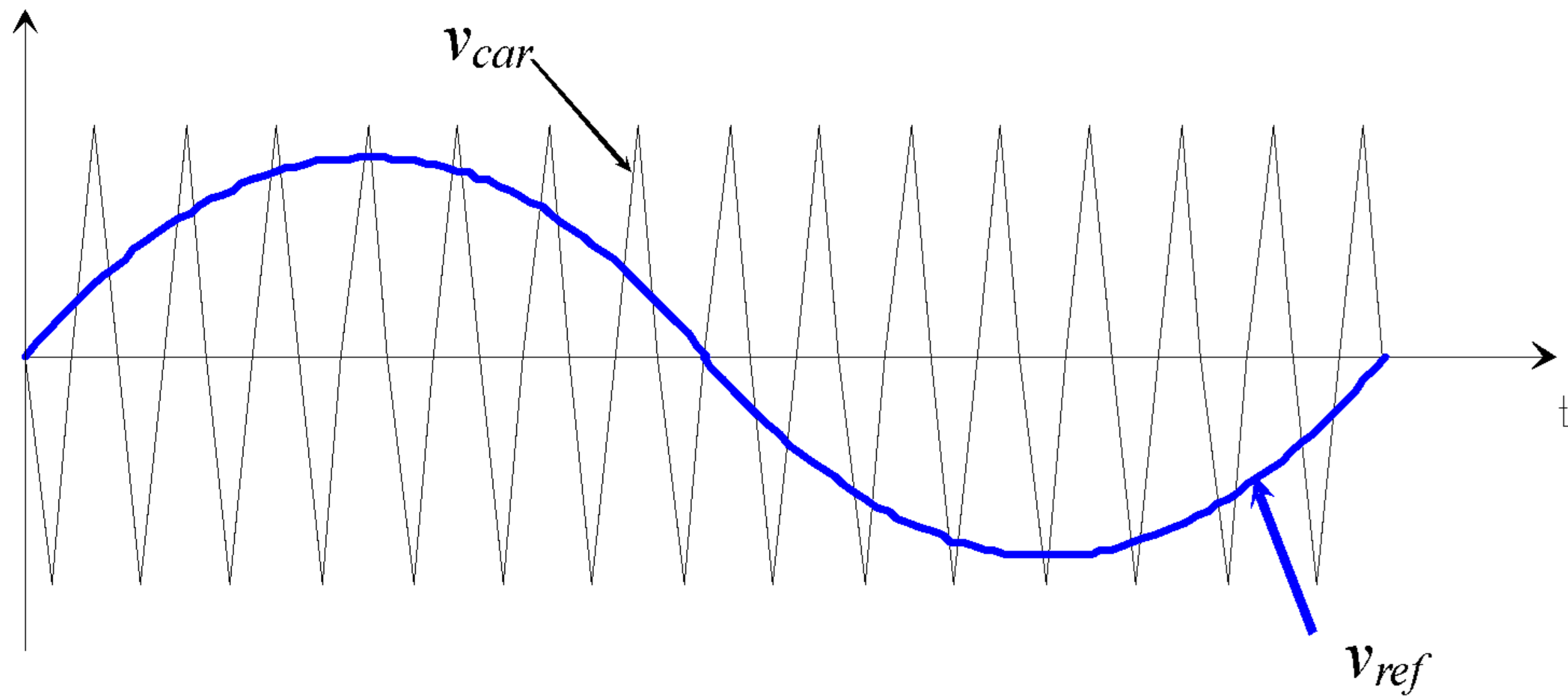


Switching of Phase a

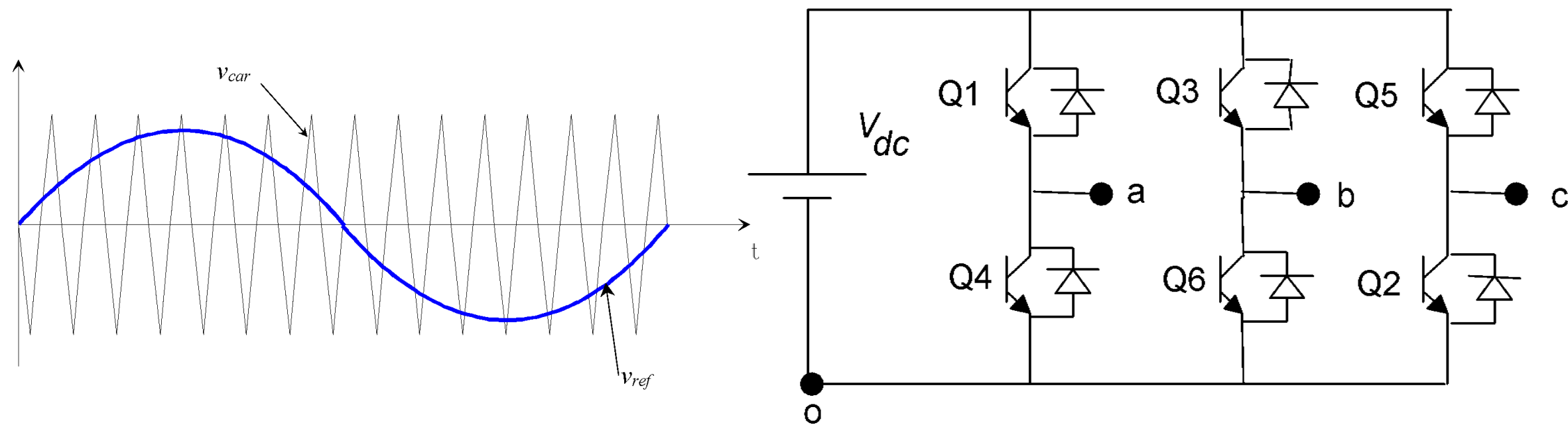


The switching rule

If $v_{ref} > v_{car}$ Then Q_1 is closed, Q_4 is open $\Rightarrow v_{ao} = V_{dc}$

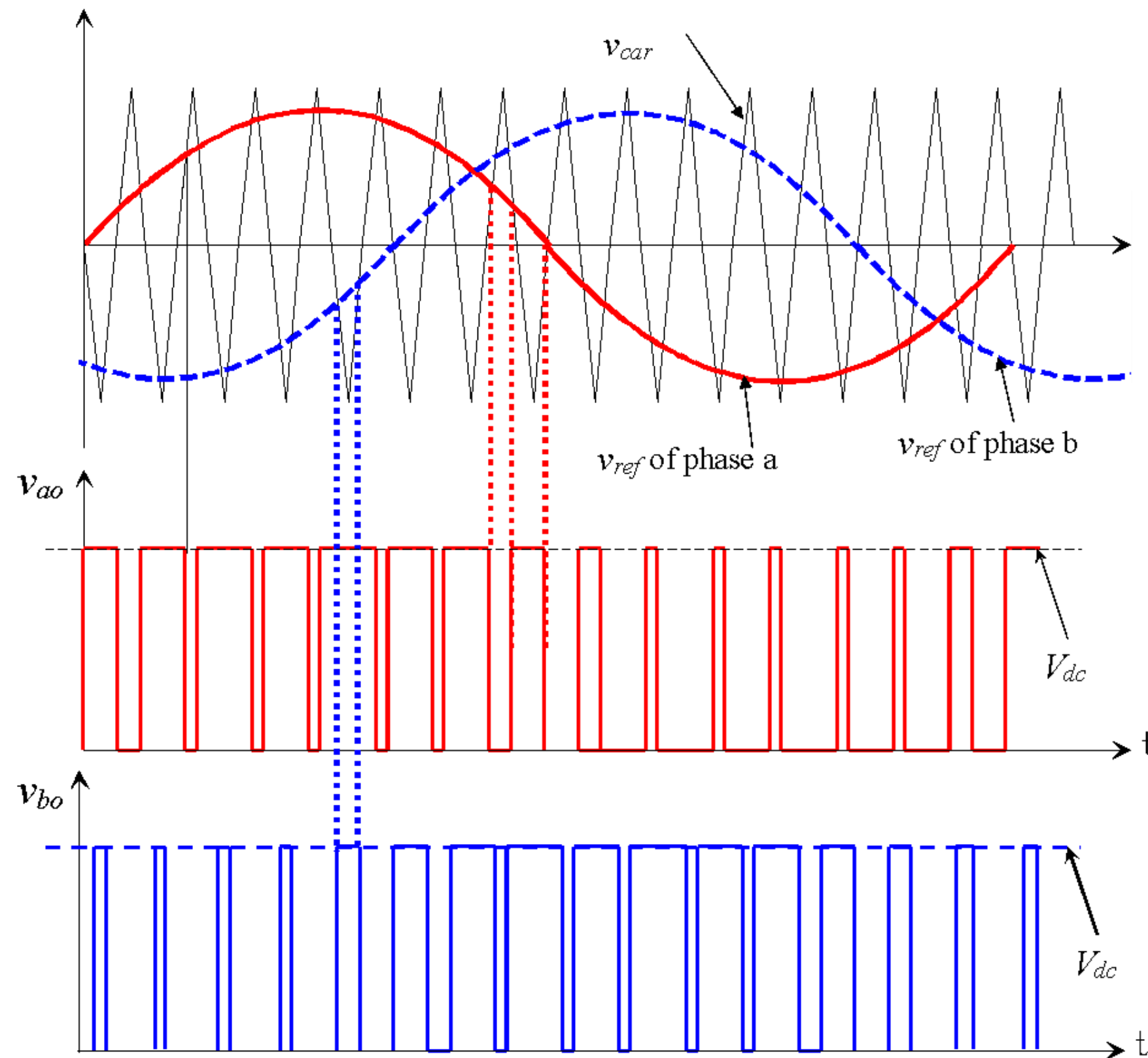If $v_{ref} < v_{car}$ Then Q_4 is closed, Q_1 is open $\Rightarrow v_{ao} = 0$



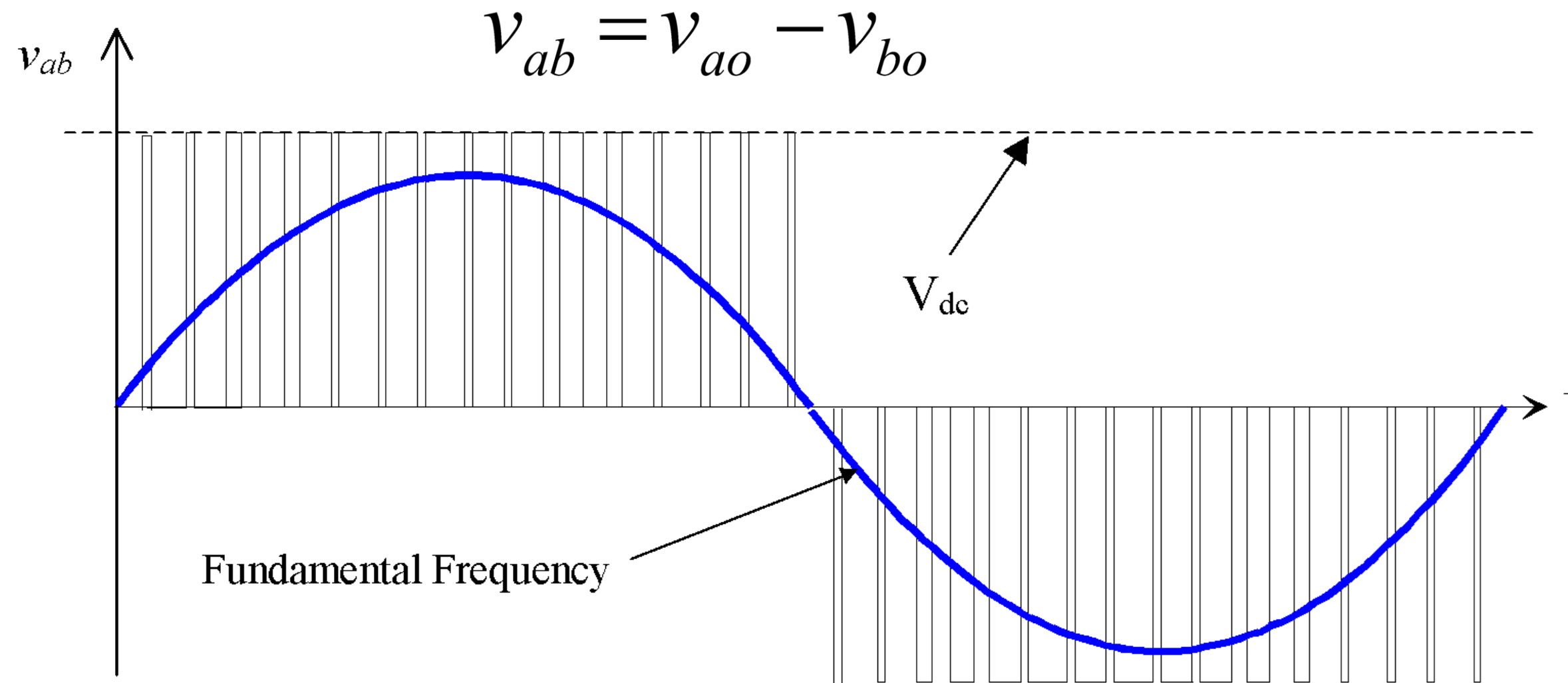

$$v_{ab}(t) = \sqrt{3} m_a \frac{V_{dc}}{2} \sin(2\pi f_s t) + \text{Bessel harmonic terms}$$

$$m_a = \frac{V_{ref}}{V_{car}} \quad \text{Amplitude Modulation}$$

$$v_{ab}(t) = \sqrt{3} m_a \frac{V_{dc}}{2} \sin(2\pi f_s t) + \text{Bessel harmonic terms}$$


Ignore harmonics $v_{ab}(t) = \sqrt{3} m_a \frac{V_{dc}}{2} \sin(2\pi f_s t)$

Phase values $v_{phase}(t) = m_a \frac{V_{dc}}{2} \sin(2\pi f_s t - 30^\circ)$

rms of phase values $V_{rms} = m_a \frac{V_{dc}}{2\sqrt{2}} = 0.354 m_a V_{dc}$

$$V_{dc} = \frac{3\sqrt{3}}{\pi} V_{max} \cos \alpha$$

$$\alpha = \alpha_{ab} - 60^\circ$$

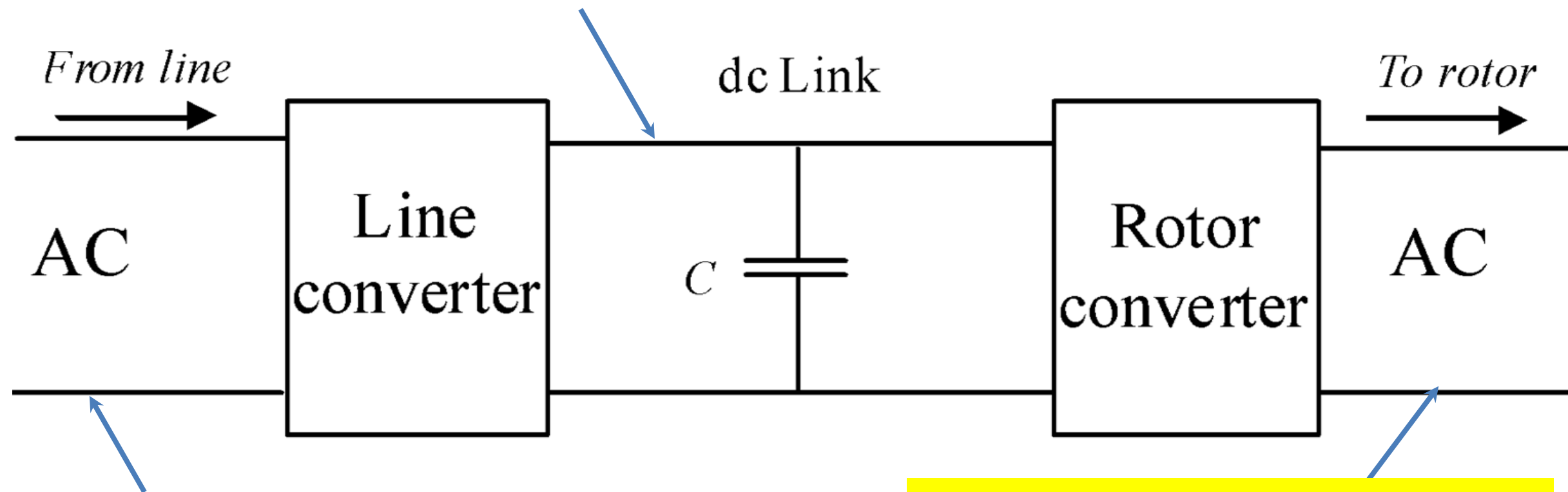

$$v_{an-in} = V_{max} \sin \omega_1 t$$


$$v_{an-out} = m_a \frac{V_{dc}}{2} \sin(\omega_2 t)$$

$$V_{out-rms} = \frac{m_a}{2\sqrt{2}} V_{dc} = 0.585 m_a V_{max} \cos \alpha$$

Control Parameters: Frequency



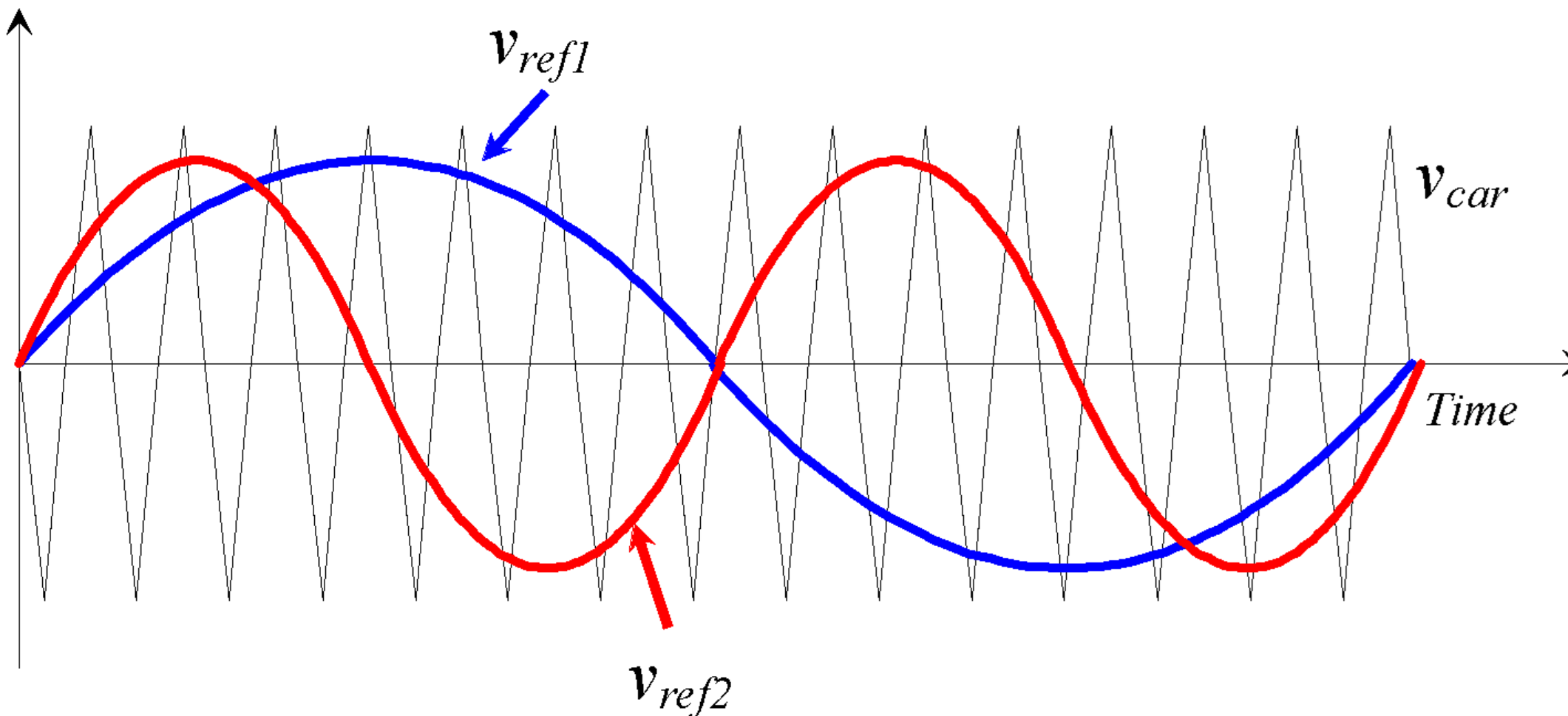
- **Frequency:** by adjusting the frequency of the reference waveform



Control Parameters: Voltage



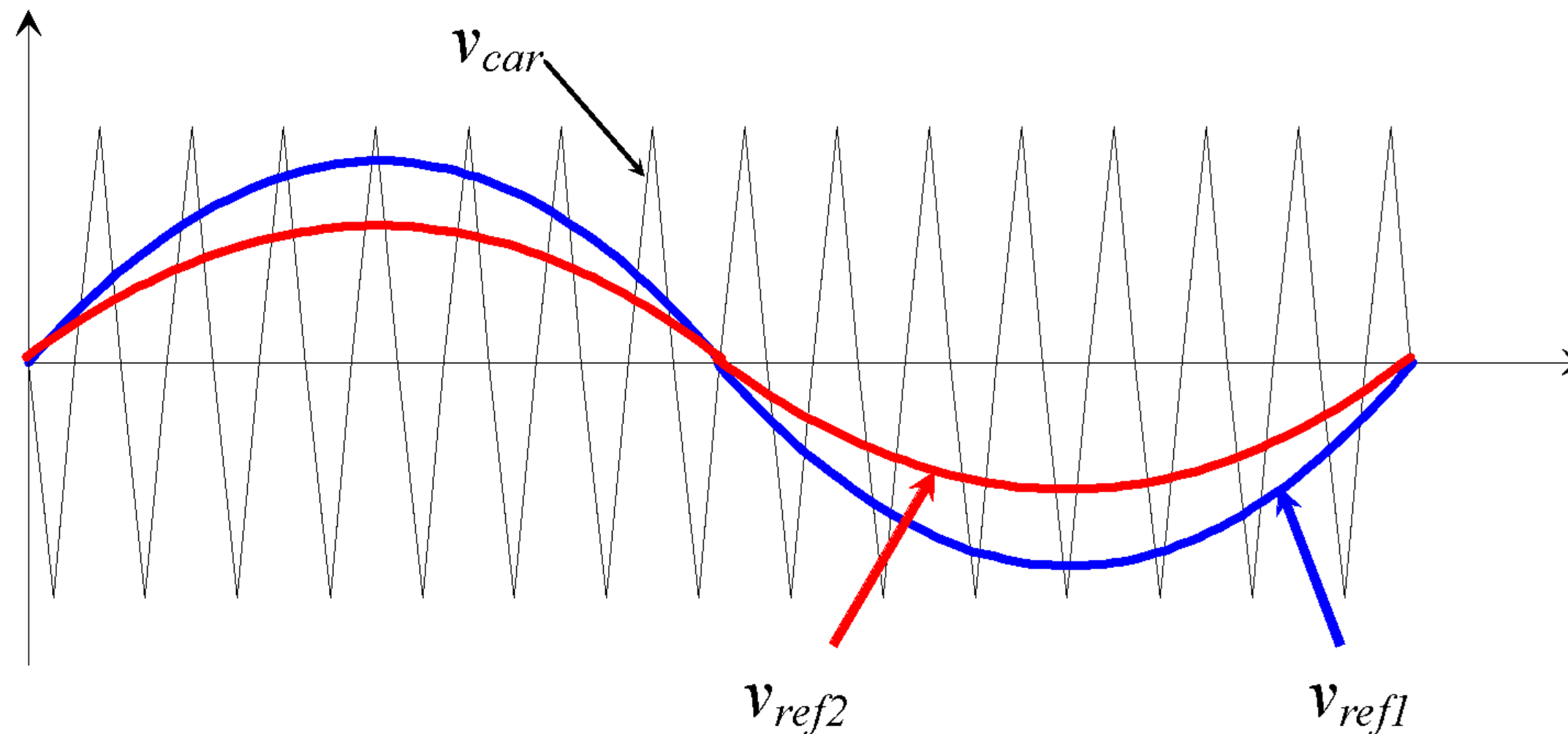
- **Voltage:** by adjusting the reference voltage and/or the triggering angle




Control Parameters: Phase Shift



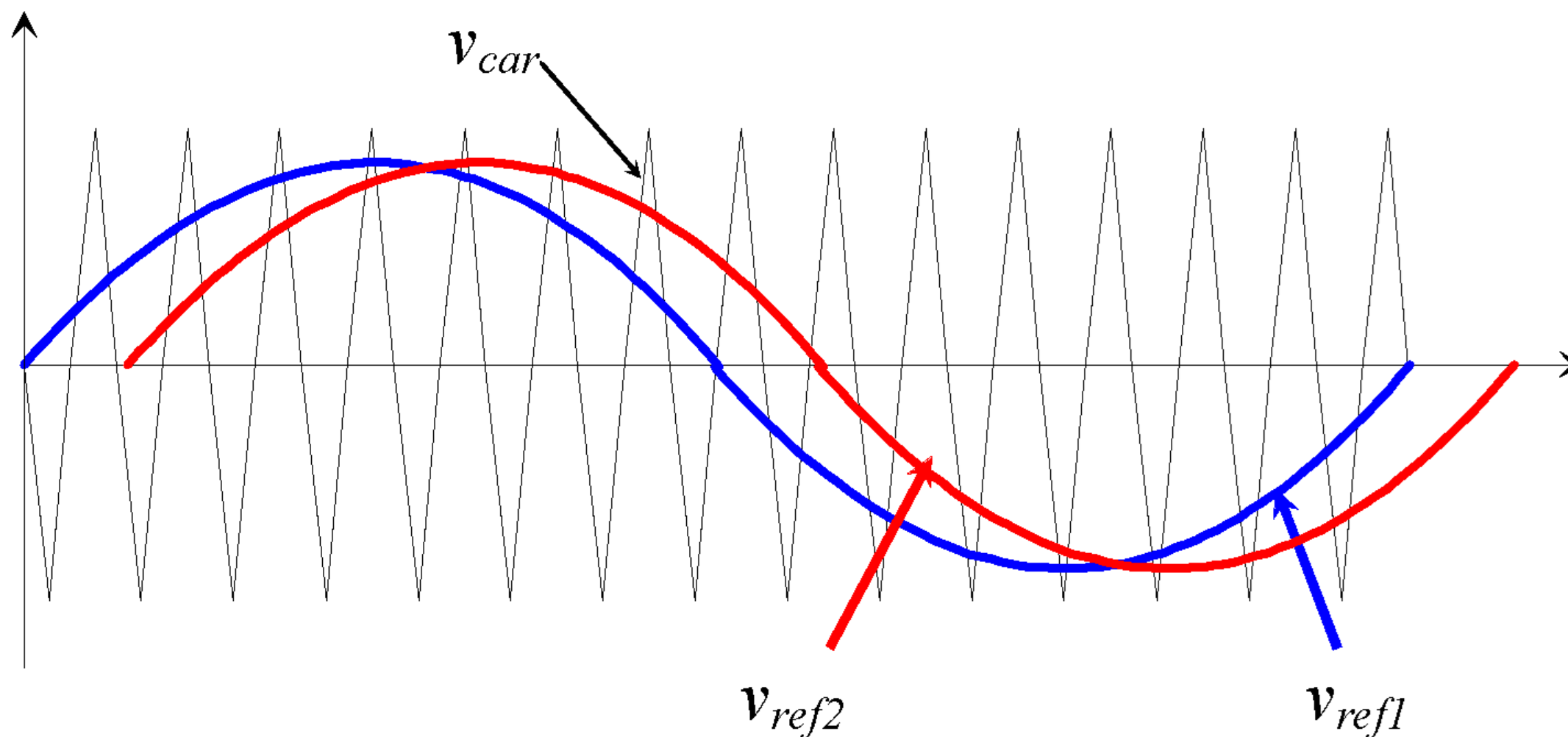- **Phase shift:** by adjusting the phase shift of the reference waveform with respect to the line voltage




Reduced Harmonics PWM Technique

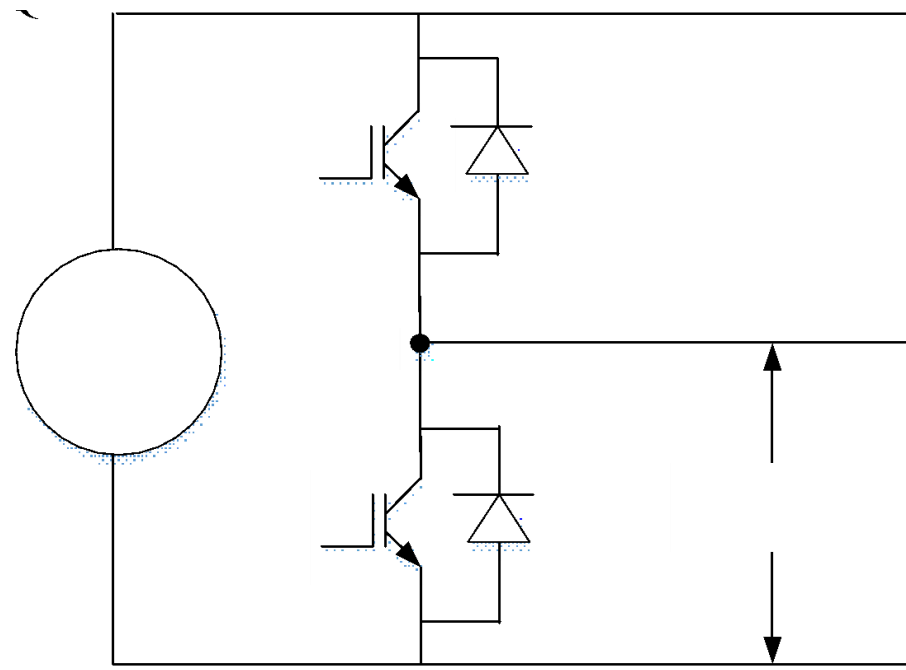

when Q_4 is closed, $v_{ao} = 0$

when Q_1 is closed, $v_{ao} = V_{dc}$

One cycle of high frequency carrier

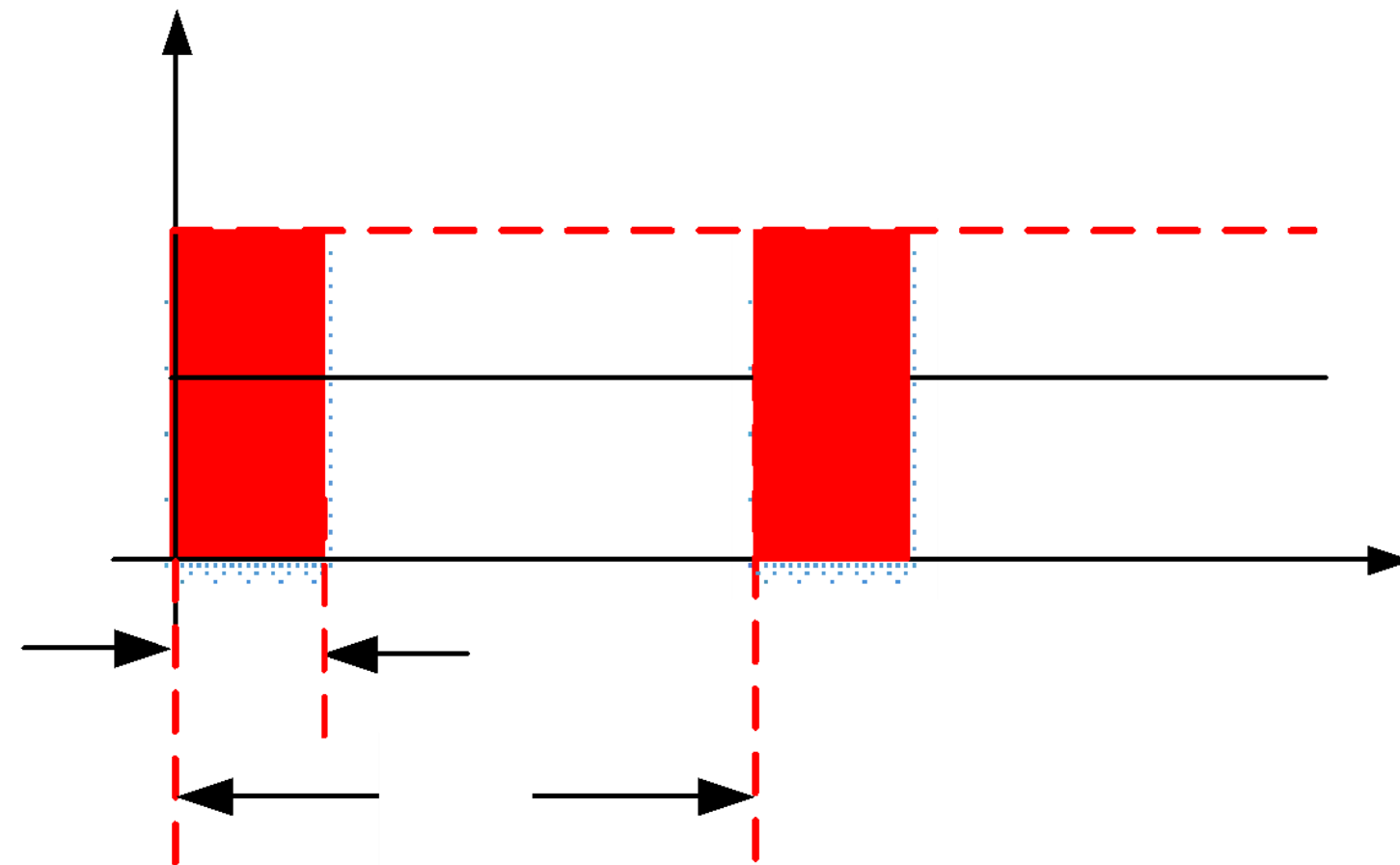

$$v_{ao} \approx V_{ao} = m V_{dc} = \frac{t_{on}}{\tau} V_{dc} = t_{on} f V_{dc}$$



Reduced Harmonics PWM Technique

$$v_{ao} = m_a V_{dc}$$

$$v_{bo} = m_b V_{dc}$$

$$v_{co} = m_c V_{dc}$$

$$m_a = 0.5 + k \sin(2\pi f_s t)$$

$$m_b = 0.5 + k \sin\left(2\pi f_s t - \frac{2\pi}{3}\right)$$

$$m_c = 0.5 + k \sin\left(2\pi f_s t + \frac{2\pi}{3}\right)$$

$$k = \frac{V_{max-r}}{V_{max-car}}$$

Reduced Harmonics PWM Technique

$$m_a = 0.5 + k \sin(2\pi f_s t)$$

$$m_b = 0.5 + k \sin\left(2\pi f_s t - \frac{2\pi}{3}\right)$$

$$m_c = 0.5 + k \sin\left(2\pi f_s t + \frac{2\pi}{3}\right)$$

$$v_{ab} = v_{ao} - v_{bo} = m_a V_{dc} - m_b V_{dc} = \sqrt{3} k V_{dc} \sin\left(2\pi f_s t - \frac{\pi}{6}\right)$$

$$v_{bc} = v_{bo} - v_{co} = m_b V_{dc} - m_c V_{dc} = \sqrt{3} k V_{dc} \sin\left(2\pi f_s t - \frac{5\pi}{6}\right)$$

$$v_{ca} = v_{co} - v_{ao} = m_c V_{dc} - m_a V_{dc} = \sqrt{3} k V_{dc} \sin\left(2\pi f_s t + \frac{\pi}{2}\right)$$



Reduced Harmonics PWM Technique

$$v_{ab} = \sqrt{3} k V_{dc} \sin \left(2\pi f_s t - \frac{\pi}{6} \right)$$

$$v_{bc} = \sqrt{3} k V_{dc} \sin \left(2\pi f_s t - \frac{5\pi}{6} \right)$$

$$v_{ca} = \sqrt{3} k V_{dc} \sin \left(2\pi f_s t + \frac{\pi}{2} \right)$$

$$v_{an} = k V_{dc} \sin(2\pi f_s t)$$

$$v_{bn} = k V_{dc} \sin \left(2\pi f_s t - \frac{2\pi}{3} \right)$$


$$v_{cn} = k V_{dc} \sin \left(2\pi f_s t + \frac{2\pi}{3} \right)$$

$$\bar{V}_{an} = \frac{k V_{dc}}{\sqrt{2}} \angle 0^\circ$$

$$\bar{V}_{bn} = \frac{k V_{dc}}{\sqrt{2}} \angle -120^\circ$$

$$\bar{V}_{cn} = \frac{k V_{dc}}{\sqrt{2}} \angle 120^\circ$$

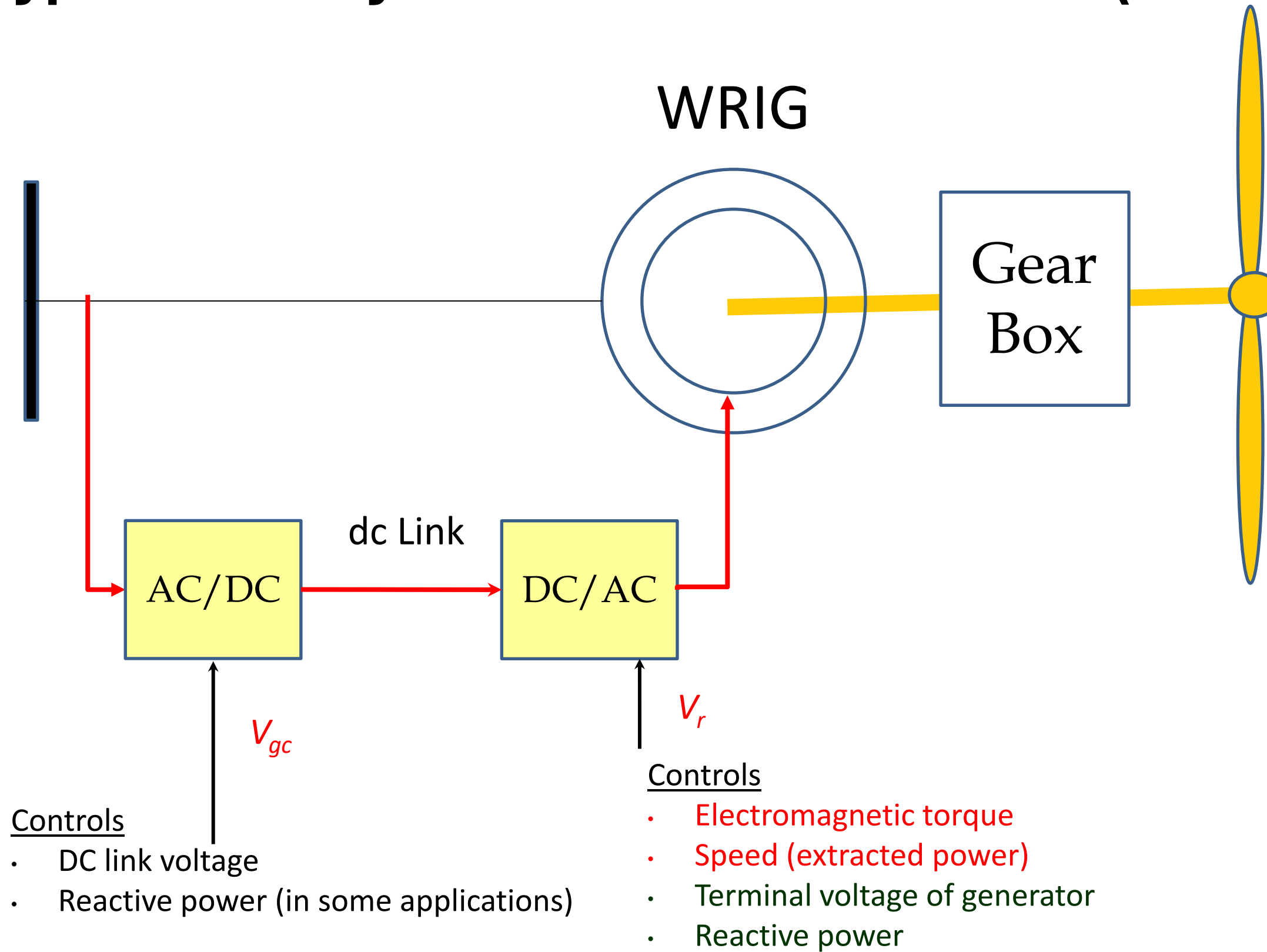Type 3: Doubly Fed Induction Generator (DFIG)





Key Features of DFIG

- The capacitor connected on the DC bus acts as a filter and a voltage source.
- The control system generates the control signals V_r and V_{gc} .
- The frequency of the injected voltage to the rotor is equal to the **desired** slip frequency

$$f_r = s_{new} f$$

- The rotor will eventually rotate at the new speed

Website

Use the	To check for announcements
course	
website:	To get copies of the lecture slides and other material
	To get the homework and project assignments

<https://lms.ttu.edu.jo/>

